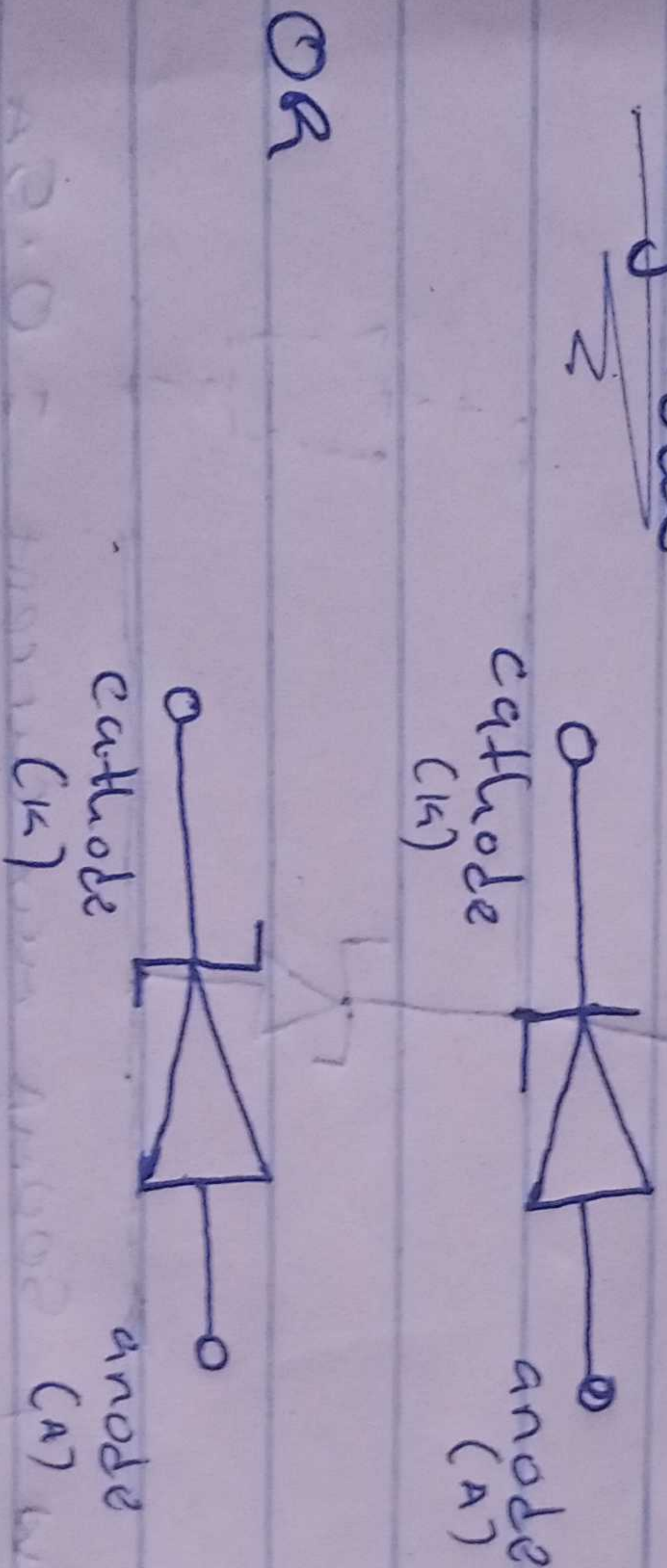



Chitima wisdom ENM1111E  
 18/ENL604/025  
 Electrical/Electronics  
 ENL6222

① The Zener diode is specially made to have a reverse voltage breakdown at a specific voltage. It's characteristics are otherwise very similar to common signal diodes. In breakdown the voltage across the Zener diode is close to constant over a wide range of currents thus making it useful as a shunt voltage regulator.



1: Symbol



I-V Characteristics Curve

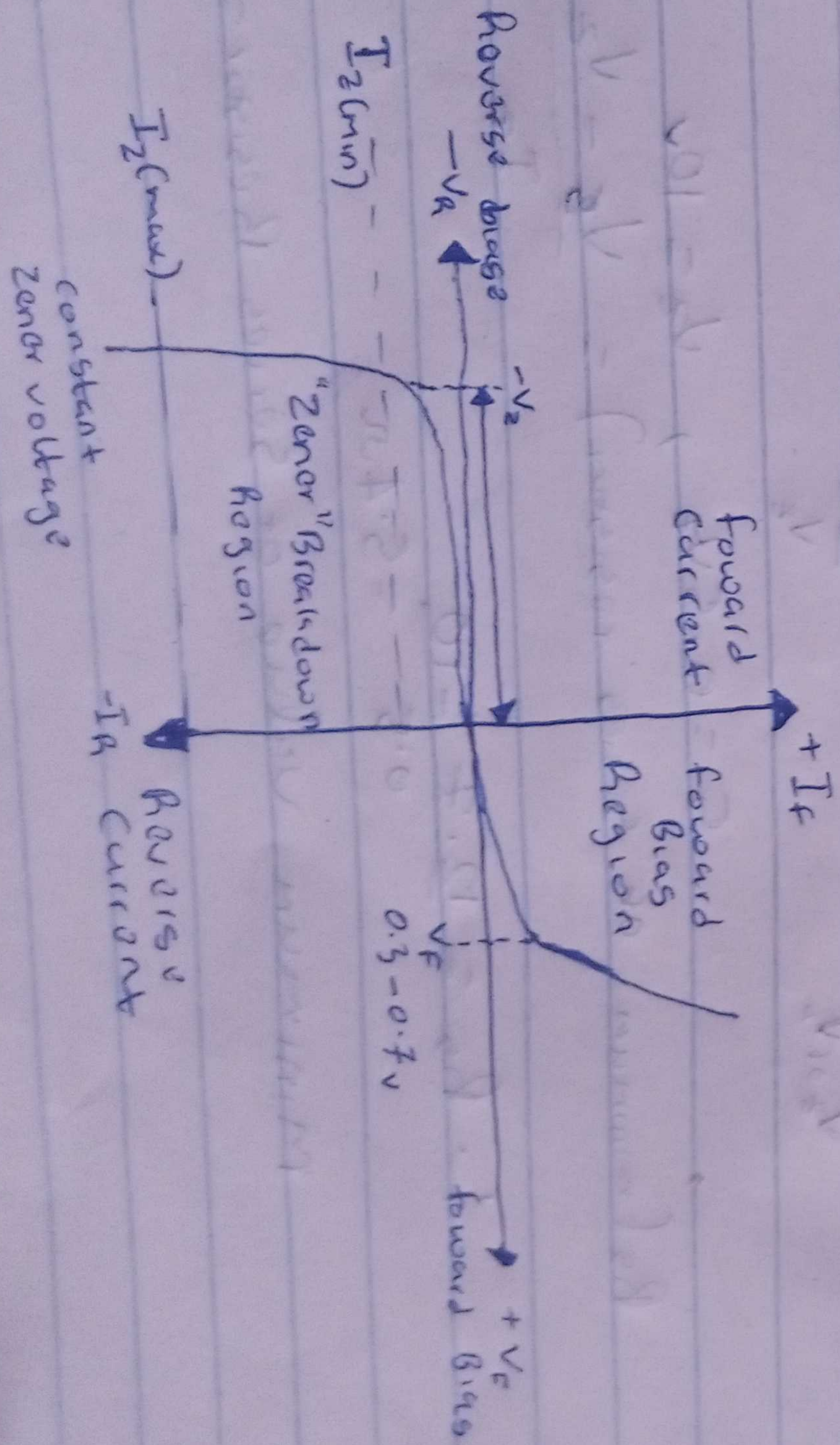

ii) Circuit diagram

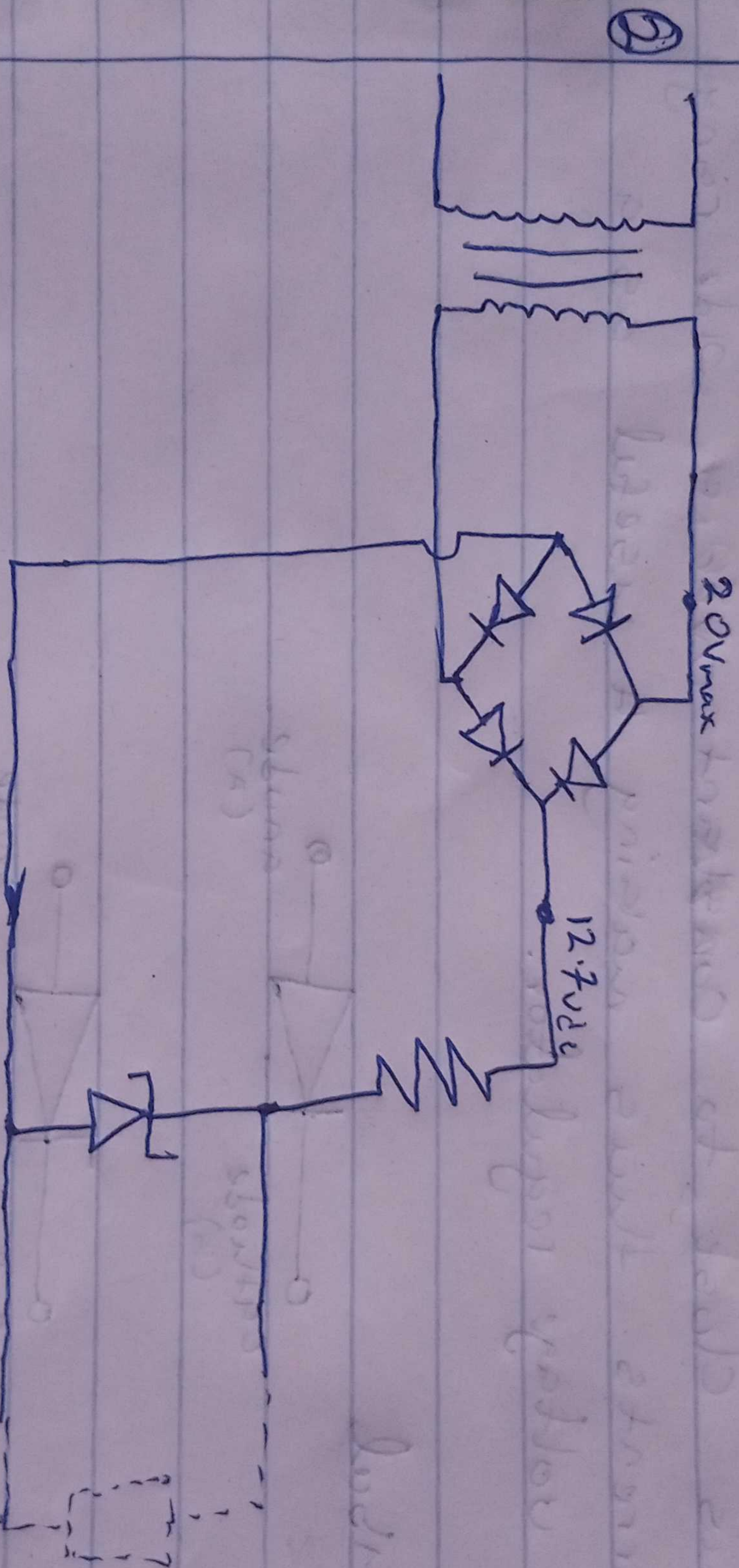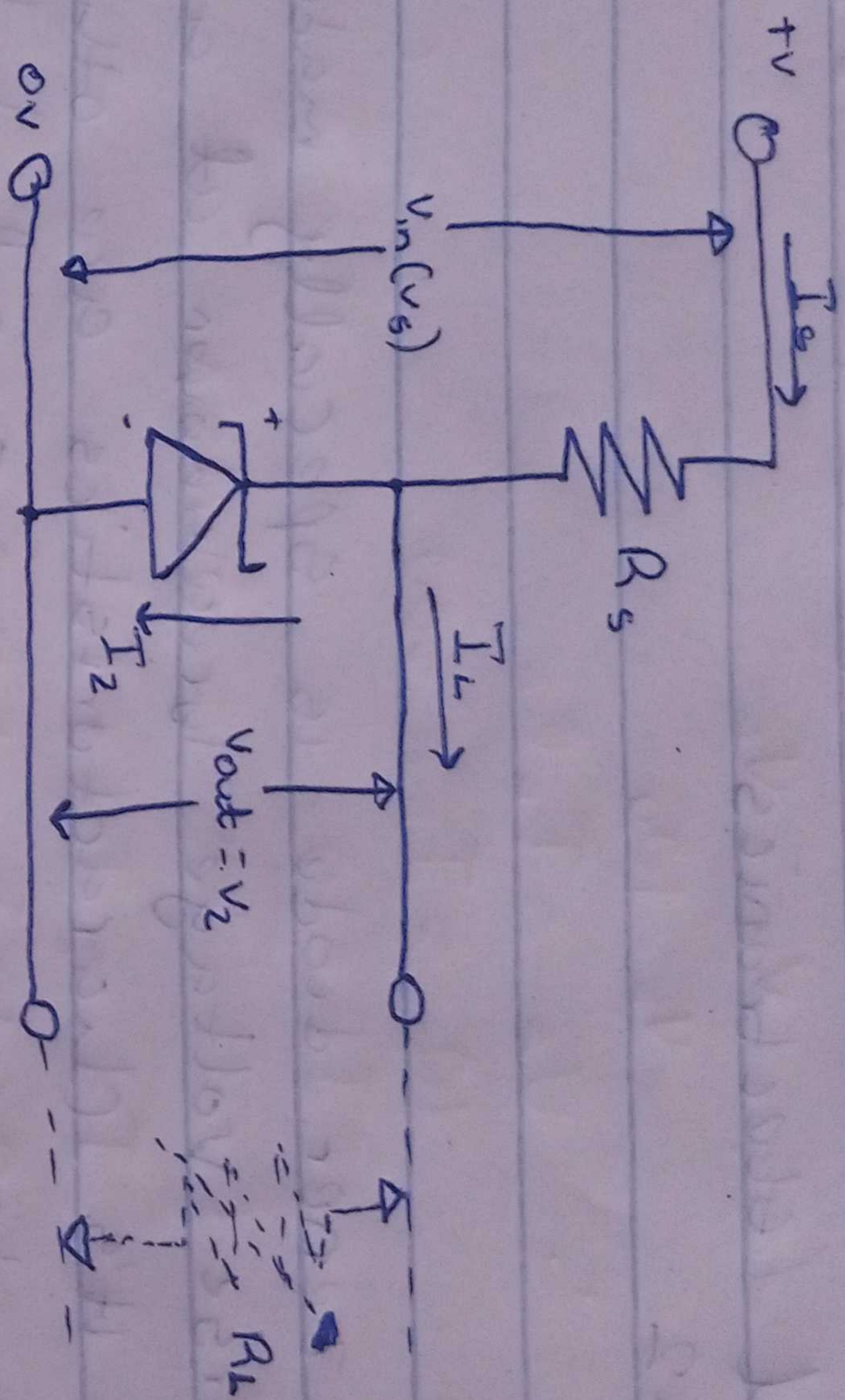

Zener rating is 5W, 500mA max current = 0.5A

$$I_{maxZ} = \frac{P}{V_z \times V_z} = 0.5 = \frac{5}{V_z}$$

$$5 = 0.5 V_z, \quad V_z = 10V$$

$$R_s (\text{minimum of series resistor}) = \frac{V_s - V_z}{I_z}$$

$$\therefore R_s = \frac{12.7 - 10}{0.5} = 5.4 \Omega$$

Minimum value of series resistor = 5.4Ω

⑪

Current across the diode at full load of 500m

$$\text{Since } V_Z = V_L$$

$$V_L = 10V$$

$$\therefore V_L = I_L R_L$$

$$10 = I_L \times 500$$

$$I_L = \frac{10}{500}$$

$$= 0.02A$$

$$I_S = I_Z + I_L$$

$$0.5 = I_Z + 0.02$$

$$I_Z = 0.5 - 0.02$$

$$I_Z = 0.48A = 480mA$$