
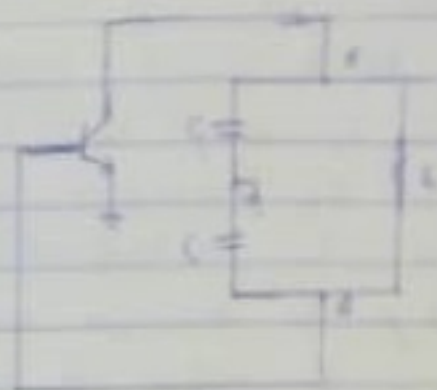


The Colpitts Oscillator

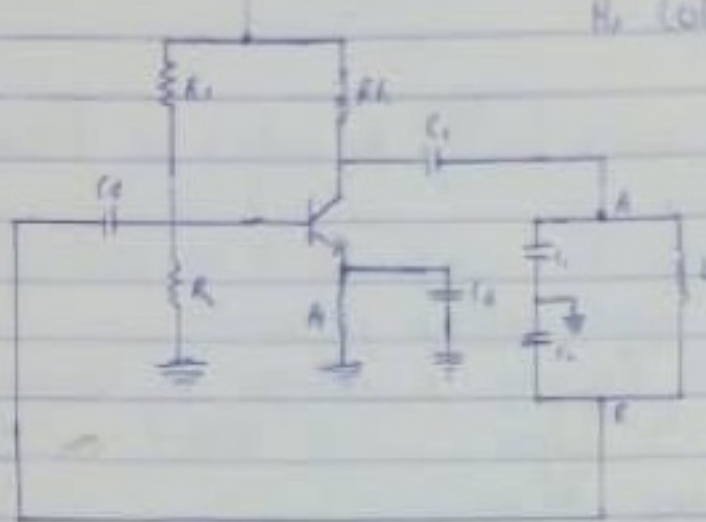

Colpitts Oscillator is an electronic oscillator which uses an inductor and capacitors to form an LC oscillator circuit. It is much similar to the Hartley oscillator except the addition of tank circuit. In Colpitts Oscillator the tank circuit consists of two capacitors in series and an inductor connected in parallel to the ~~inductor~~ series combination.

Fig: In the circuit diagram resistor R_1 and R_2 gives a voltage divider biasing to the transistor. Resistor R_C limits the collector current of the transistor. C_E is the input DC decoupling capacitor while C_e is the output decoupling capacitor. R_E is the emitter resistor and it mounts for thermal stability. C_E is the emitter bypass capacitor. Job of the emitter bypass capacitor is to bypass the amplified AC signal from dropping across R_E . The emitter bypass capacitor is not there, the amplified AC signal will drop across R_E and it will affect the DC biasing condition of the transistor and the result will be reduced gain. Capacitors C_1 , C_2 and inductor L form the tank circuit. Feedback to the base of transistor is taken from the junction of capacitors C_1 and inductor L in the network.

The feedback fraction $\beta = \frac{C_2}{C_1 + C_2}$

The oscillator to start, the voltage gain ($A\beta$) must be greater than 1 ($A\beta > 1$) or in other words, $A > \frac{1}{\beta}$. The frequency of oscillation (angular mutant ω) is given by the relation:

$$\omega = \frac{1}{\sqrt{LC}}$$

where C is the effective value of capacitance and equal to

$$\frac{C_1 C_2}{C_1 + C_2}$$

For a colpitts oscillator

- i. For the colpitts oscillator in 'a' where having the values of L & C are $C_1 = 100\text{pF}$ and $C_2 = 500\text{pF}$ find
 - i. The frequency of oscillation
 - ii. The feedback voltage if the input voltage is 10V
 - iii. The minimum gain if the frequency is changed by changing the value of the inductor 'L' above
 - iv. The value of C_1 be equal to 10
 - v. The new frequency of the oscillator for the "ii" above


Solution

~~1. The frequency of oscillation =~~
 ~~$f_o = \frac{1}{2\pi\sqrt{LC}}$~~
 $L = 40\text{mH} = 40 \times 10^{-3}\text{H}$
 $C_1 = 100\text{pF} = 100 \times 10^{-12}$, $C_2 = 500\text{pF} = 500 \times 10^{-12}$


1. Frequency of Oscillation =
 $f_o = \frac{1}{2\pi\sqrt{LC}}$
 $f_o = \frac{C_1 \times C_2}{L + C_1} = \frac{((100 \times 10^{-12}) \times (500 \times 10^{-12}))}{((500 \times 10^{-12}) + (100 \times 10^{-12}))}$
 $= 81.32 \times 10^{-11}\text{ s}$
 $\therefore f_o = \frac{1}{2\pi \times 81.32 \times 10^{-11} \times 10^{-11}}$
 $= 87.173\text{a kHz}$

ii. The feedback voltage = $\frac{V_o}{\text{gain}}$
 $V_o = 10\text{V}$
 $\text{Gain} = \frac{C_2}{C_1} = \frac{500}{100} = 5$
 Feedback voltage = $\frac{10}{5} = 2\text{V}$

Multistable

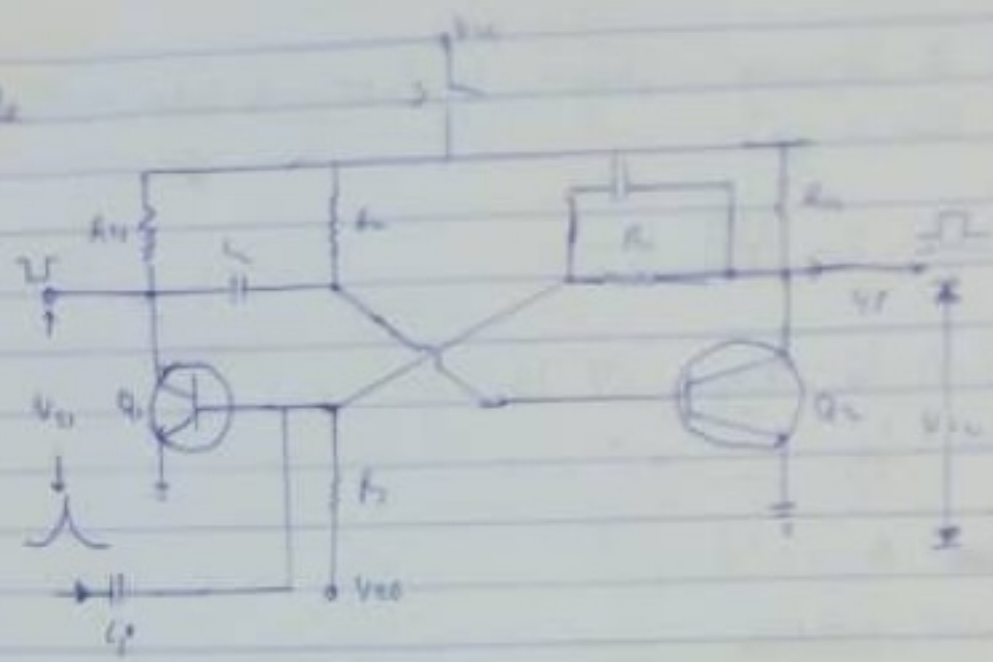

Bistable

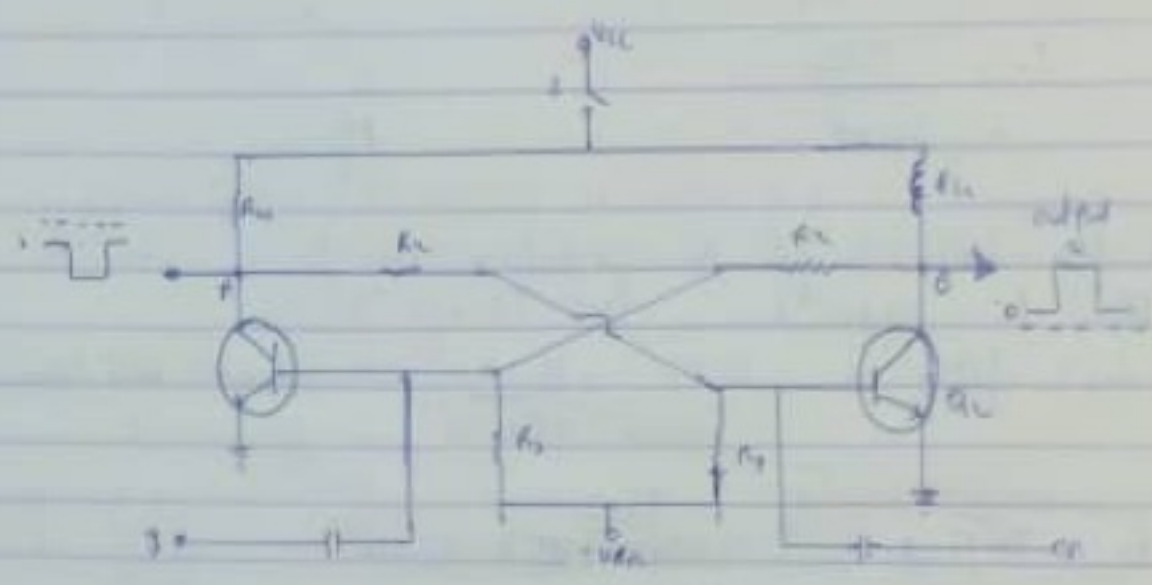

Calculate the value of the capacitor to be used in an astable multivibrator to provide a train of pulse pulses with a repetition rate of 100 kHz. Given $R_1 = R_2 = 10 \text{ k}\Omega$


Answer

Pulse width = $1 \mu\text{s} = 1 \times 10^{-6} \text{ s}$

$f = 100 \text{ kHz} = 100 \times 10^3 \text{ Hz}$

$R_1 = R_2 = 10 \text{ k}\Omega = 10 \times 10^3 \Omega$

using the formula

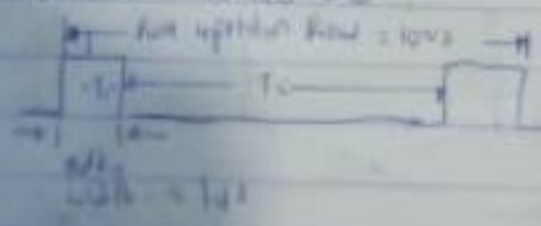

frequency of oscillation $f = \frac{1}{T_c}$

$100 \times 10^3 = \frac{1}{T_c}$

Minimum gain, if the frequency is changed by changing the value

$$Gain = \frac{C_2}{C_1}$$

$$= \frac{500}{100} = 5$$

iv. The value of C_2 for a gain of 10

$$Gain = \frac{C_2}{C_1}$$

$$10 = \frac{500 \times 10^{-12}}{C_1}$$

$$C_1 = \frac{500 \times 10^{-12}}{10}$$

$$= 50 \text{ pf}$$

v. The new frequency of the Oscillator for the '10' above

When $C_1 = 50 \times 10^{-12} \text{ F}$ $C_2 = 500 \times 10^{-12} \text{ F}$

$$f_{eq} = \frac{1}{2\pi\sqrt{LC_{eq}}} = \frac{1}{2\pi\sqrt{L \frac{C_1 C_2}{C_1 + C_2}}} = 45455 \times 10^{-4} \text{ Hz}$$


$$f = \frac{1}{2\pi\sqrt{LC_{eq}}} = \frac{1}{2\pi\sqrt{45455 \times 40 \times 10^{-12}}}$$

$$= 118 \text{ kHz}$$

Question 2.

Draw the circuit diagram of Astable, Monostable and Bistable multivibrator

Astable Multivibrator

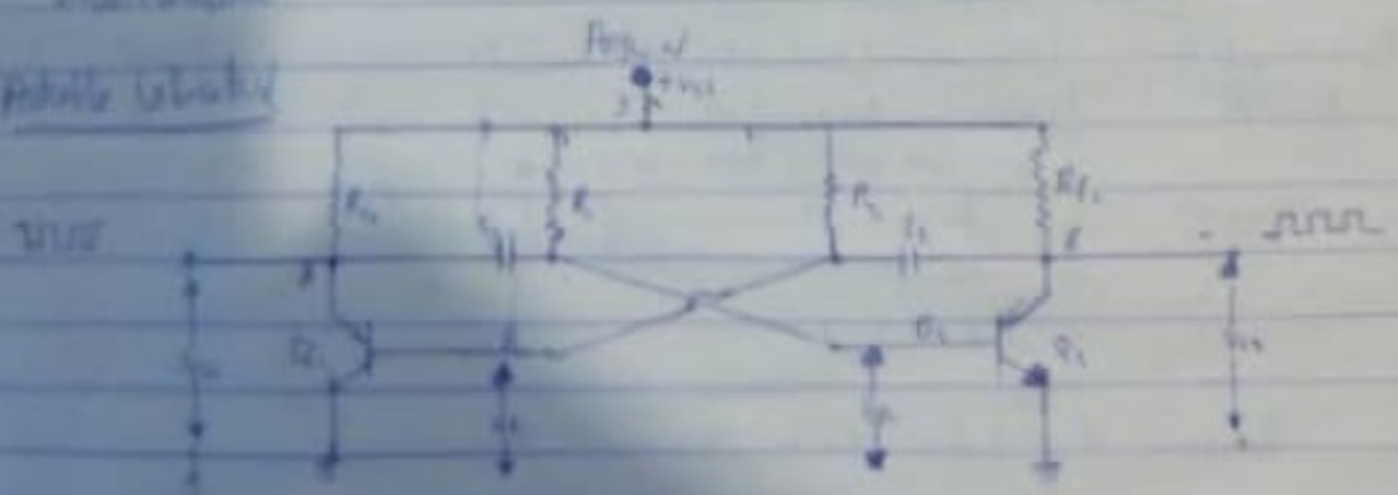

$t_c = \text{value} \times \text{frequency}$

$$T_c = \frac{1}{100} \times 10^3 = 10 \times 10^{-4} \text{ sec}$$

$$\text{width (1)} = 1 \times 10^{-4} = 0.69 R_1 C_1$$

$$C_1 = \frac{1 \times 10^{-4}}{0.69 \times 10 \times 10^3}$$

$$= 1.45 \times 10^{-11} \text{ f}$$

$$= 145 \text{ pF}$$

From (2),

$$R_2 \times 10 \times 10^{-4} = T_c / T_c$$

$$= 1 \times 10^{-4} / 7c$$

$$T_c = 10 \times 10^{-4} = 1 \times 10^{-4}$$

$$= 9 \times 10^5 \text{ sec}$$

$$T_c = 0.69 R_2 C_2$$

$$C_2 = \frac{T_c}{0.69 R_2}$$

$$C_2 = \frac{9 \times 10^5}{0.69 \times 10 \times 10^3}$$

$$= 1304 \times 10^{-11} \text{ f}$$

$$= 1304 \text{ pF}$$

c. Calculate the input pulse width for a monostable multivibrator for the design values of $R_1 = 2k\Omega$, $R_2 = 20k\Omega$, $C = 0.1\mu\text{f}$ and $V_{cc} = 12\text{V}$. Assume

$V_{be(sat)} = 0.2\text{V}$, $V_{ce(sat)} = 0.4\text{V}$ and $\beta = 50$

Solution

$V_{cc} = 12\text{V}$

Input pulse width,

$$T_c = R_1 C_1 \ln \frac{2V_{cc} - V_{be(sat)}}{V_{cc} - V_{be(sat)}}$$

$$= 2k\Omega \times 0.1 \times 10^{-6} \ln \frac{2 \times 12 - 0.2}{12 - 0.2}$$


$$= 1.0585 \mu\text{s}$$



c Explain briefly the basic principle crystal oscillator very appropriate circuit

Answer

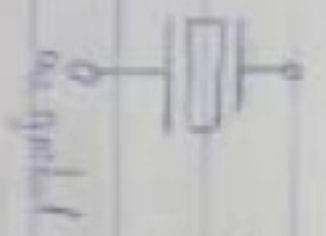A Crystal Oscillator is an electronic oscillator circuit that uses the mechanical resonance of a vibrating crystal of piezoelectric material to create an electrical signal with a precise frequency. These oscillators are built crystal and are used to generate highly stabilized output signal with frequency up to hertz to pHz accuracy as an crystal oscillator.



10



Function

The compiler is not responsible for the details it uses only for the actual parsing, because the input stream is huge and the compiler requires typed elements that are not being used.

Problems

It was regular hardware. It was special hardware.


Experimental steps

To input a regular hardware. It should require only input to operate, it could operate without any input.

Type of input

To input can be provided in any form. To input provided by hardware along with the hardware.

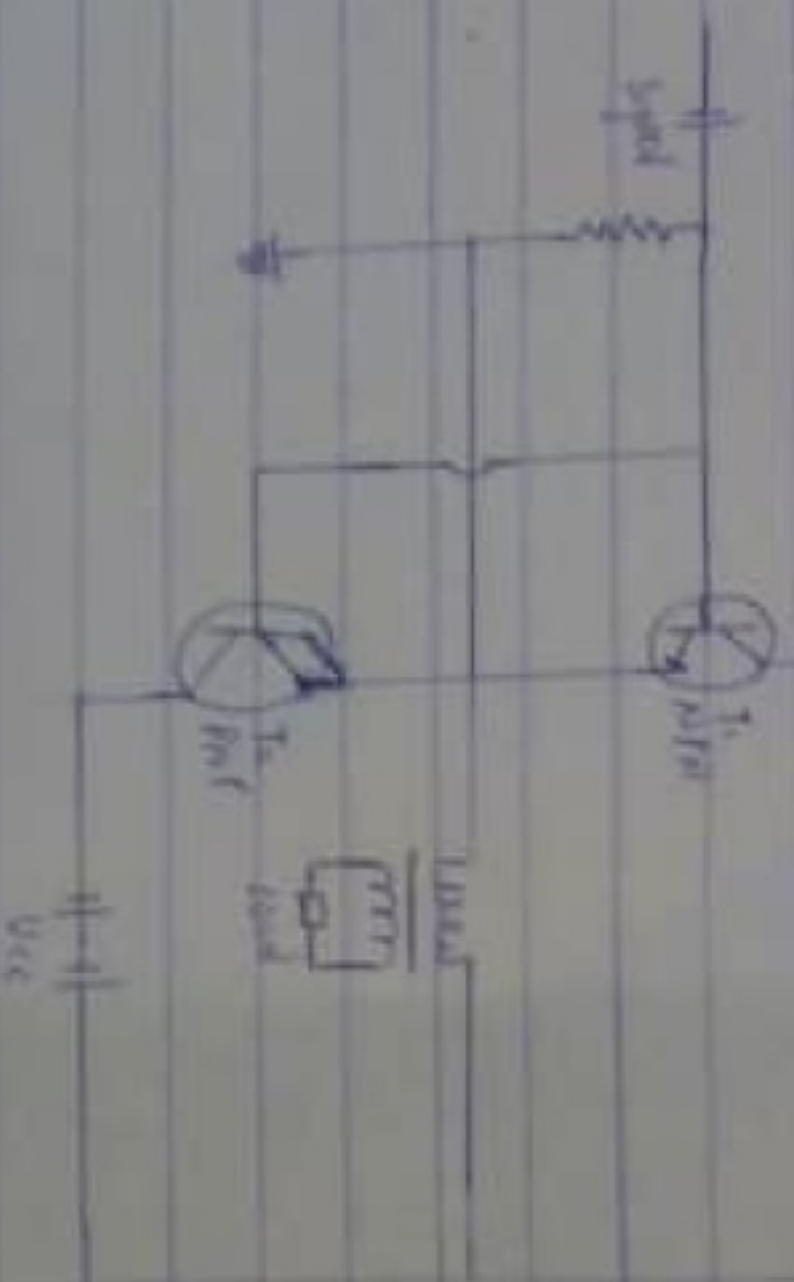1) Explain the following briefly
Compiler overhead



To avoid cross conduction or when transistor about a few hundred
 resistance in push pull configuration when the signal is applied, during
 the positive half cycle of the signal signal, the other transistor conduct
 and the first transistor cut off during the negative half cycle, the
 other transistor cut off and the first transistor conduct.

In this way the other transistor conduct during positive half cycle of
 the signal and first transistor conduct during negative half cycle of
 signal. The transistor can be replaced by each other. If at
 someplace any thing connected in push pull configuration of circuit,

$$2.810 \times 10^{-20} \text{ m}^3$$

c. Fermi level energy

$$E_F = \frac{h^2}{2m} \left(\frac{3n}{4\pi} \right)^{2/3}$$

$$E_F = \frac{h^2 n^{2/3}}{2m} = \frac{(6.626 \times 10^{-34})^2 \times (1.410 \times 10^{23})^{2/3}}{2 \times 9.1 \times 10^{-31}} = 0.051 \text{ eV}$$

$$= 0.051 \text{ eV}$$

$$E_F = \frac{h^2}{2m} \left(\frac{3n}{4\pi} \right)^{2/3}$$


$$= 99.2 \text{ eV}$$

Q. Factor of k_B required

$$Q = \frac{2.81 \text{ eV}}{k_B}$$

$$= \frac{2.81 \times 1.60 \times 10^{-19} \text{ J}}{1.38 \times 10^{-23} \text{ J/K}}$$

$$= 517$$

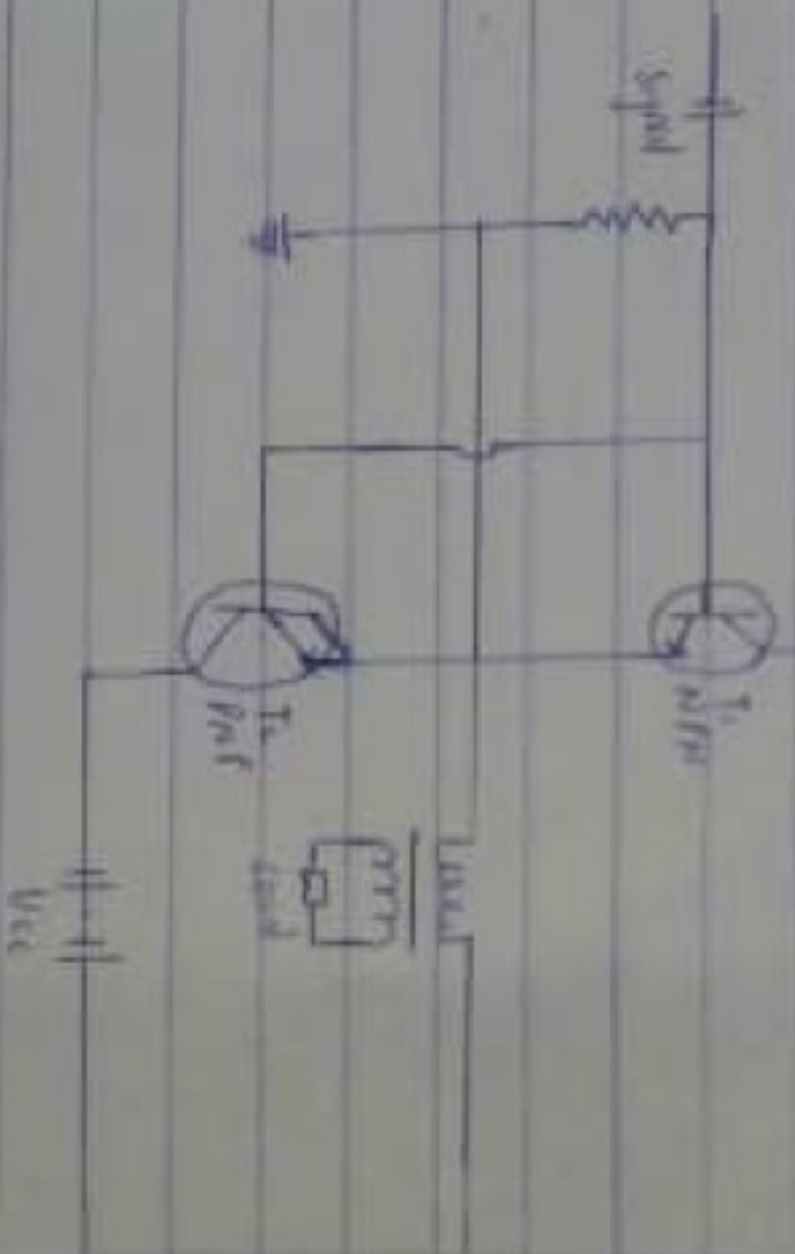

The circuit above employs an NPN transistor about a PNP transistor connected in push pull configuration when the input signal is applied, during the positive half cycle of the input signal, the NPN transistor conducts and the PNP transistor cut off. During the negative half cycle, the NPN transistor cut off and the PNP transistor conducts.

In this way, the NPN transistor amplifier during positive half cycle of the input while PNP transistor amplifier during negative half cycle of the input. In the load resistor, we have complementary to each other, yet at same time, they are connected in push pull configuration.