

MARIA OI KOPPEL-EREBELI

18/ENG04/051



EFFECT/ELECT

ENG222


BASIC EFFECT.

- Zener diodes are widely used as voltage references and as shunt regulators to regulate the voltage across small circuits. When connected in parallel with a variable voltage source, so that it is reverse biased, a zener diode conducts when the voltage reaches the diode's reverse breakdown voltage.


The zener diode is like a general-purpose signal diode consisting of a silicon P-N junction. When biased in the forward direction it behaves just like a normal signal diode passing the rated current, but as soon as a reverse voltage of the device, the diode's breakdown voltage is reached at which point a process called Avalanche Breakdown occurs in the semiconductor depletion layer and a current starts to flow through the diode to limit this increase in voltage.

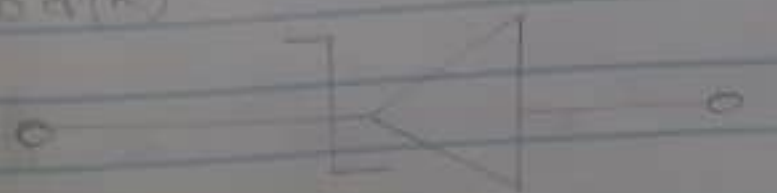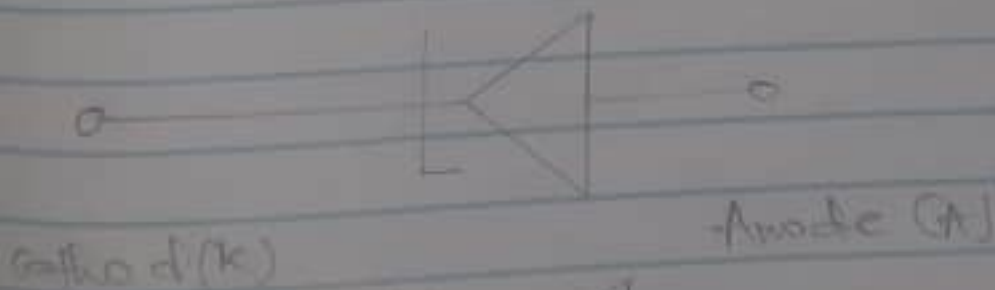

SYMBOL.

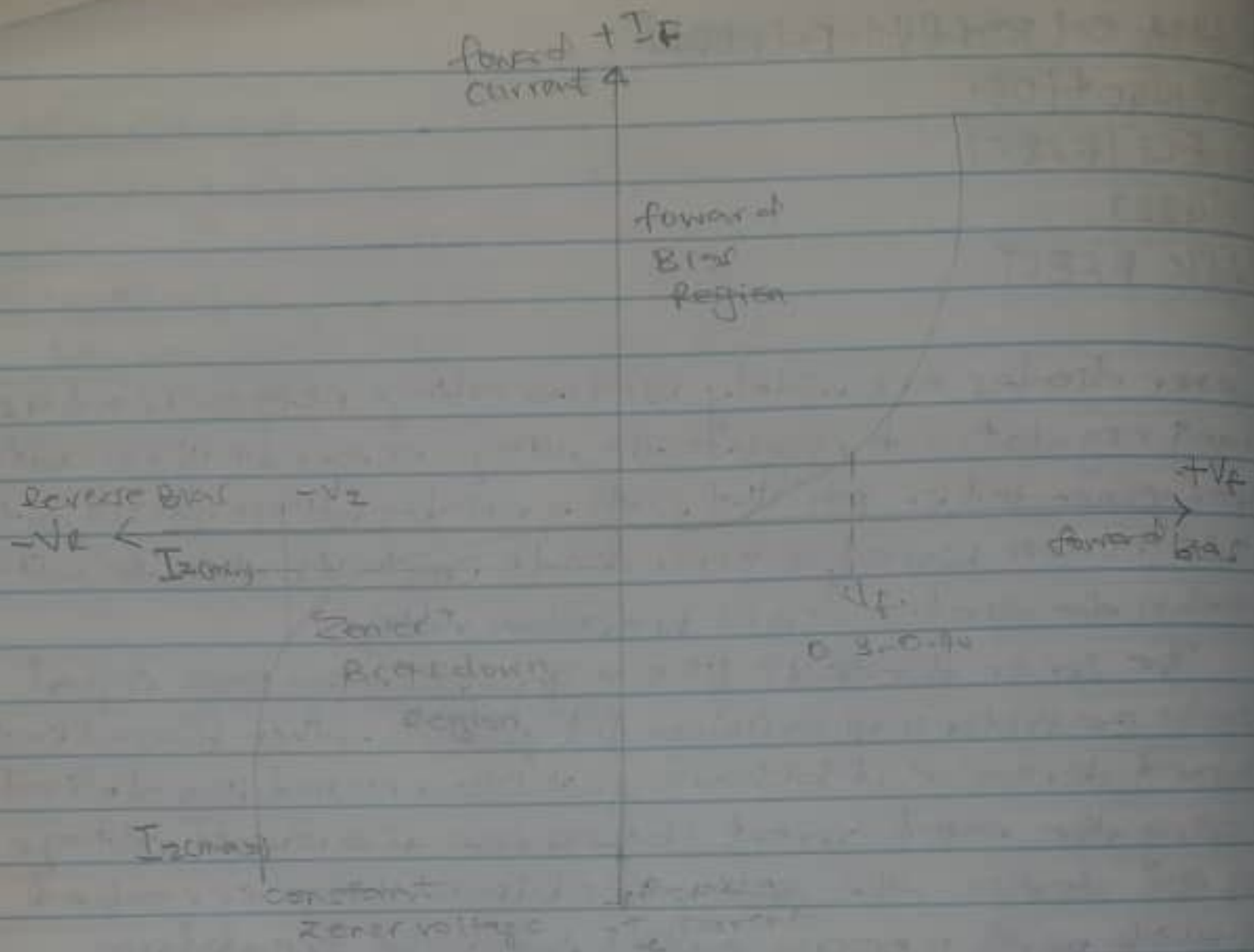

ZENER DIODE I-V Characteristic CURVE

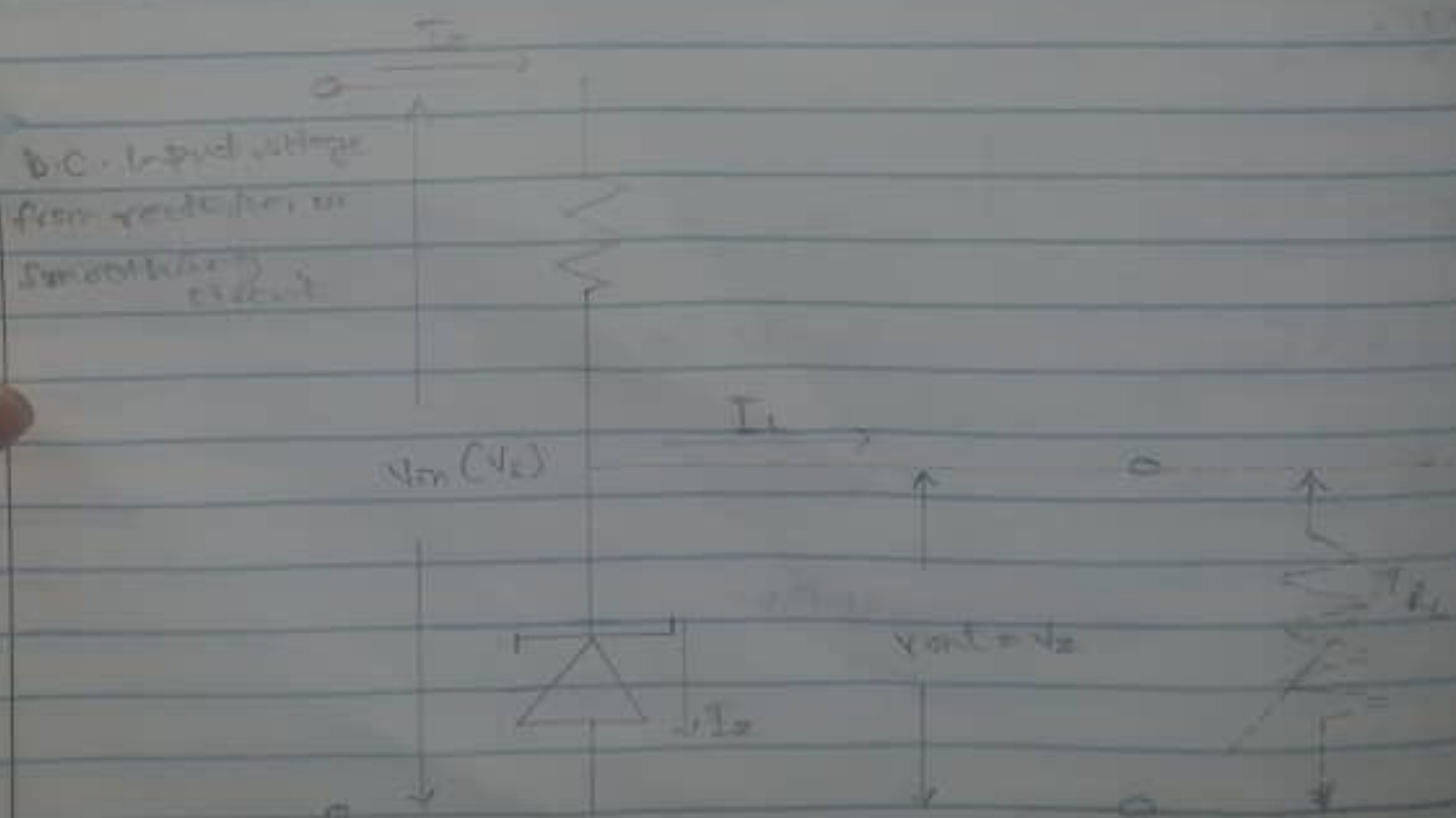

ZENER DIODE CIRCUIT diagram

$$\text{Sol } I_2 = 500 \text{ mA} = 500 \times 10^{-3}$$

$$P_3 = 5 \text{ W}$$

$$\sqrt{e} \text{ } 20 \text{ V}_{\text{max}} = \sqrt{e} C = \frac{2 \text{ V}_m}{\sqrt{\pi}}$$

$$= \frac{2 \times 20}{\sqrt{\pi}}$$

$$= 12.73 \text{ V}_{\text{DC}}$$

$$\text{Recall } P = IV$$

$$V_2 = \frac{P_2}{I_2} = \frac{5}{500 \times 10^{-3}}$$
$$= 10 \text{ V}$$

$$\text{Also Recall } V_1 + V_2 = V_3$$

$$\therefore V_1 = V_3 - V_2$$
$$= 12.73 - 10$$
$$= 2.73 \text{ V}$$

$$V_1 = IR$$

$$R = \frac{V}{I}$$

$$= \frac{2.73}{500 \times 10^{-3}}$$

$$= 5.46 \text{ } \Omega$$

$$\text{Sol } I_3 = I_2 + I_1$$

$$= I_1 = \frac{V_1}{R}$$

$$= \frac{2.73}{500}$$

$$= 0.02 \text{ A}$$

$$= 20 \text{ mA}$$

$$\text{Recall } I_3 = I_2 + I_1, \therefore I_2 = I_3 - I_1$$
$$= 500 \text{ mA} - 20 \text{ mA}$$

$$= 480 \text{ mA}$$

$$= 0.48 \text{ A}$$