
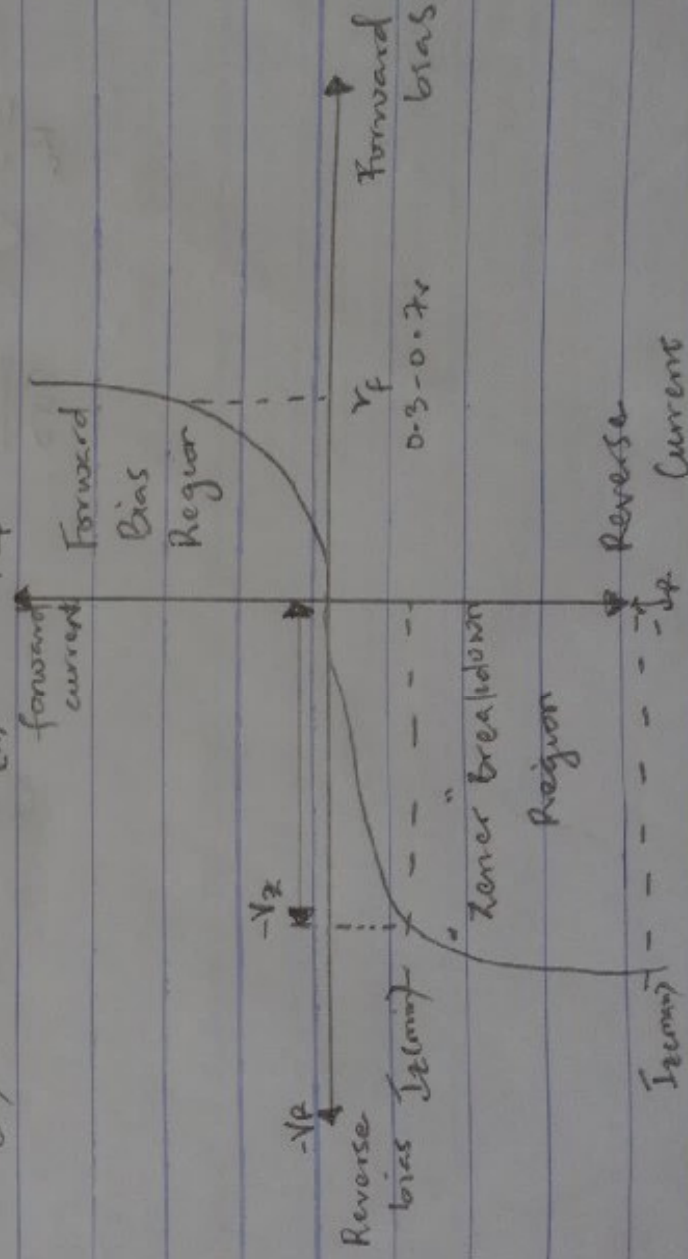



Name: Sule Mubarak A.
DEPT: CIVIL ENGINEERING
MAT. No.: 18/FHG03/055
COURSE: BASIC ELECT ENG.
DATE: 29-04-2020

Assignment.

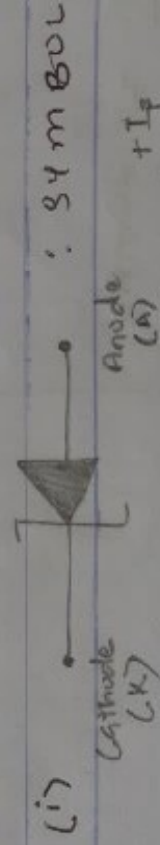1. → When a zener diode regulator is like a general purpose signal diode consisting of a PN junction. When biased in the forward direction it behaves just like a normal signal diode passing the rated current but as soon as a reverse voltage is applied across, the zener diode exceeds the rated voltage of the device, the diodes breakdown voltage is reached at which point a process called "Avalanche Breakdown" occurs in the semiconductor depletion layer and a current starts to flow through the diode to limit this increase in voltage.



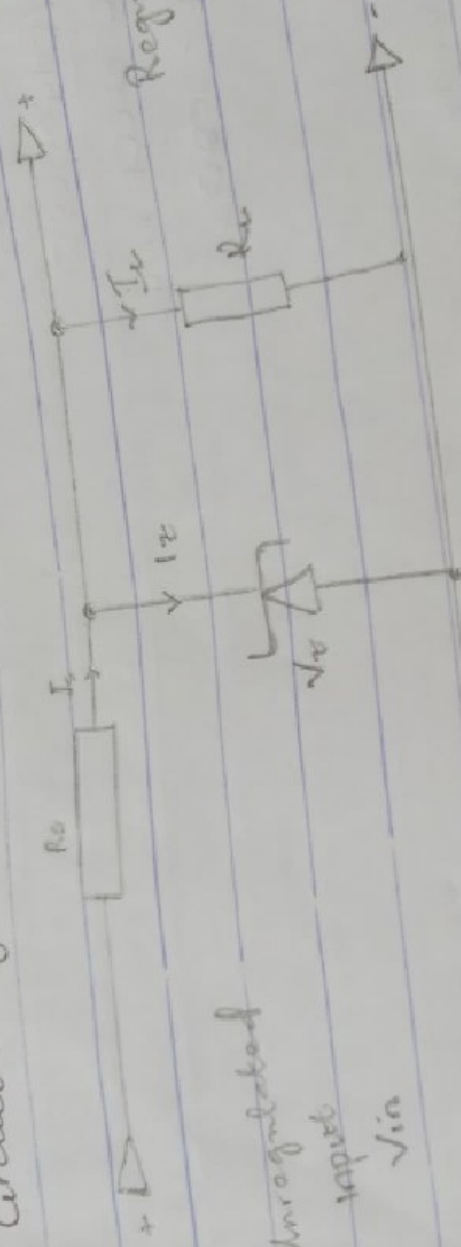(1) Circuit diagram for zener diode regulator.



Unregulated
input
 V_{in}

Regulated
Output
 V_0

-

(2) Minimum value of the series resistor, R_s

$$I_z = 500 \text{ mA}$$

$$R_s = \frac{V_s - V_z}{I_z}$$

$$V_s = 20 \text{ V}$$

Watts
Voltage

=

Watts
Voltage

Since

10V

=

$$V_z = \frac{5}{500 \times 10^{-3}}$$

20 Ω

(25)

Minimum value,

Current = 500 mA

power = 5W

$V_{max} = 20V$

max current = watts/voltage

500 mA = 5V

$V = 5 / 500 \times 10^{-3} = 10 \text{ volts}$

$V_{dc} = \frac{2V_{max}}{\pi} = \frac{2 \times 20}{\pi} = 12.732V$

$R_s = \frac{V_s - V_c}{I_c} = \frac{20 - 10}{500 \times 10^{-3}} = 5.46 \Omega$

$R_s = 5.46 \text{ ohms}$

b) $V_c = IR$

$I = V/R = 10 / 500 = 20 \text{ mA}$

$R_a = I_c + I_r$

500 mA = $R_c + 20 \text{ mA}$

$R = 500 \text{ mA} - 20 \text{ mA} = 480 \text{ mA}$