

NAME: ALFA FATIMA AHMED

MATRIC NO: 18/ENG06/008


DEPARTMENT: CHEMICAL ENGINEERING

COURSE: ENG 222


1) Describe a Zener diode regulator

A regulator provides a constant output voltage to a Load connected in parallel with it in spite of the ripples in the supply voltage or the variation in the Load current and the zener diode will continue to regulate the voltage until the diodes current falls below the minimum $I_{Z(min)}$ value in the reverse breakdown region.

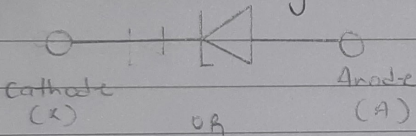
2) Sketch the symbol and I-V characteristics curve.



SYMBOL.

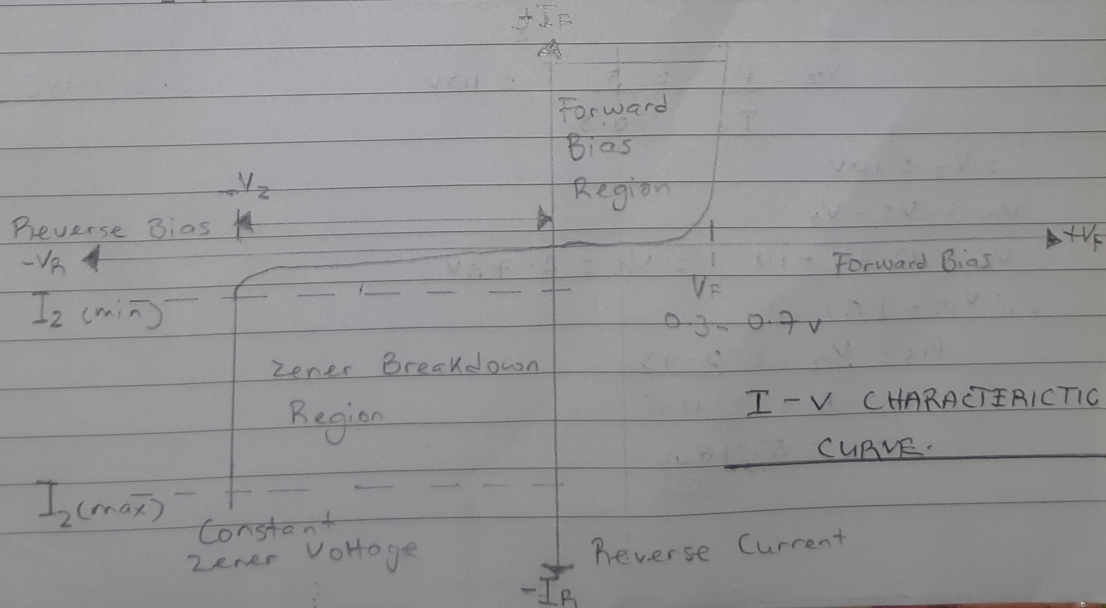

ii) Sketch and Label the circuit diagram

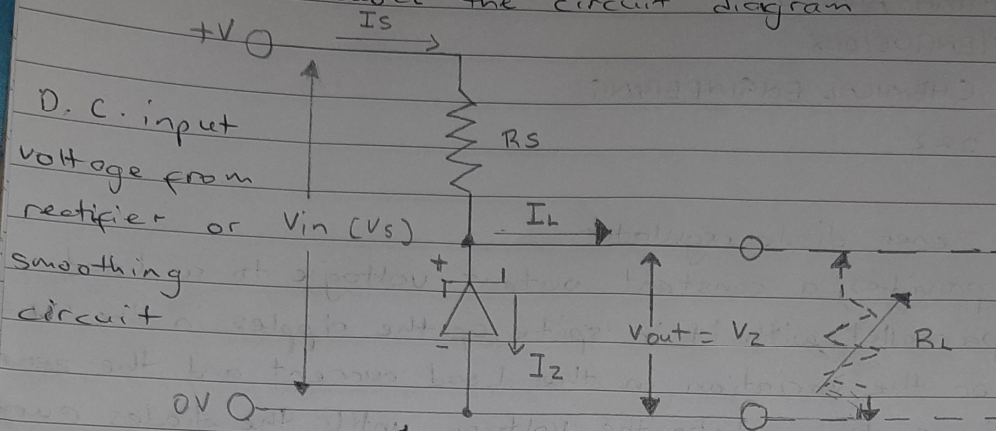

2) Max power = 5W

$$I_S = 500 \text{ mA} = 0.5 \text{ A}$$

$$V_{\text{max}} = 20 \text{ V}_{\text{max}}$$

$$V_{\text{max to D.C}} = \frac{2V_{\text{max}}}{\pi}$$

$$V_S = \frac{2 \times 20}{\pi} = 12.73 \text{ V}$$

$$I_S = (\text{Max current}) = \frac{P}{V_Z}$$

$$V_Z = \frac{P}{I_S} = \frac{5}{0.5} = 10 \text{ V}$$

$$= V_Z = 10 \text{ V}$$

$$V_R = V_S - V_Z$$

$$V_R = 12.73 - 10 = V_R = 2.73 \text{ V}$$

$$\therefore V_R = I R_S$$

$$R_S = \frac{V_R}{I} = \frac{2.73}{0.5}$$

$$I = 0.5$$

$$R_S = 5.46 \Omega$$

$$\text{ii) } I_L = \frac{V_Z}{R_L}$$

$$V_Z = 100$$

$$R_L = 500$$

$$I_L = \frac{100}{500} = 0.02\text{A} = 20\text{mA}$$

$$I_Z = I_S - I_L$$

$$= 500 - 20 = 480\text{mA}$$