
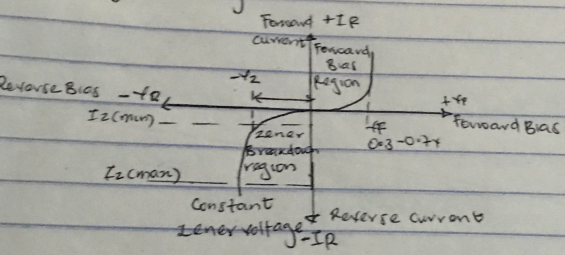


Aigbonoga Emmanuel
 18/ENG 06/006
 Mechanical Engineering

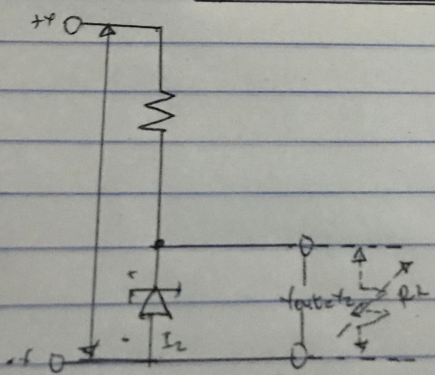A Zener diode is always operated in its reverse biased condition. As such a simple voltage regulator circuit can be designed using a Zener diode to maintain a constant DC output voltage across the load in spite of variations in input voltage or changes in the load current.




I-V characteristics curve




input voltage or changes in the load current. designed using a zener diode to

ii)

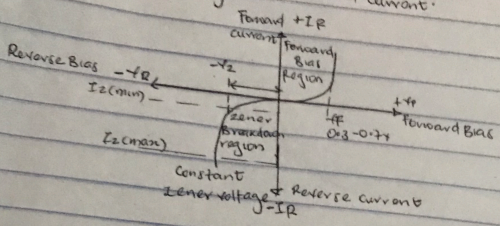

ii)

I-V characteristics curve

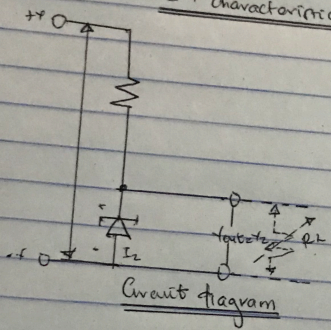

3)

$V_s = 20V$ $I_z = 500mA = 500 \times 10^{-3} A$

$V_z = \frac{\text{power}}{\text{current}} = \frac{5}{500 \times 10^{-3}} = 10V$

$R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{0.5}$

$R_s = 20\Omega$

$R_L = 500\Omega$

$I_L = \frac{V_z}{R_L} = \frac{10}{500} = 0.02A$