

Adebokun Precious Adeola

181ENG021006



Computer-Engineering


ENG 222

Basic Electrical Engineering II

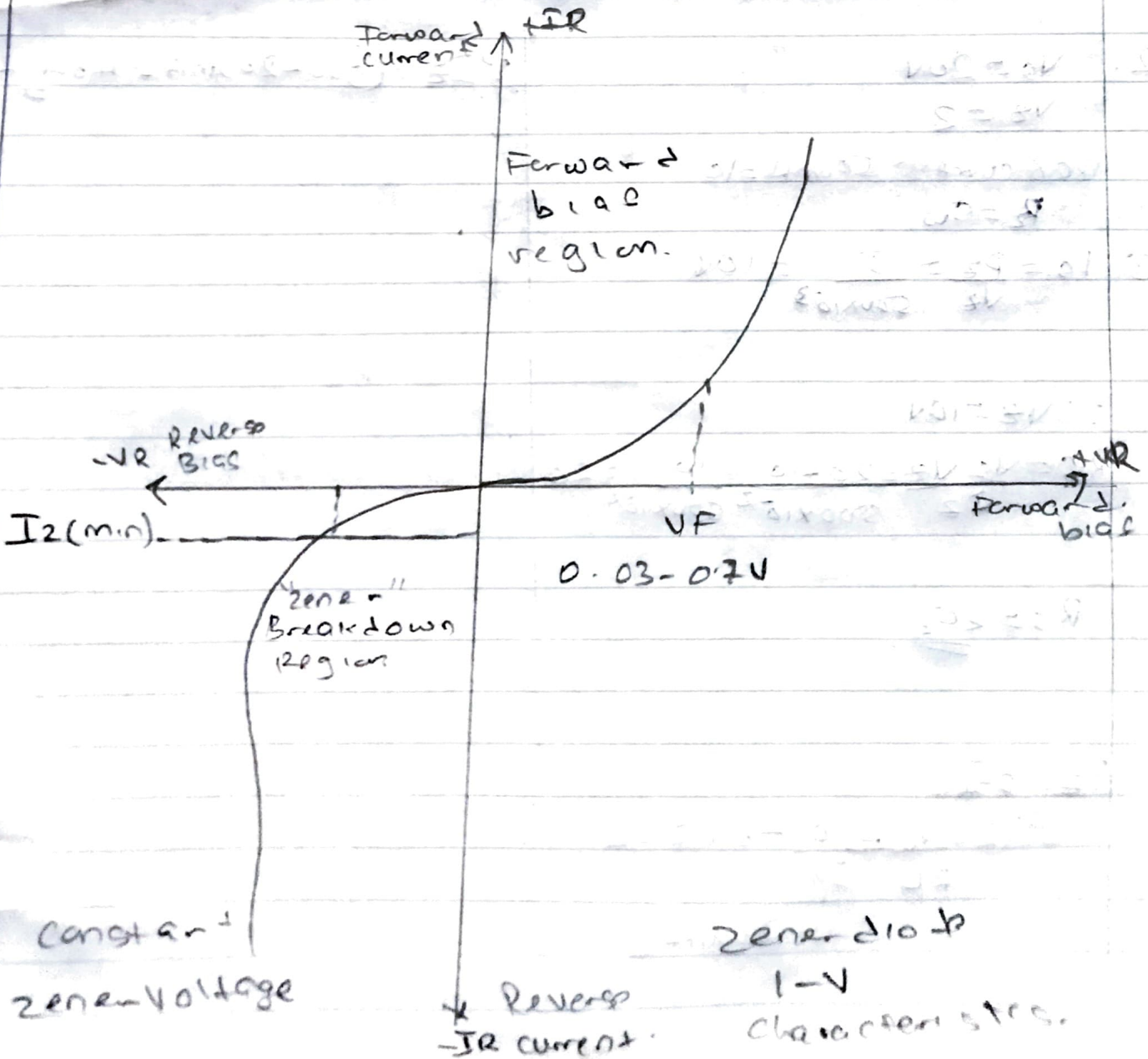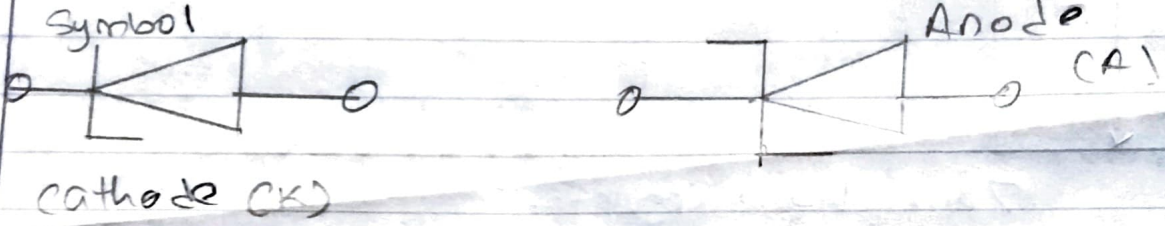(F) A Zener diode is a diode similar to the standard PN junction diode but they are specially designed to have low and specified reverse Break down voltage.

It is a type of diode that allows current to flow in the conventional manner - from its anode to its cathode i.e when the anode is positive with respect to the cathode.



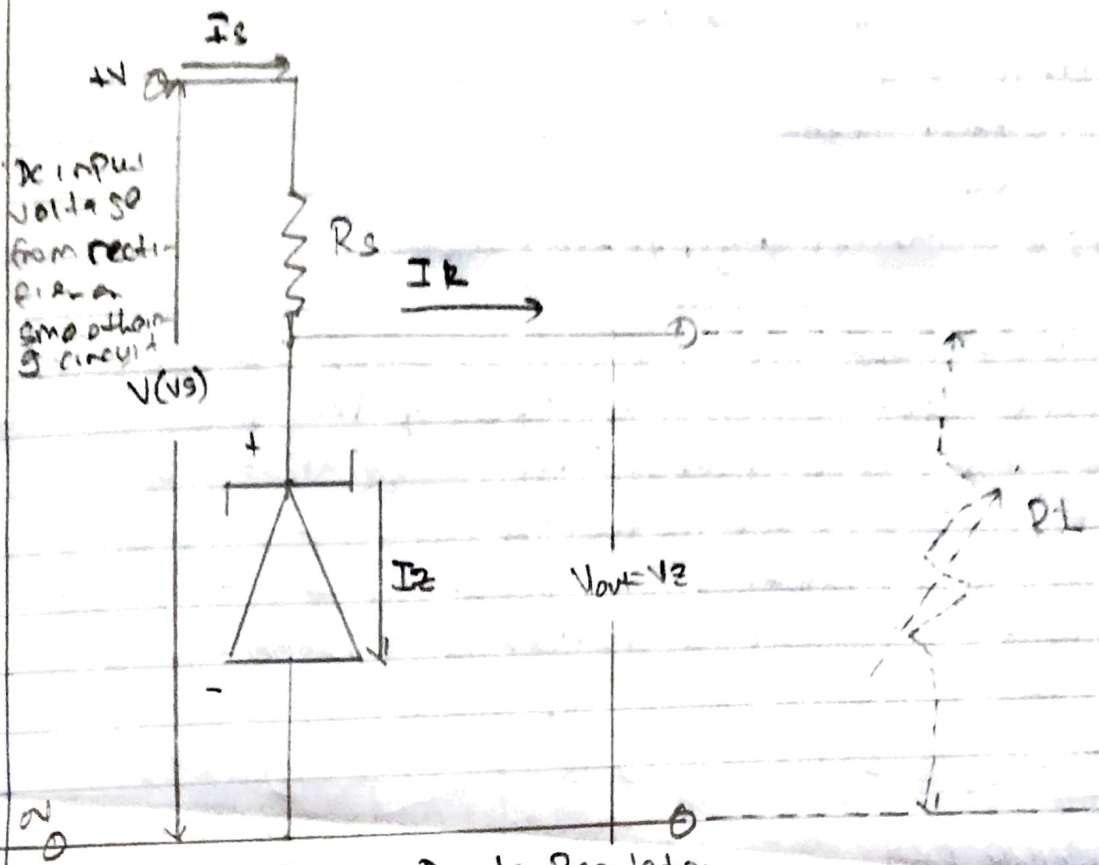

Zener Diode Regulator.

2. $V_s = 20V$
 $V_Z = 2$

max current $500mA = 1c$
 $R_s = 500$

① $I_s = \frac{P_Z}{V_Z} = \frac{5}{500 \times 10^{-3}} = 10A$

$\therefore V_Z = 10V$

$R_s = \frac{V_s - V_Z}{I_Z} = \frac{20 - 10}{500 \times 10^{-3}} = \frac{10}{500 \times 10^{-3}} = 20$

$R_s = 20\Omega$

$I_Z = 10 - I_L$

$P_{RL} = \frac{V_L^2}{R_L} = \frac{10^2}{500} = 0.02W$
 $= 20mA$

$\therefore I_Z = (500 - 20)mA = 480mA$