


Name: Arush Jesse Gokulm



Mat No: 18/EN403/013

Dept: Civil Engineering


1) Zener diodes are widely used as voltage regulators and a shunt regulators to regulate the voltage across small circuits. When connected in parallel with a variable voltage source so that it is reversed biased, a Zener diode conducts when the voltage reaches the diodes reverse breakdown voltage.

(i)

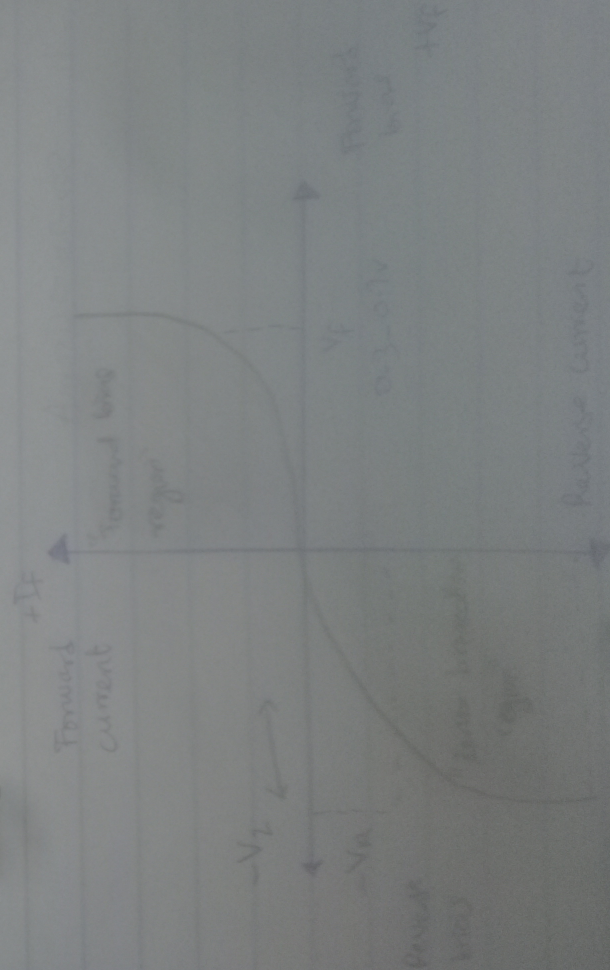

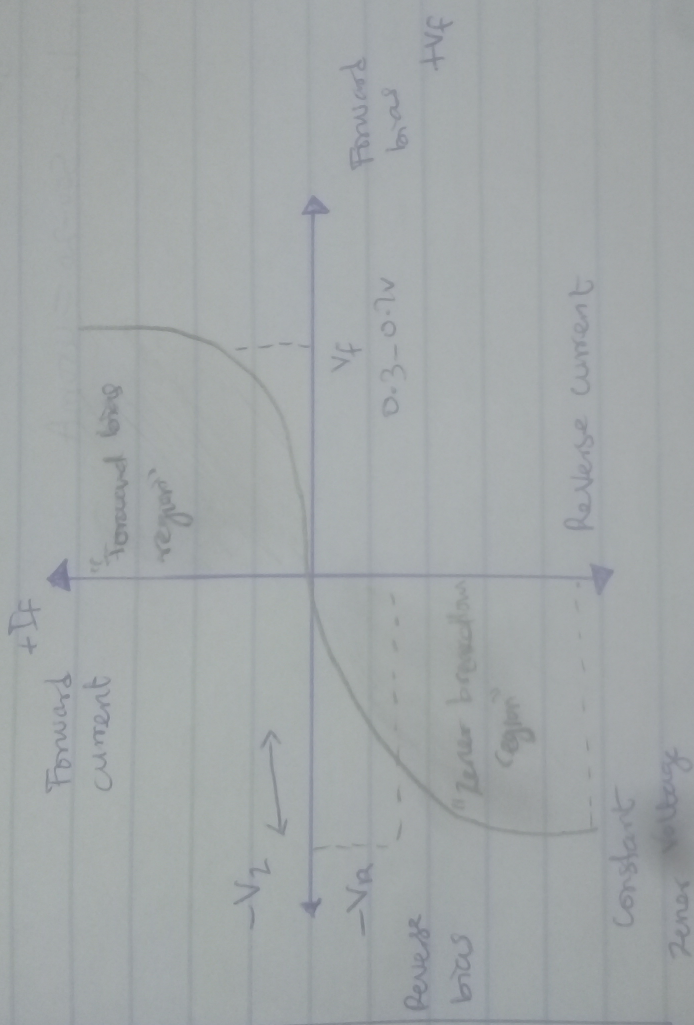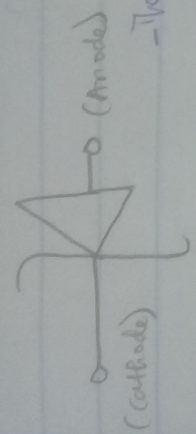

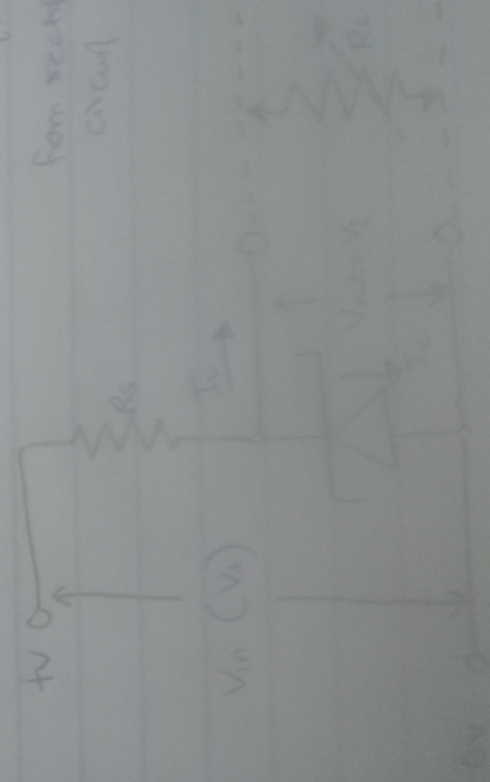D.C Input voltage
from rectifier or smoothing
circuit



2) Max Power = 5W

$$I_L = 500 \text{ mA} \leq 0.5 \text{ A}$$

$$V_S = 25 \text{ V max}$$

$$\text{Max current} = 5 \text{ W} = 0.5 \text{ A} \therefore I_2 = 0.5 \text{ A}, \text{ so } V_2 = 10$$

$$\text{Minimum resistance} = \frac{V_S - \sqrt{2} \cdot I_2}{I_2}$$

$$V_{DC} = 0.637 V_{\text{max}}$$

$$= 0.637 \times 20 = 12.74 \text{ V dc}$$

so

$$\text{Minimum resistance} = \frac{12.74 - 10}{0.5} = 5.48 \Omega$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{500} = 20 \text{ mA}$$

$$I_2 = I_S - I_L = 500 - 20 = 480 \text{ mA}$$