 




NAME: Ogunjimi Alleen Akinola
MATRIC NO: 18/EM604/060
DEPT: ELECT/ELECT


Assignment

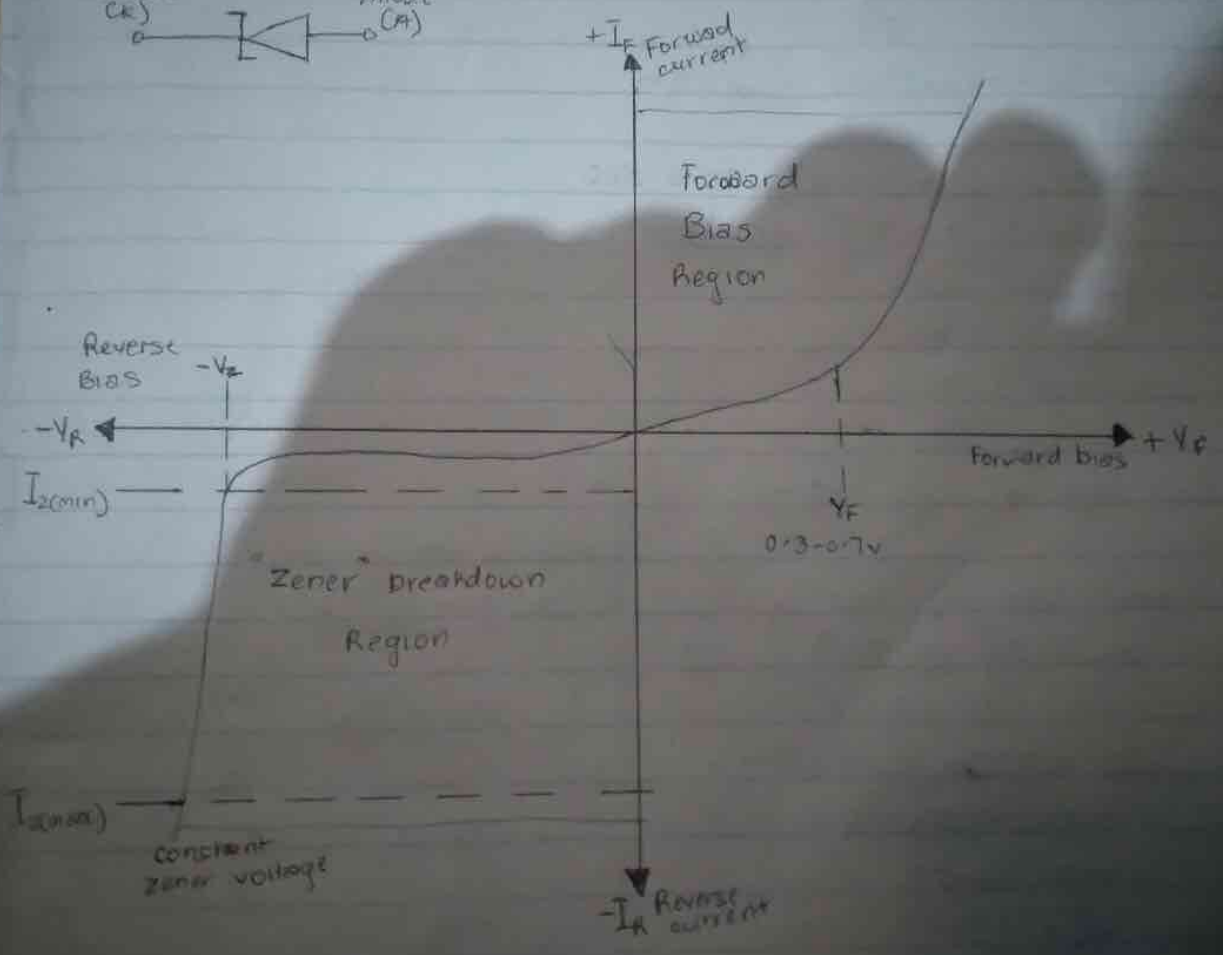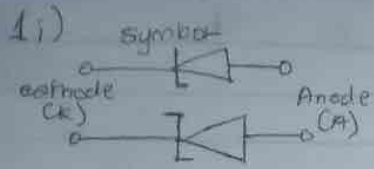1) A zener diode regulator can be used to great effect to regulate or stabilise a voltage ~~source~~ source against supply or load variations. The fact that the voltage across the diode in the breakdown region is almost ~~constant~~ constant turns out to be an important application of the zener diode as a voltage regulator.

The function of a regulator is to provide a constant output voltage to a load connected in parallel with it in spite of the ripples in the supply voltage or the variation in the load current and the zener diode will continue to regulate the voltage until the diode's current falls below the minimum $I_{Z(\min)}$ value in the reverse breakdown region.





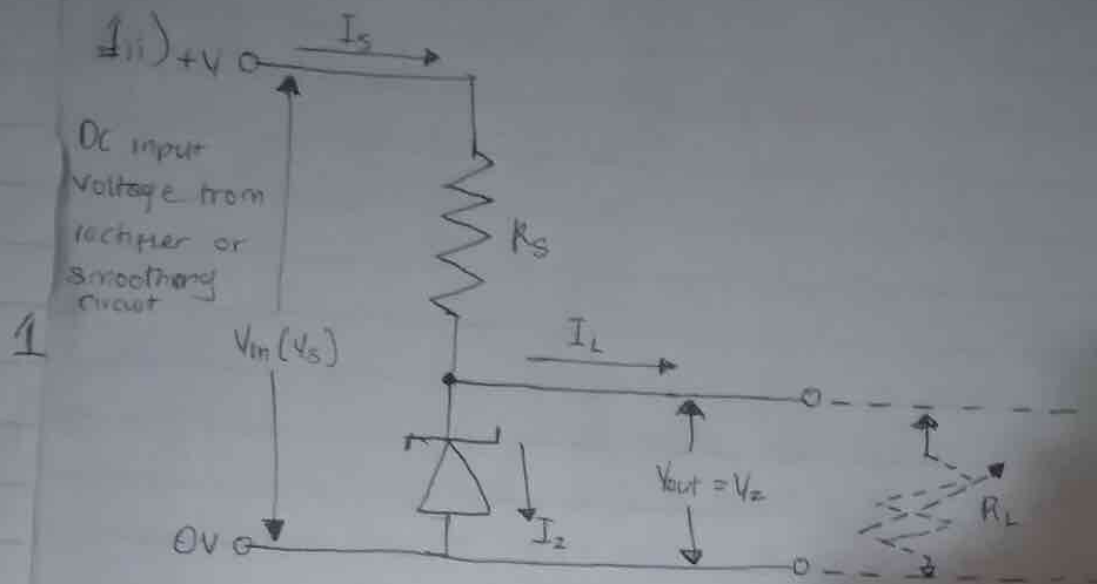

2) $I_z = 500 \text{ mA}$
 $P_z = 5 \text{ W}$, $V_s = 20 \text{ V}_{\text{max}}$

$0.001 \text{ watt/volt} = 1 \text{ mF}$
 $x = 500 \text{ mA}$
 $x = 0.5 \text{ watt/volt}$

~~$V_z = 0.5 \times 5 \text{ W}$~~ $V_z = \frac{0.5}{5 \text{ W}} = 0.1 \text{ V}$

i) $R_s = \frac{V_s - V_z}{I_z}$
 $= \frac{20 - 0.1}{500} = \frac{19.9}{500} = 0.04$
 $= 0.04 \times 1000 = 40 \Omega$

ii) $I_L = \frac{V_z}{R_L}$
 $I = \frac{0.1}{500} = 0.0002 \text{ A}$