


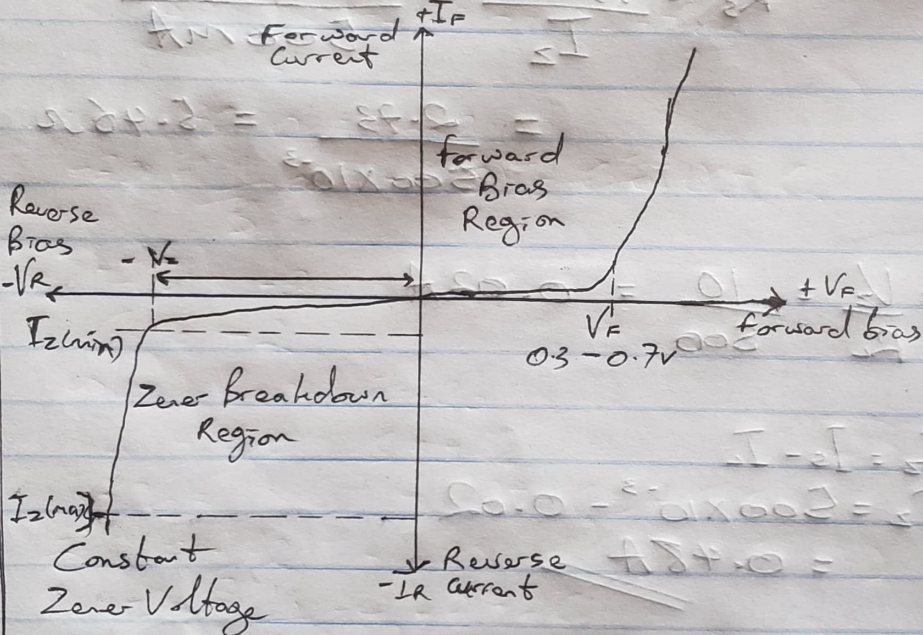
NAME :- AWE FARUQ OLADIMEJI

MATRIC :- 19/ENG 06/065


DEPARTMENT :- MECHANICAL ENGINEERING
ENG 222

D) Zener diode regulator is like a general-purpose signal diode ^{which} when biased in the forward direction behaves just like a normal signal diode, but when a reverse voltage is applied to it, the voltage remains constant for a wide range of currents.

b)  Zener diode symbol



I-V Characteristics Curve

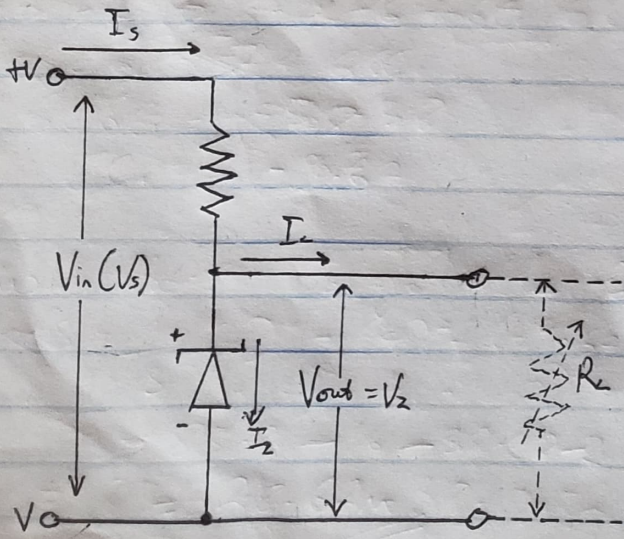

Circuit diagram

2

$$P_2 = 5 \text{ watts}$$

$$V_2 = 3.92 \text{ V}_s = 20 \text{ V}$$

$$R_s =$$

$$I_s = 500 \text{ mA}$$

$$\text{Voltage} = \frac{\text{Watt}}{\text{Current}} = \frac{5}{500 \times 10^{-3}} = 10 \text{ V}$$

$$V_{dc} = 2V_{max} = 2 \times 20 = 12.73$$

i

The minimum value of the series resistor to the Zener diode, $R_s = \frac{V_s - V_z}{I_z} = \frac{12.73 - 10}{500 \text{ mA}}$

$$= \frac{2.73}{500 \times 10^{-3}} = 5.46 \Omega$$

ii

$$I_L = \frac{V_z}{R_L} = \frac{10}{500} = 0.02 \text{ A}$$

$$I_z = I_s - I_L$$

$$I_z = 500 \times 10^{-3} - 0.02 = 0.48 \text{ A}$$

