

Azuka Dnyngye Anastasia

18/EWA02/1025


Computer Engineering

1) Zener diode.

This is a special property of diode that was invented by a man named Clarence Zener. The special property of this diode is that it can conduct in reverse bias. It can also conduct in forward bias just like a normal diode. The junction for the Zener diode will be heavily doped. Because of this reason, it can work as normally as a basic junction in the forward bias, and can tolerate the reverse current during reverse bias. The main purpose of it is to be used in stabilizers.


Zener diode is a diode in which the flow of current is from anode to cathode and cathode to anode defining that it has the capacity of conducting in both forward and reverse biases. It is used as voltage references and as a shunt regulator to regulate the voltage across a small circuit.

2) i) a) The symbol:

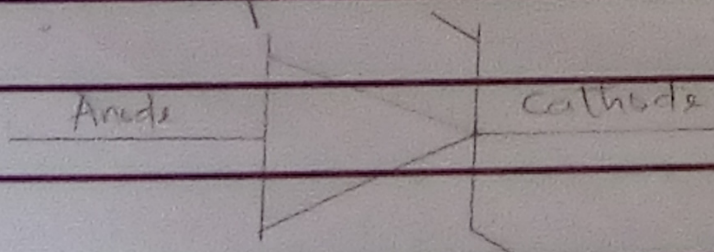


The Zener diode symbol.

b.

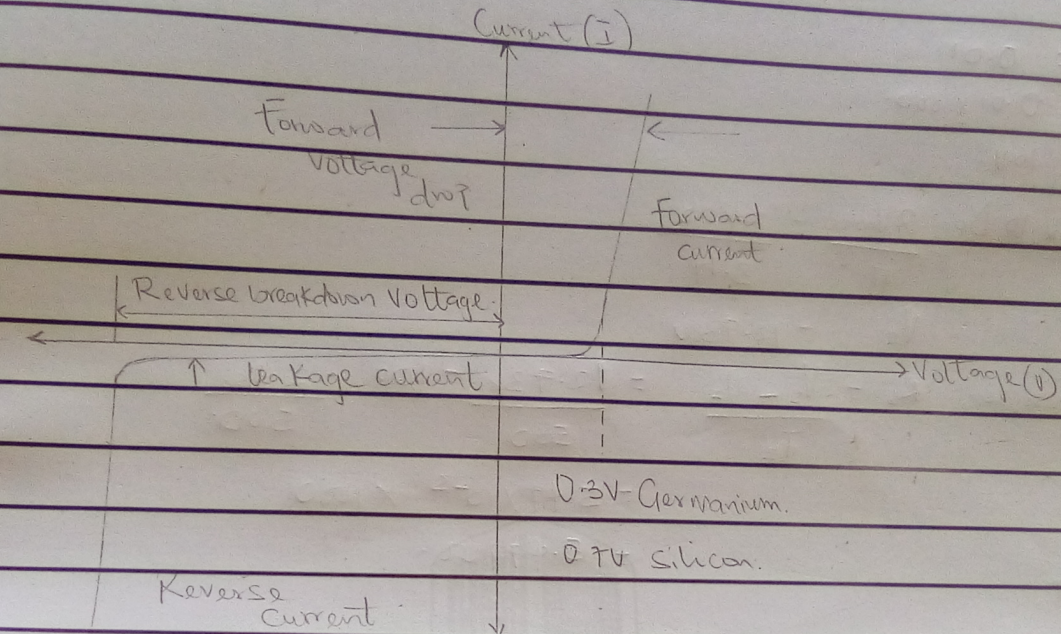


I-V Characteristic curve for a Zener diode

ii)

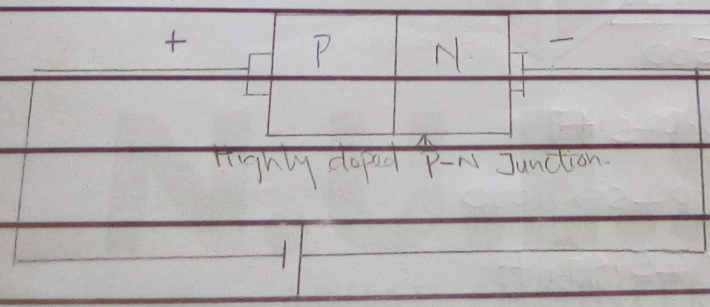

Zener diode circuit

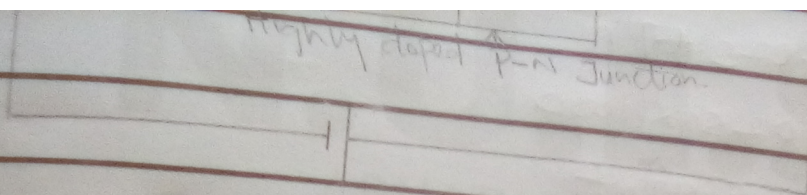

Zener diode circuit

2) Maximum power = 5W;

Maximum current $I_s = 500 \text{ mA}$.

$$V_{\text{max}} = 20 \text{ Vmax}$$

To find the maximum value of the series resistor, $R_s = \frac{V_s - V_z}{I_z}$

To get V_z ∴ Maximum current = $\frac{\text{watts}}{\text{Voltage } (V_z)}$

$$\text{Voltage } (V_z) = \frac{\text{watt}}{\text{max current}} = \frac{5 \text{ W}}{500 \text{ mA}}$$

$$= 0.01$$

$$= 0.01 \times 10000$$

$$= 100$$

$$V_{\max. \text{ to Dc}} = 2 V_{\max} = \frac{2 \times 20}{\pi} = \frac{2 \times 20}{3.14}$$

$$V_s = 12.738 \text{ V}$$

$$\text{Therefore, } R_s = \frac{V_s - V_z}{I_z} = \frac{12.738 \text{ V} - 10 \text{ V}}{500} = \frac{2.738}{500}$$

$$= 5.47 \times 10^{-3} \times 10000$$

$$= 5.477 \Omega$$

i) The current across the diode.

$$I = \frac{V_z}{R_L} = \frac{10}{500}$$

$$= 0.02 \text{ A}$$

$$= 0.02 \times 1000 = 20 \text{ mA}$$

At full load $\therefore 500 \text{ mA} - 20 \text{ mA}$

$$= 480 \text{ mA}$$