

NAME: ABIDTE FOLAWHO ABUL-AZEEM
 MAT No: 181ENG031002
 DEPARTMENT: CIVIL ENGINEERING
 COURSE: BASIC ELECT
 COURSE CODE: ENG1 222

2. The minimum value of the Series Resistor to the Zener diode;

Firstly: Max Power = 5W

$$I_Z = 500\text{mA} = 0.5\text{A}$$

$$V_S = 20\text{Vmax}$$

$$(i) \text{ Maximum current} = \frac{\text{Max Power}}{\text{Voltage}}$$

$$= \frac{5\text{W}}{0.5\text{A}} = 0.5\text{A}$$

$$\therefore V = 5\text{W}$$

$$\frac{0.5\text{A}}$$

$$\therefore V_Z = 10\text{V}$$

$$\therefore \text{The minimum resistance} = \frac{V_S - V_Z}{I_Z}$$

$$V_{dc} = 0.65\text{Vmax}$$

$$= 0.637 \times 20$$

$$= 12.74\text{Vdc}$$

$$\therefore \text{Minimum resistance} = \frac{20 - 12.74 - 10}{0.5} = 5.48\Omega$$

(ii) The Current Across the diode at full Load of 500Ω

$$\text{Load current } I_L = \frac{V_Z}{R_L} = \frac{10}{500}$$

$$= 0.02\text{A or } 20\text{mA}$$


$$I_Z = I_S - I_L$$

$$= 500 - 20$$

$$= 480\text{mA}$$

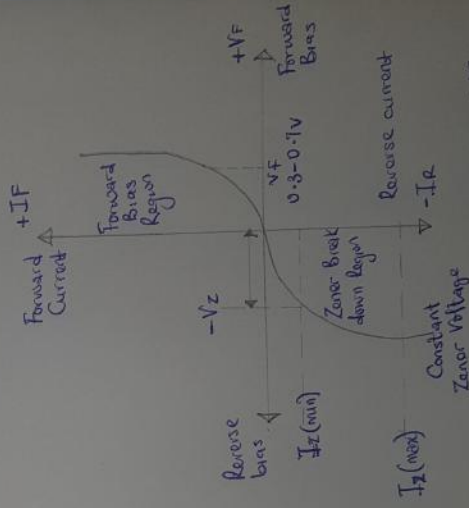- (i) Describe a Zener diode Regulator, and;
- (ii) Sketch the symbol and I-V characteristics;
- (iii) Sketch and Label the Circuit diagram


A Zener diode is always operated in its reverse biased condition. As such, a simple voltage regulator circuit can be designed using a Zener diode to maintain a constant DC output voltage across the Load in spite of variations in the input Voltage or Change in the Load current



I-V CHARACTERISTIC CURVE

(H)

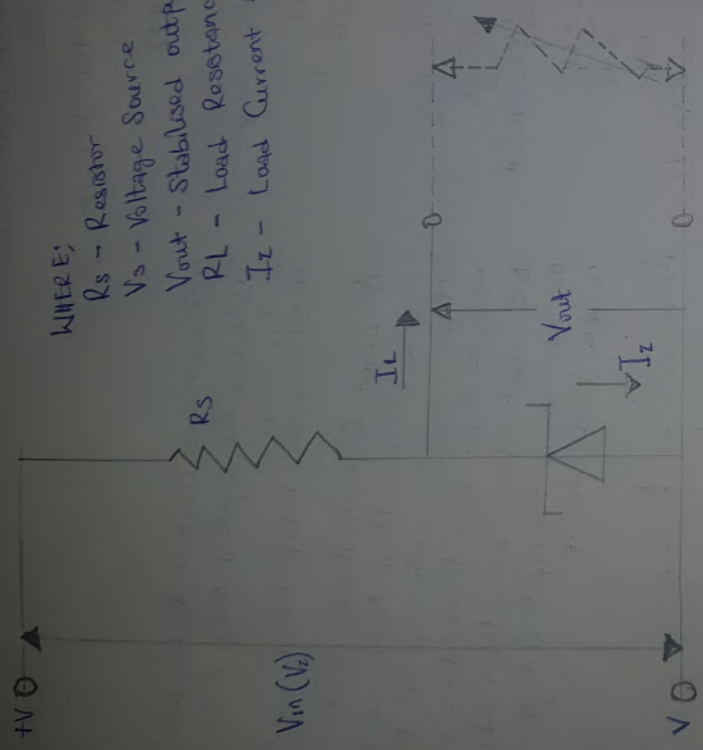WHERE:
 R_s - Resistor
 V_s - Voltage Source
 V_{out} - Stabilised output voltage
 R_L - Load Resistance
 I_z - Load Current Across Zener diode.



[Faint handwritten notes and diagrams are visible in the background of the page.]