



18/ENG05/030

Maren Emmanuel B.

Mechatronics


ENG222

Assignment


17 Zener Diode as voltage regulator. They are widely used as shunt voltage regulators to regulate voltage across small loads. Zener diodes have a sharp reverse breakdown voltage and breakdown voltage will be constant for a wide range of currents. Thus we will connect the zener diode parallel to the load such that the applied voltage will reverse bias it. Thus if the reverse bias voltage across the zener diode exceeds the knee voltage, the voltage across the load will be constant.

Symbol

i)

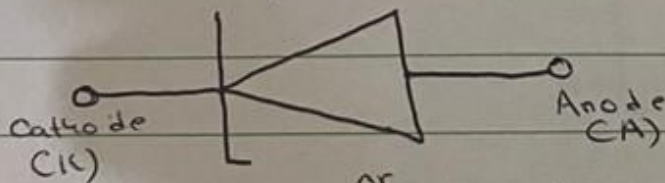

or

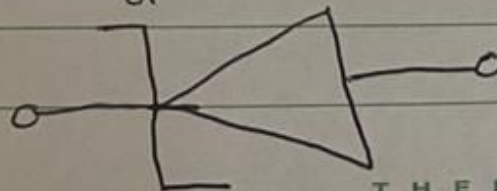



ENGINEERING
ASSEMBLY

THEME
Entrepreneurship and Manufacturing in Nigeria:
Challenges and Opportunities for a Better Future

7TH - 9TH AUGUST, 2017

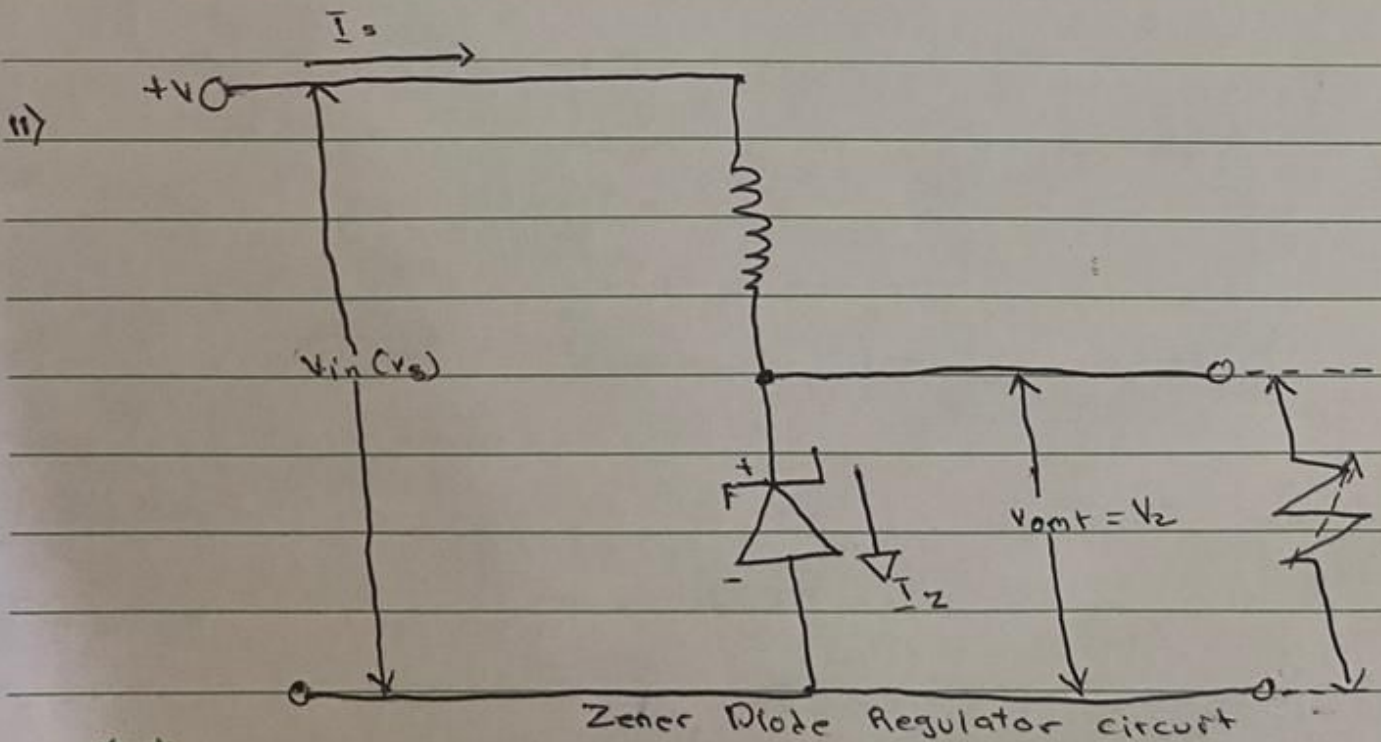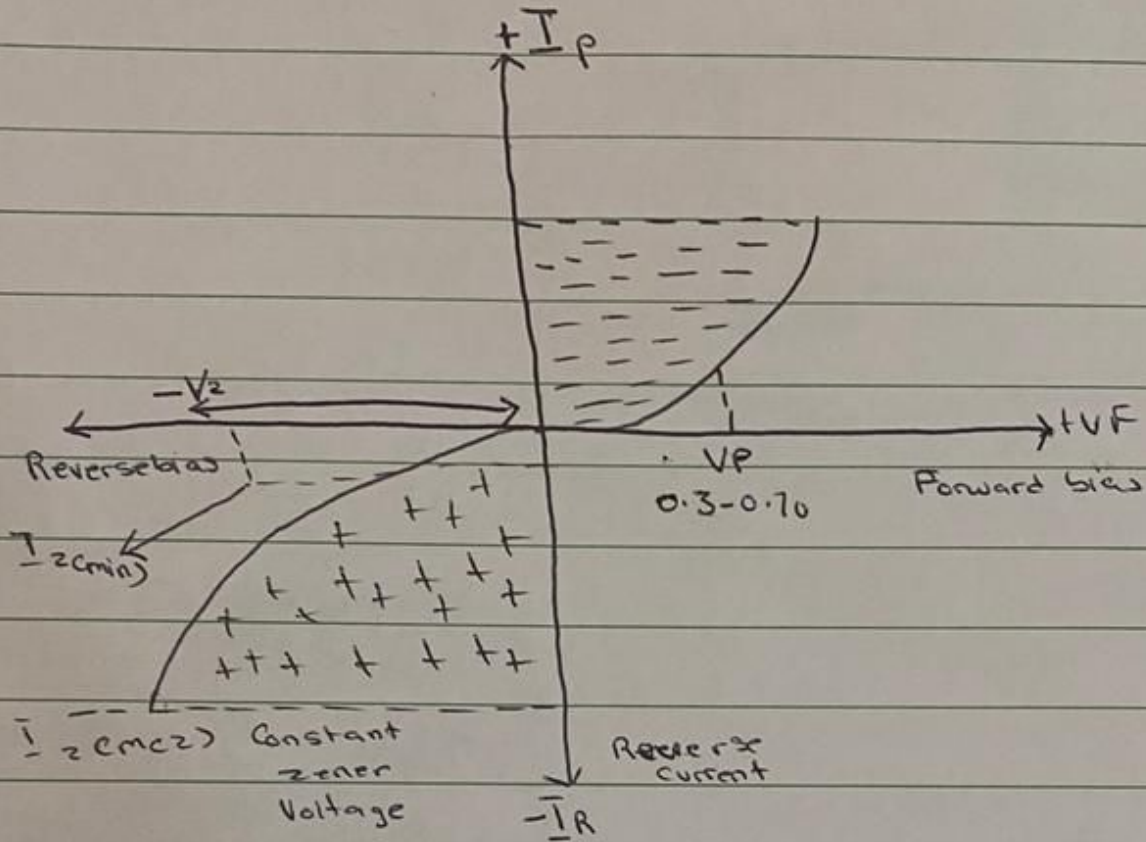VENUE: INTERNATIONAL CONFERENCE CENTRE (ICC), ABUJA
9:00AM DAILY







2) To determine the minimum value of the series resistor to the Zener diode

$$R_s = \frac{V_s - V_z}{I_z}$$

We need to determine V_z

$$\text{max current} = \frac{\text{watts}}{\text{Voltage}}$$

$$500 = \frac{5}{x}$$

$$x = 10 \text{ V}$$

$$V_s = 20 \text{ V}_{\text{max}} = 12.74 = 0.657 \times 20$$

$$R_s = \frac{12.74 - 10}{500} = 4 \Omega$$

$$I_L = \frac{V_z}{R_L} = \frac{10}{500} = 20 \text{ mA}$$

$$I_z = I_s - I_L = 500 \text{ mA} - 20 \text{ mA} = 480 \text{ mA}$$