

**NAME: SUNDAY WINNER CHIGOZIRIM**  
**COURSE: ENG 222 (BASIC ELECTRICAL ENGINEERING)**  
**DEPT: MECHATRONICS ENGINEERING**  
**MATRIC: 18/ENG05/057**

1.

NAME: SUNDNY WINNER CATHCOURM


COURSE:

MATRIC: 18/ENG05/057


DEPT: MECHATRONIC ENGINEERING

BASIC ELECTRICAL ENGINEERING ASSIGNMENT SOLUTION

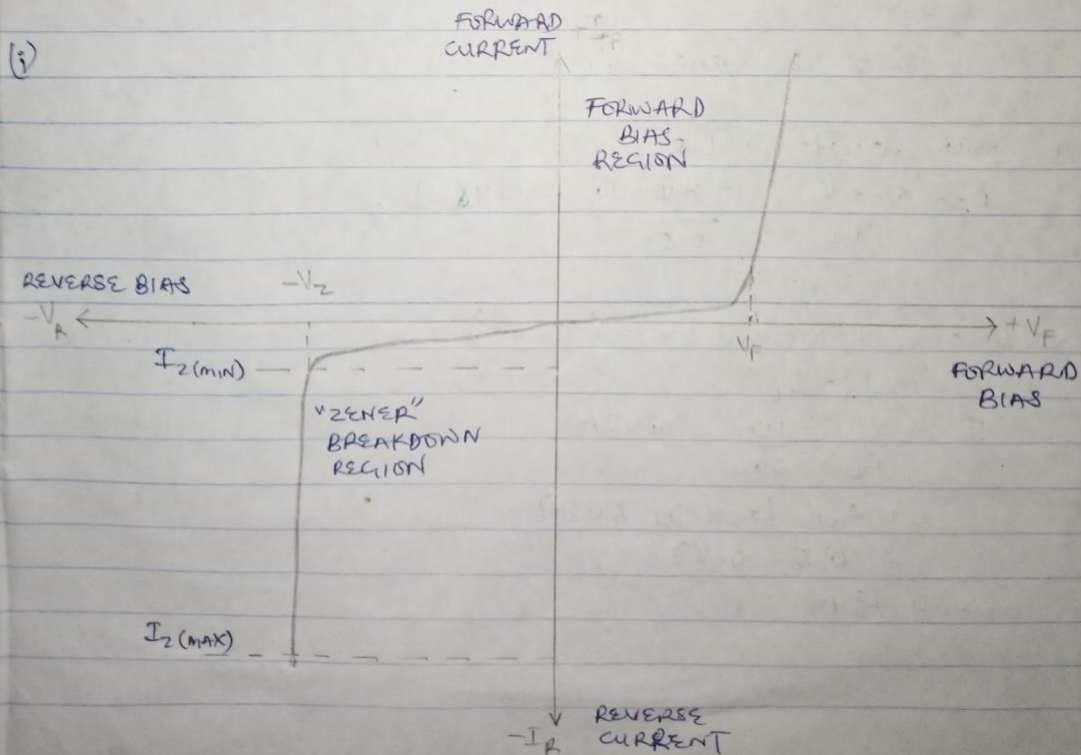(i) The zener diode is like a general purpose signal diode. When biased in the forward direction, it behaves just like a normal signal diode, but when a reverse voltage is applied to it, the voltage remains constant for a whole wide range of currents. The reverse voltage can increase until the diode breakdown voltage is achieved. This point is called the "avalanche region" or "breakdown region". At this point maximum current will flow through the zener diode. This point of breakdown is called the "zener voltage". At its reverse bias, the diode has a constant negative voltage regardless of the current flowing through the diode and remains ~~constant~~ nearly constant even with large changes in current as long as zener diode current remains nearly constant between the breakdown current and the maximum current.




(ii)

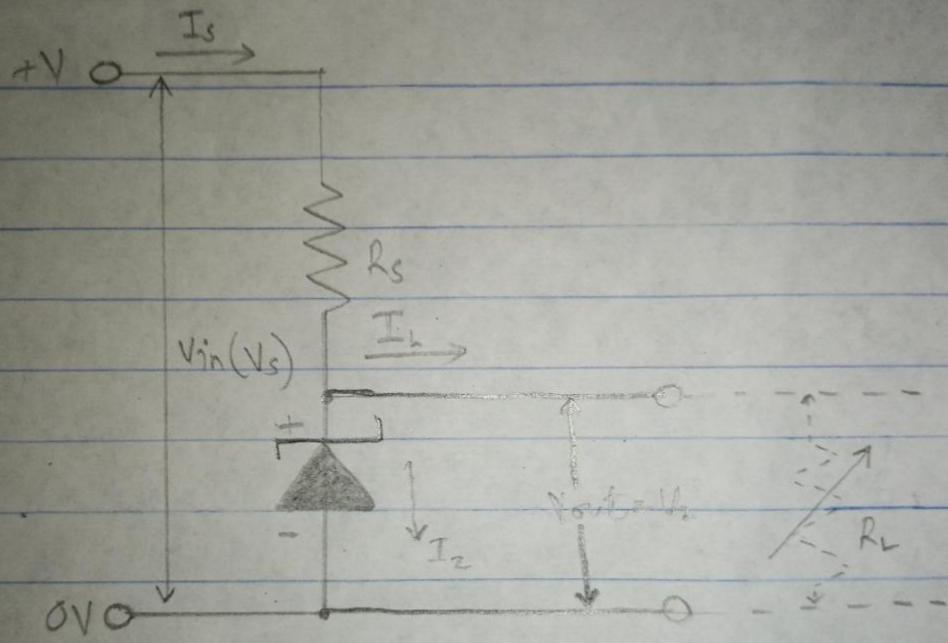

2.

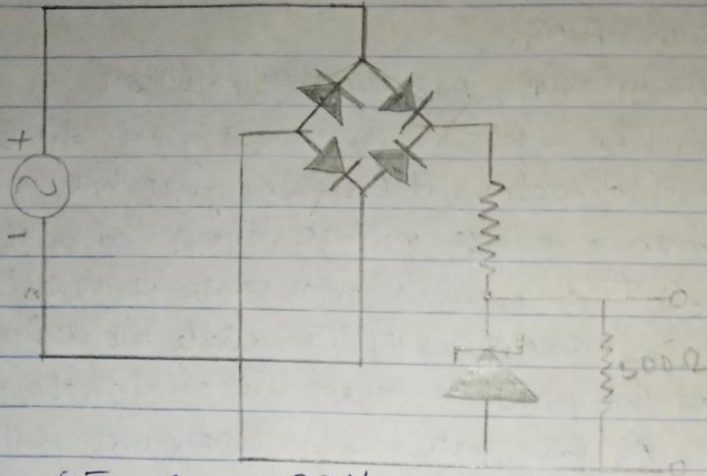(2) Power =  $SW = P_r$   
 $I_s = 500 \text{ mA} = 0.5 \text{ A}$



Since  $V_{\text{max}} = 20 \text{ V}$

$V_{\text{DC}} = 0.637 \times V_{\text{max}} = 0.637 \times 20 = 12.74 \text{ V} = V_s$

$\therefore 12.74 \text{ V}$  produced from A-C source.

(a) Power = current  $\times$  Voltage

$SW = 0.5 \text{ A} \times V_2$

$V_2 = \frac{5}{0.5} = 10 \text{ V}$

$\therefore 10 \text{ V}$  is across the Zener diode

Minimum resistor value:

$R_s = \frac{V_s - V_2}{I_2} = \frac{12.74 - 10}{0.5} = 5.48 \Omega //$

(b) Zener current at full load ( $500 \Omega$ )

$I_2 = I_s - I_L$

$I_L = \frac{V_2}{R_L} = \frac{10}{500} = 0.02 \text{ A}$

$I_2$  at full load of  $500 \Omega$ ;  
 $= 0.5 - 0.02$

$\Rightarrow 0.48 \text{ A} //$