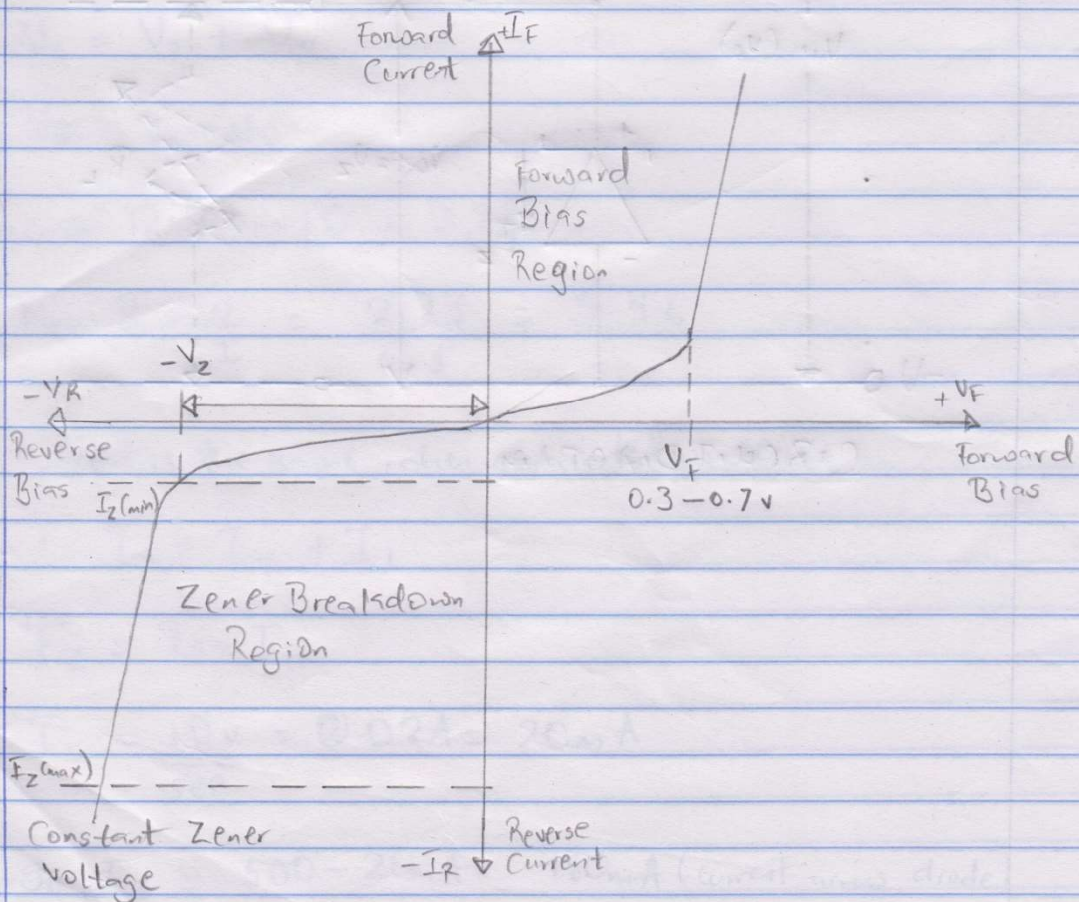


CHIOKE VICTOR U.P.
18/ENG02/031
COMPUTER ENGINEERING
ENG 222 ASSIGNMENT
BASIC ELECTRICAL ENGINEERING

1. Zener diode

The zener diode (Breakdown Diode) are basically the same as a standard PN junction diode but specially designed to have a low pre-determined Reverse Breakdown voltage that takes advantage of this high reverse voltage. It is also a simple type of voltage regulator which ~~also conducts~~ is like a general-purpose signal diode consisting of a silicon PN junction.



ZENER DIODE I-V CHARACTERISTICS

2 Given the parameters

$$P_z = 5W$$

$$I_z = 500mA$$

$$V_{max} = 20V$$

V_{max} to V_{dc}

$$V_{dc} = \frac{2V_{max}}{\pi} = \frac{2 \times 20}{\pi} = 12.73V_{dc}$$

Since $P = IV$

$$V_z = \frac{P}{I} = \frac{5}{500 \times 10^{-3}} = 10V$$

$$V_s = V_z + V_R$$

$$V_R = V_s - V_z$$

$$= 12.73 - 10 = 2.73V$$

$$\text{Now } R = \frac{V}{I} = \frac{2.73}{0.5} = 5.46$$


Current is the same when connected in series

$$\therefore I_s = I_z + I_L$$


$$I_z = I_s - I_L$$

$$I_L = \frac{10V}{500} = 0.02A = 20mA$$
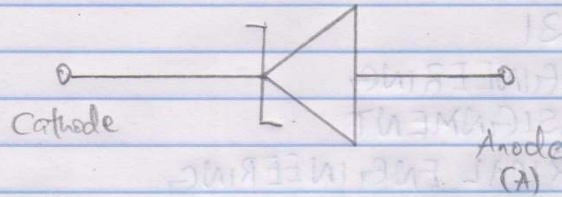
$$\text{So } I_z = 500 - 20mA = 480mA \text{ (current across diode)}$$



SYMBOL FOR ZENER DIODE

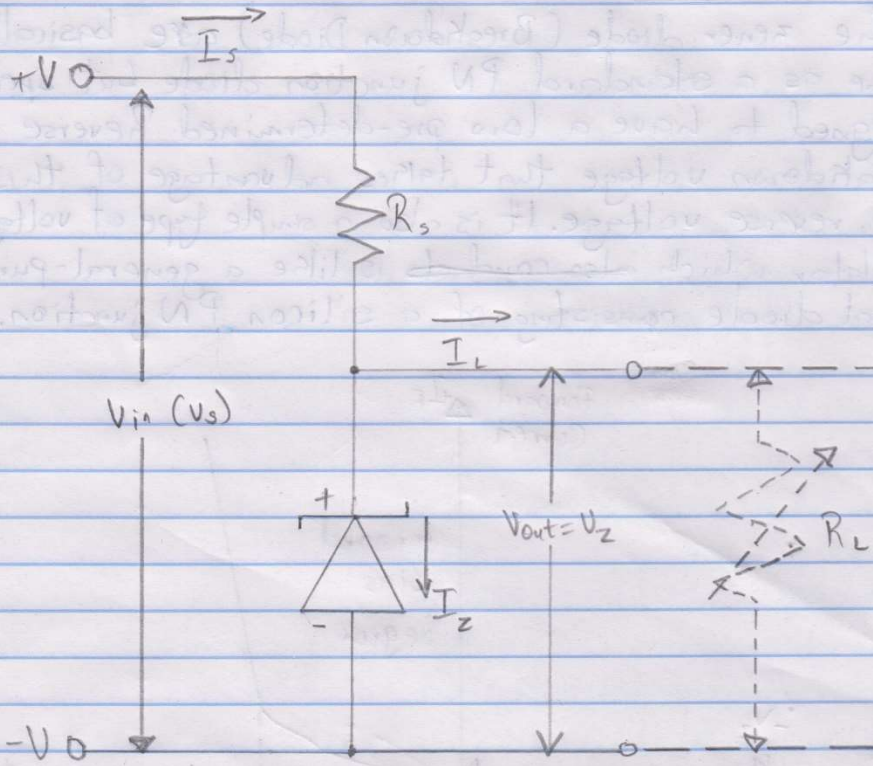

CIRCUIT DIAGRAM