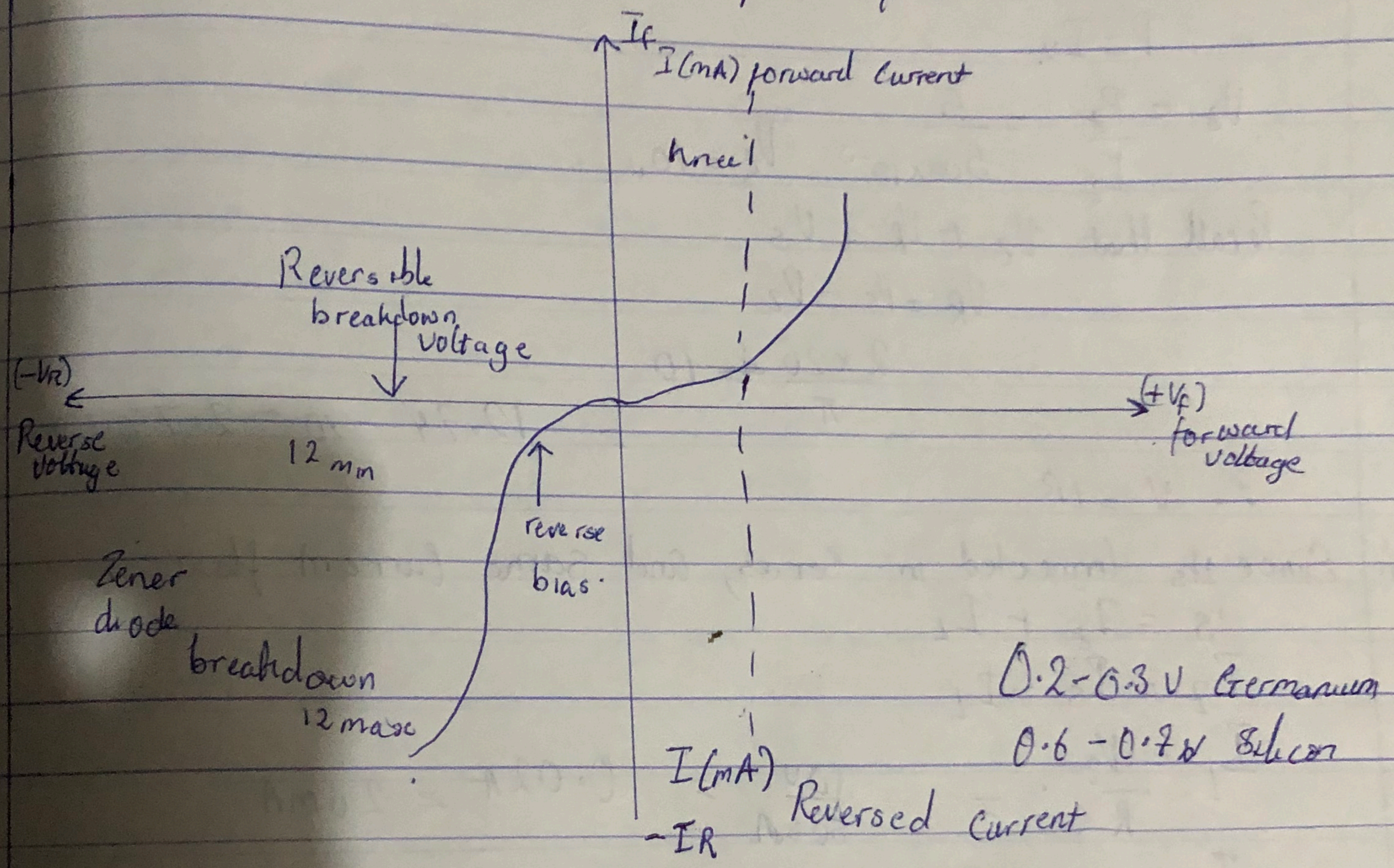


Name: Uba Chukama Raphael
 Matric NO: 18/ENGR06/066
 Course Code: ENG 222
 Mechanical Engineering


Assignment

i. A Zener diode is a type of diode that allows current to flow in the conventional manner - from its anode to its cathode. i.e. when the anode is positive with respect to the cathode.



I-V Characteristic Curve

ii. Zener diode regulator circuit

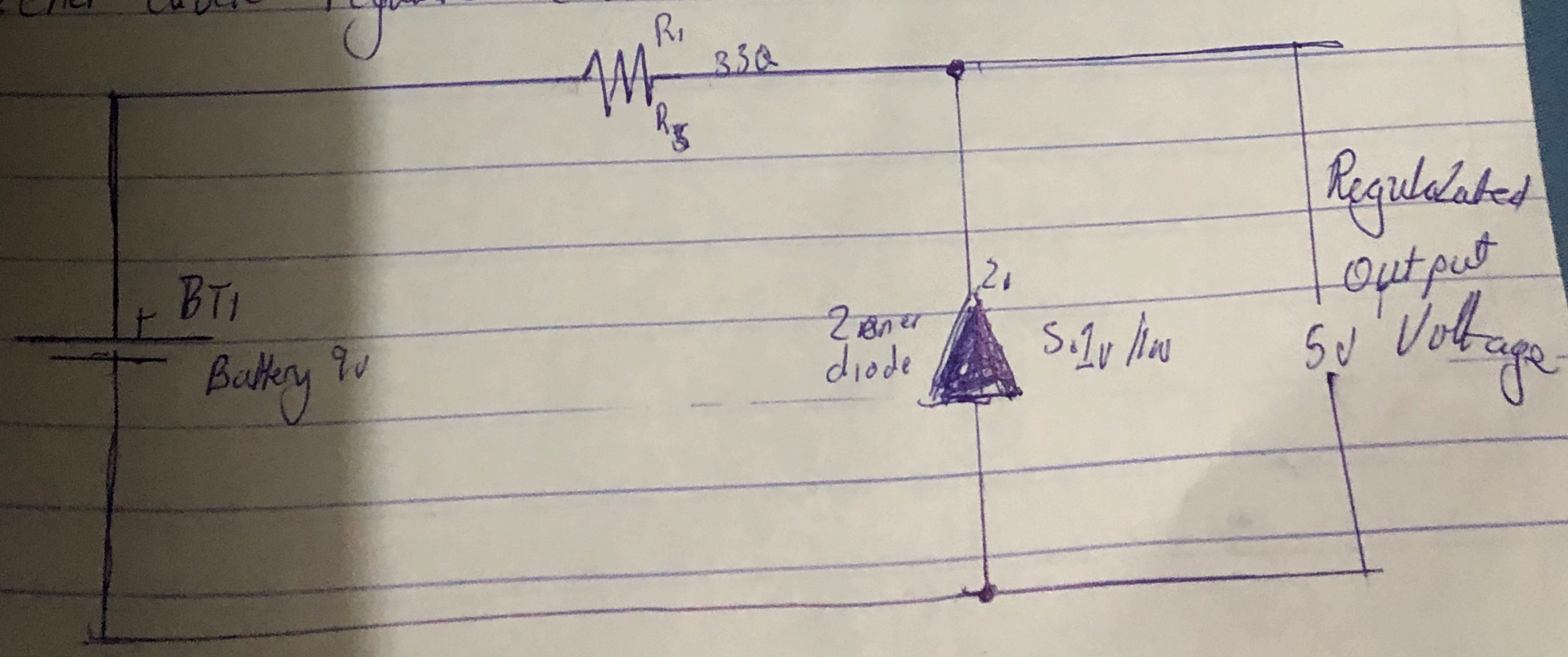

Solution

2i A ~~5w~~ maximum ~~width~~ = 5w = I_z

$$\text{Current} = 500 \text{ mA } I_z$$

$$20 \text{ V}_{\text{max}}$$

To convert + V_{max} to V_{DC} ,

$$V_{\text{DC}} = \frac{2 V_{\text{max}}}{\pi}$$

π

$$V_s = \frac{2 \times 20}{\pi} = 12.74 \text{ V}_{\text{DC}}$$

π

$$P = I V$$

$$\therefore V_z = \frac{P_z}{I_z} = \frac{5}{500 \times 10^{-3}} \quad V_z = 10 \text{ V}$$

Recall that $V_z + V_R = V_s$

$$V_R = V_s - V_z$$

$$\frac{2 \times 20}{\pi} = 10$$

π

$$= 12.74 - 10 = 2.74 \text{ V}$$

$$\therefore V = IR$$

ii Since I_s connected in series, and same current flow

$$I_s = I_z + I_L$$

$$I_z = I_s - I_L$$

$$I_L = \frac{V_z}{R} = \frac{10 \text{ V}}{500 \Omega} = 0.02 \text{ A} = 20 \text{ mA}$$

$$I_z = 500 \text{ mA} - 20 \text{ mA}$$

$$= 480 \text{ mA} = \underline{0.48 \text{ A}}$$