

AYUNU OGHEMARI

18/ENG06/015

MECHANICAL ENGINEERING

ENG 222

1) Describe a Zener diode

A Zener diode voltage regulator consists of a current limiting resistor R_L connected in series with the input voltage V_{in} with the Zener diode Z_1 in the reverse-biased condition.


The function of the regulator is to provide a constant output voltage to a load connected in parallel with it in spite of the changes in the supply voltage ~~and~~ the load current and the Zener diode will continue to regulate the voltage until the diode current falls below the minimum $I_{Z(min)}$ values to reverse-bias region.

There are two types of the regulator these are


1) Regulation

2) Load Regulation

I-V Characteristics Curve.

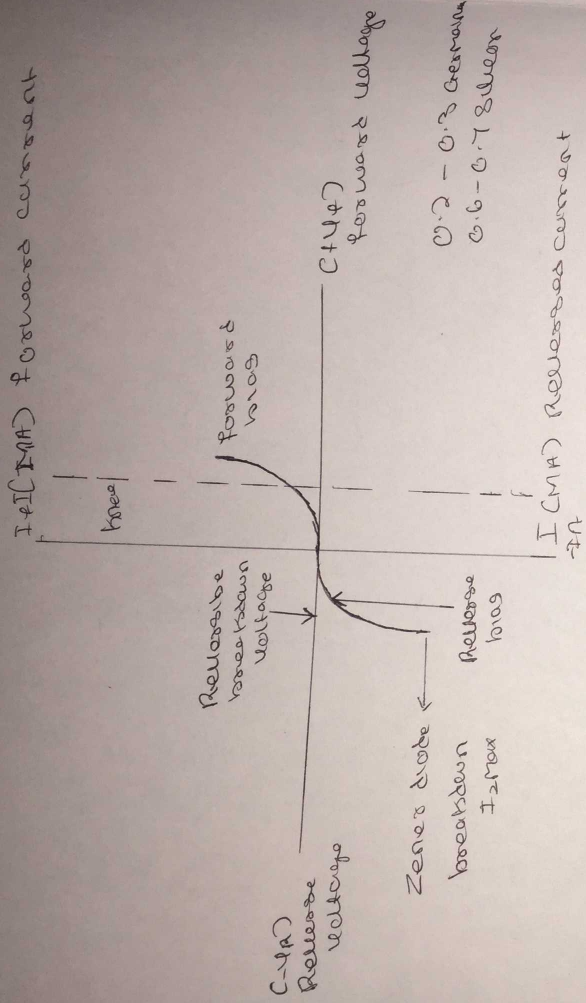

(iii) Zener diode regulator circuit

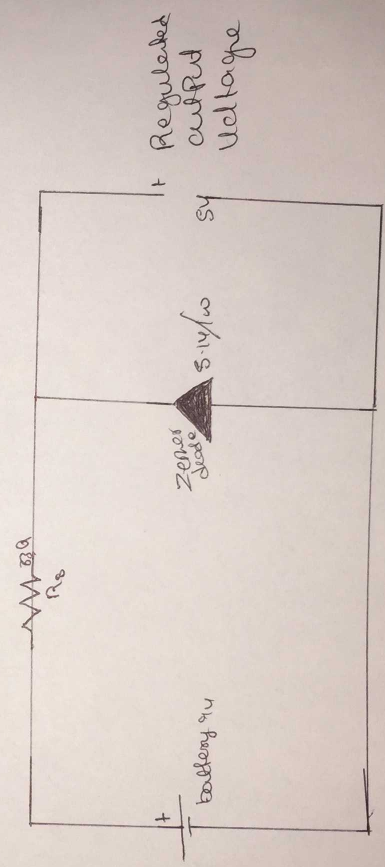

ii) Since it's connected in series with same current flow

$$I_s = I_z + I_L$$

$$I_z = I_s - I_L$$

$$I_z = \frac{V_z}{R}$$

$$= \frac{10V}{500\Omega}$$

$$= 0.02A$$

$$= 20mA$$

$$I_z = 500mA - 20mA$$

$$= 480mA$$

$$= 0.48A$$

2) A SW maximum rated Zener diode has 500mA maximum current flowing through it. If a 20V max voltage source is connected as input to the regulator circuit.

Solution

1) The minimum value of the series resistor to the zener diode

$$S_w = P_z$$

$$\text{Current} = 500 \text{mA} = I_z$$

$R_{z\text{max}}$

V_{dc} to V_{dc1}

$$V_{dc} = \frac{2V_{z\text{max}}}{K}$$

$$V_s = \frac{2 \times 20}{K} = 12.74 \text{V}$$

$$P = I V$$

$$\therefore V_z = P_z = \frac{5}{500 \times 10^{-3}}$$

$$V_z = 10 \text{V}$$

Recalling $V_z + V_R = V_s$

$$V_R = V_s - V_z$$

$$\frac{2 \times 20}{K} - 10$$

$$= 12.74 - 10$$

$$= 2.74 \text{V}$$

$$\therefore V = IR$$

$$R = \frac{V}{I} = \frac{2.74}{500 \times 10^{-3}}$$

$$R = 5.48 \Omega$$