

OYEBADE RAPHAEL FEM 18/EN904/069 ELECT/ELECT

$$P_z = 5W$$

$$I_z = 500mA$$

$$20V_{max}$$

To convert V_{max} ~~to V_{dc}~~ , to V_{dc}

$$V_{dc} = \frac{2V_{max}}{\pi}$$

$$V_s = \frac{2 \times 20}{\pi} = 12.73V_{dc}$$

Recall that $P = IV$

$$\therefore V_z = \frac{P_z}{I_z} = \frac{5}{500 \times 10^{-3}}$$

$$\cancel{V_z} \quad V_z = 10V$$

Recall that $V_z + V_R = V_s$

$$V_R = V_s - V_z$$

$$\frac{2 \times 20}{\pi} - 10$$

$$= 12.73 - 10$$

$$= 2.73V$$

$$\therefore V = IR$$

$$R = \frac{V}{I} = \frac{2.73}{500 \times 10^{-3}}$$

$$R = 5.46$$

Since its connected in series, and same current flows

$$I_s = I_z + I_L$$

$$I_z = I_s - I_L$$

$$I_L = \frac{V_z}{R}$$

$$= \frac{10V}{500\Omega} = 0.02A = 20mA$$

$$I_z = 500mA - 20mA$$

$$= 480mA = 0.48A //$$

OFERADE RAPHEL OLUNWEMI 15FENG041069

① Zener diode voltage regulator can be used to produce a stabilised voltage output with low ripple under varying load current conditions. By passing a small current through the diode from a voltage source via a suitable current limiting resistor (R_L), the Zener diode will conduct sufficient current to maintain a voltage drop of V_{out} . The DC output voltage from the half or full-wave rectifiers contains ripple superimposed onto the DC voltage and that as the load value changes so does the average output voltage. By connecting a simple zener stabiliser circuit as shown below across the output of the rectifier, a more stable output voltage can be produced.

