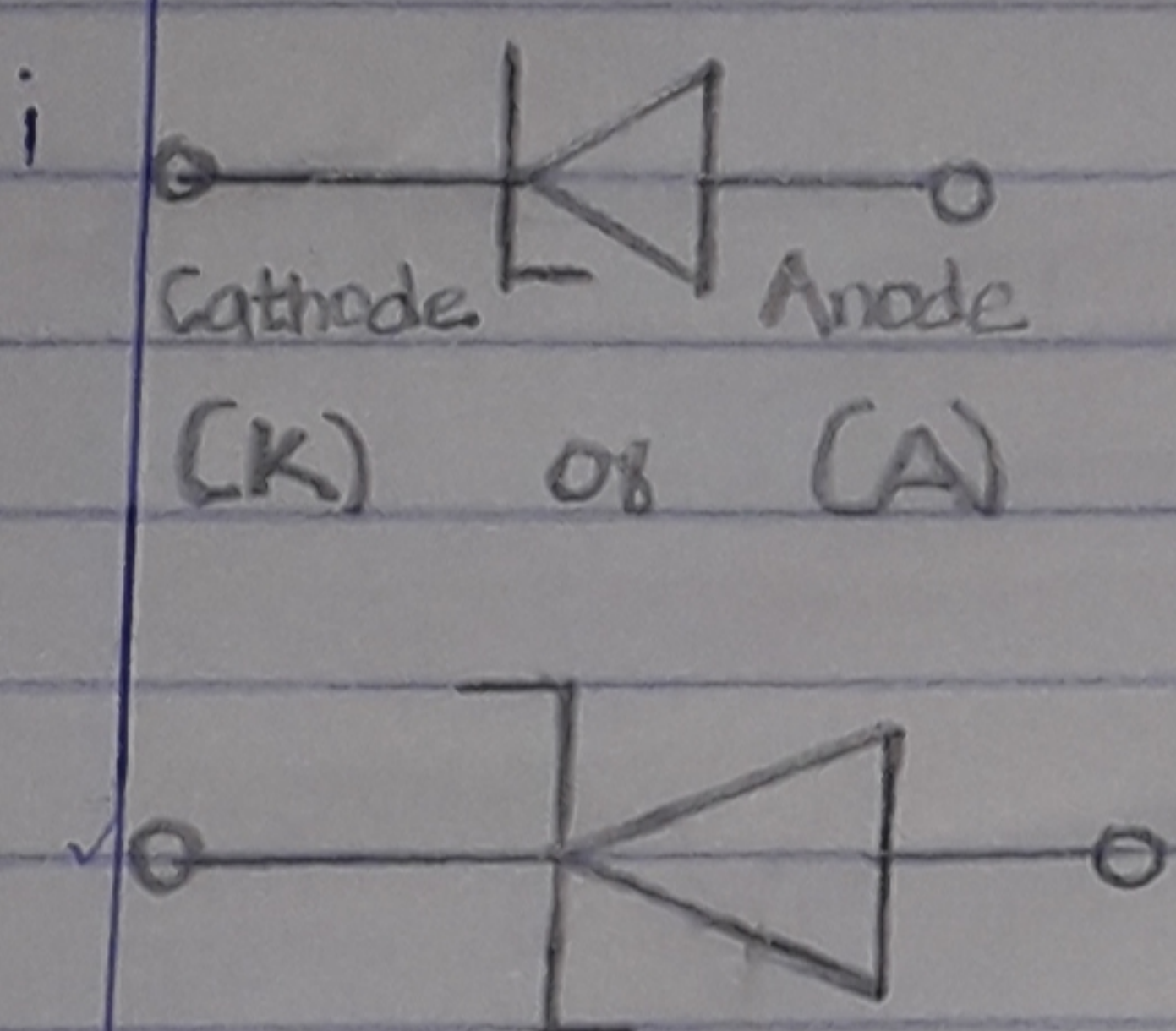


Name: Icheqoo Favours Esuchi
 Dept: Computer Engineering
 Matric No: 181ENG021042
 Course: ENG 222 (Basic Elect)


Assignment


1. The Zener diode behaves just like a normal general purpose diode consisting of a Silicon PN junction and when biased in the forward direction, that is Anode positive with respect to its cathode, it behaves just like a normal signal diode passing the rated current. The Zener diode is used in its "reverse bias" or reverse breakdown mode, i.e the diodes anode connects to the negative supply.

Symbol



I-V Characteristics Curve

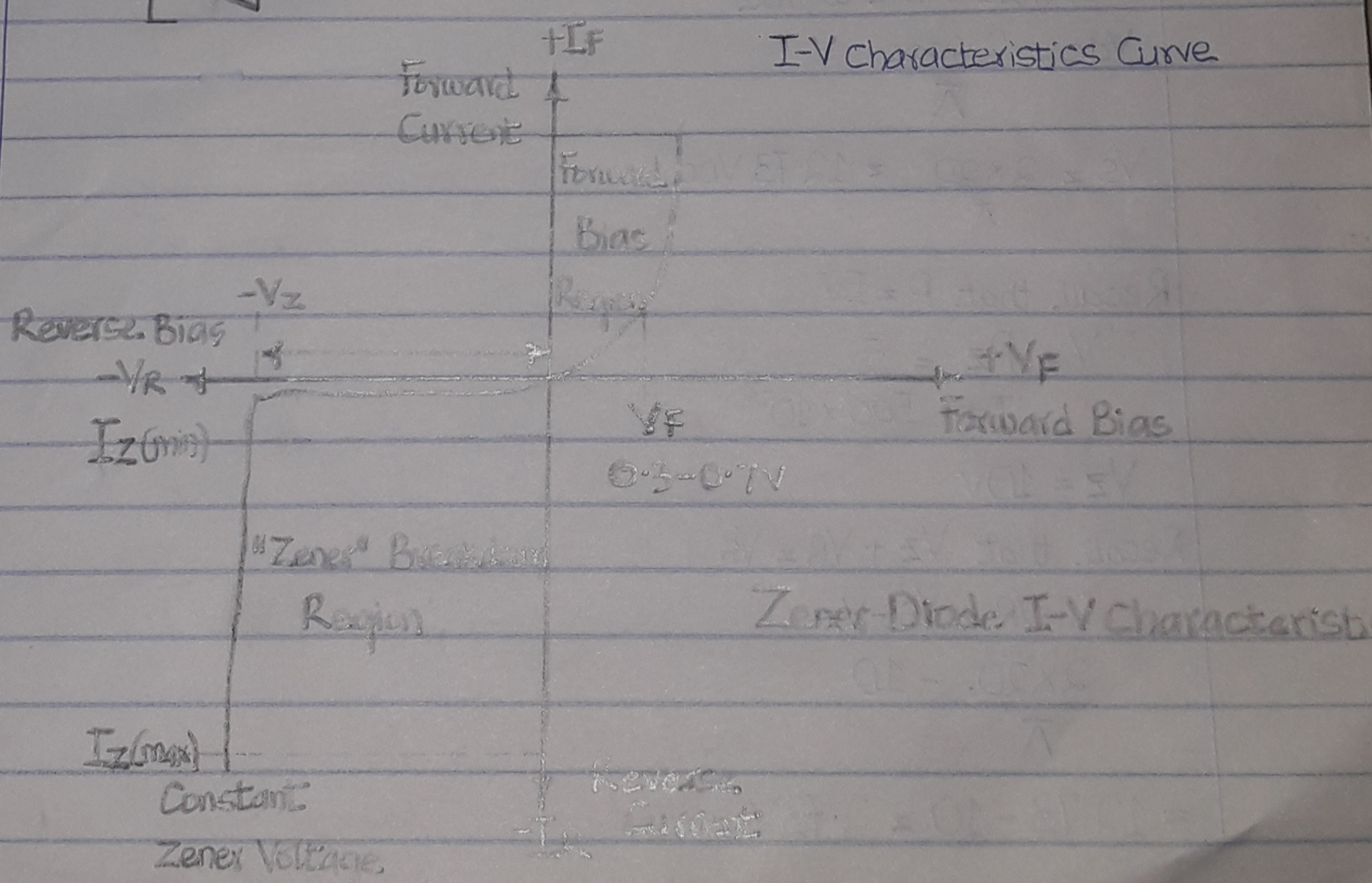

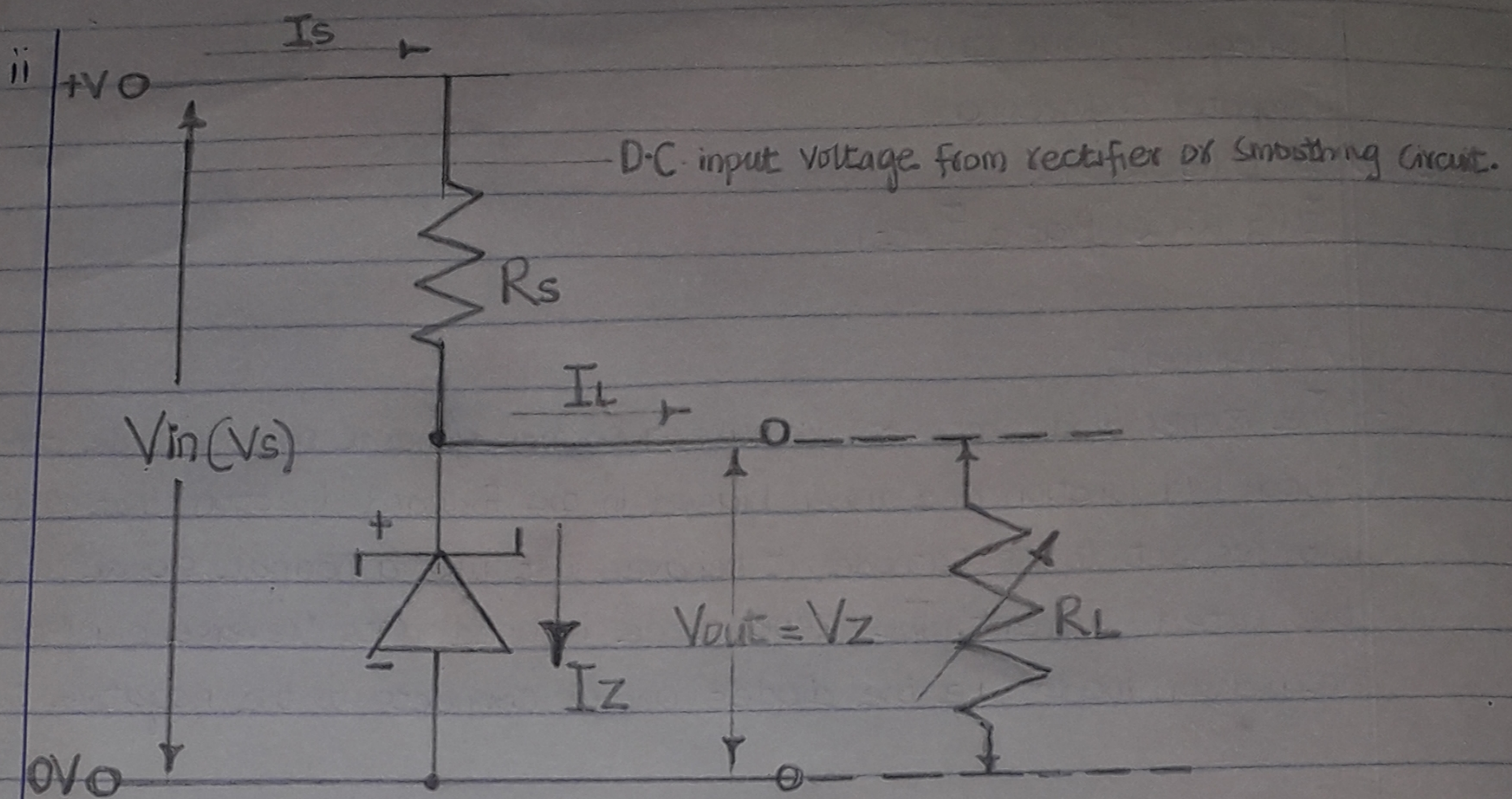

Circuit diagram

2) $P_Z = 5W$

$I_Z = 500mA$

$20V_{max}$

To convert V_{max} to VDC

$$V_{dc} = \frac{2V_{max}}{\pi}$$

$$V_s = \frac{2 \times 20}{\pi} = 12.73 \text{ VDC}$$

Recall that $P = IV$

$$\therefore V = \frac{P_Z}{I_Z} = \frac{5}{500 \times 10^{-3}}$$

$$V_Z = 10V$$

Recall that $V_Z + V_R = V_s$

$$\therefore V_R = V_s - V_Z$$

$$\frac{2 \times 20}{\pi} - 10$$

$$= 12.73 - 10 = 2.73V$$

$$V = IR$$

$$R = \frac{V}{I} = \frac{2.73}{500 \times 10^{-3}}$$

$$R = 5.46 \Omega$$

Since it's connected in series, and same current flows

$$I_s = I_z + I_L$$

$$I_z = I_s - I_L$$

$$I_L = \frac{V_z}{R}$$

$$= \frac{10V}{500\Omega} = 0.02A = 20mA$$

$$I_z = 500mA - 20mA$$

$$= 480mA = 0.48A$$