
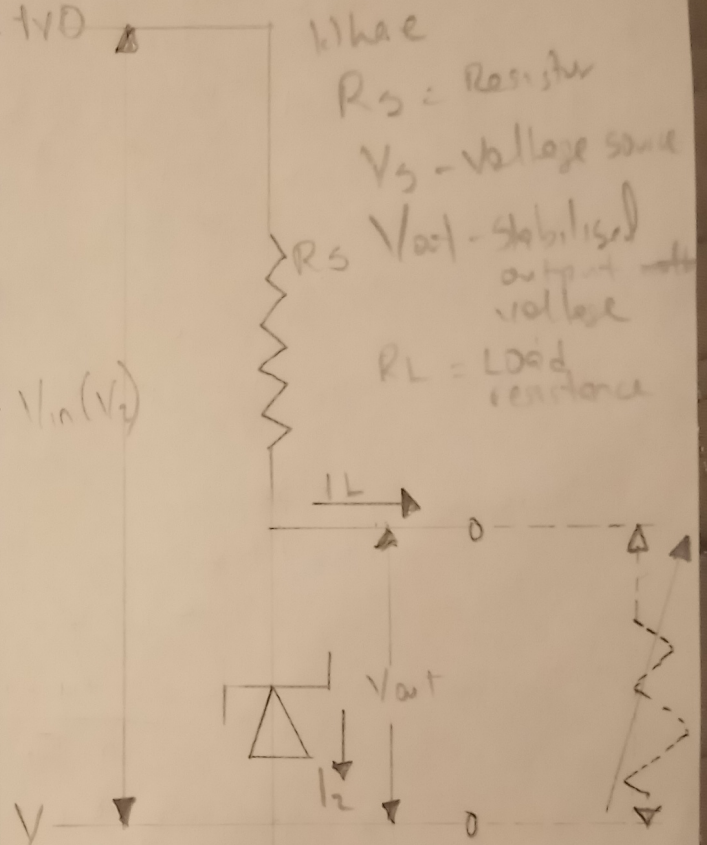


- ABUJLE AFOLABI ABDULRAHMAN
 - 18/ENG06/002
 - MECHANICAL ENGINEERING
 - BASIC ELECT
 - ENG 222

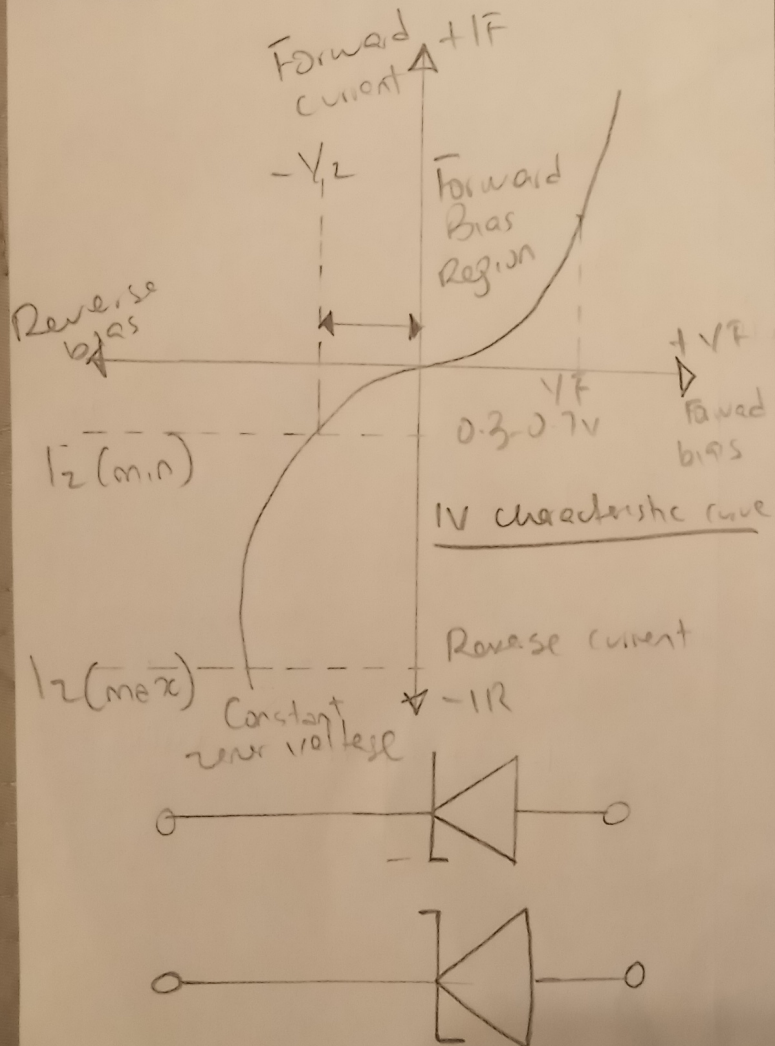- 1) Describe a Zener diode Regulator, and
 (i) Sketch the symbol and I-V characteristics curve,
 (ii) Sketch and label the circuit diagram

A Zener diode is always operated in its reverse biased condition. As such a simple voltage regulator circuit can be designed using a Zener diode to maintain a constant DC output voltage across the load in spite of variations in the input voltage or changes in the load current.



I_Z - Load Current across zener diode

2) The minimum value of the series Resistor to the Zener diode;

Firstly - Max Power = 5W
 $I_Z = 500 \text{ mA} = 0.5 \text{ A}$
 $V_s = 20 \text{ V}_{\text{max}}$

(i) Maximum current = $\frac{\text{Max Power}}{\text{Voltage}}$

$$= \frac{5 \text{ W}}{V} = 0.5 \text{ A}$$

$$\therefore V = \frac{5 \text{ W}}{0.5 \text{ A}}$$

$$\therefore V_Z = 10 \text{ V}$$

\therefore The minimum resistance = $\frac{V_s - V_Z}{I_Z}$

$$\begin{aligned} V_{dc} &= 0.637 V_{\text{max}} \\ &= 0.637 \times 20 \\ &= 12.74 \text{ V}_{dc} \end{aligned}$$

$$\begin{aligned} \therefore \text{Minimum Resistance} &= \frac{12.74 - 10}{0.5} \\ &= 5.48 \Omega \end{aligned}$$

(ii) The current across the diode at full load of 500Ω

$$\begin{aligned} \text{Load current } I_L &= \frac{V_Z}{R_L} = \frac{10}{500} \\ &= 0.02 \text{ A or } 20 \text{ mA} \end{aligned}$$

$$\begin{aligned} I_Z &= I_s - I_L \\ &= 500 - 20 \\ &= 480 \text{ mA} \end{aligned}$$