

Bassam Jay Anishe  
18/11/2004

Chemical Engineering  
Basic Elect.

2 →  $P_z = 5W$

$I_z = 500mA$

Then conv.  $V_{max}$  to VDC

20V max

$\therefore V_{dc} = \frac{P_{max}}{I}$

$V_s = \frac{2 \times 20}{1} = 12.73VDC$

Recall that  $P = IV$

$\therefore V_z = \frac{P_z}{I_z} = \frac{5}{500 \times 10^{-3}}$

Recall that  $V_z + V_R = V_s$

$\therefore V_R = V_s - V_z$

$\therefore \frac{2 \times 20}{1} - 10 = 12.73 - 10 = 2.73V$

$\therefore V = IR \quad \therefore R = \frac{V}{I} = \frac{2.73}{500 \times 10^{-3}}$

$\therefore R = 5.46$

The connection is in series so  $I_s = I_z + I_L$

$I_z = I_s - I_L$

$I_L = \frac{V_L}{R} = \frac{10V}{500\Omega} = 0.02A$



$I_z = 500mA - 20mA = 480mA = 0.48A$

$\therefore 480mA = 0.48A$


1 → Describe a Zener diode regulator circuit.

A Zener diode is always operated in its reverse biased condition. As such a simple voltage regulator circuit can be designed using a Zener diode to maintain a constant DC output voltage across the load in spite of

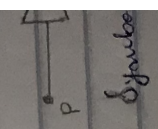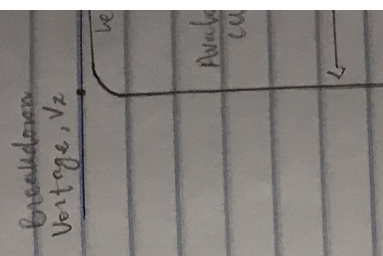variations in the load current. i → Sketch the symbol





Sketch and

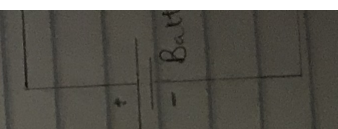

Variations in the input voltage or changes in the load current.

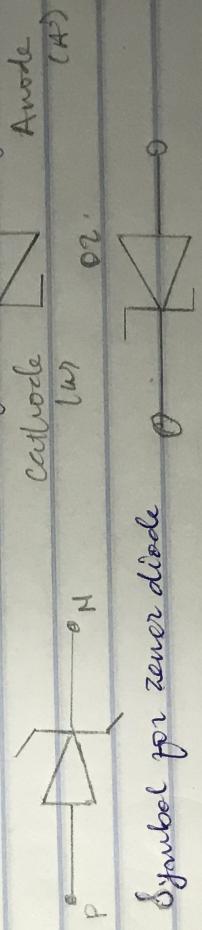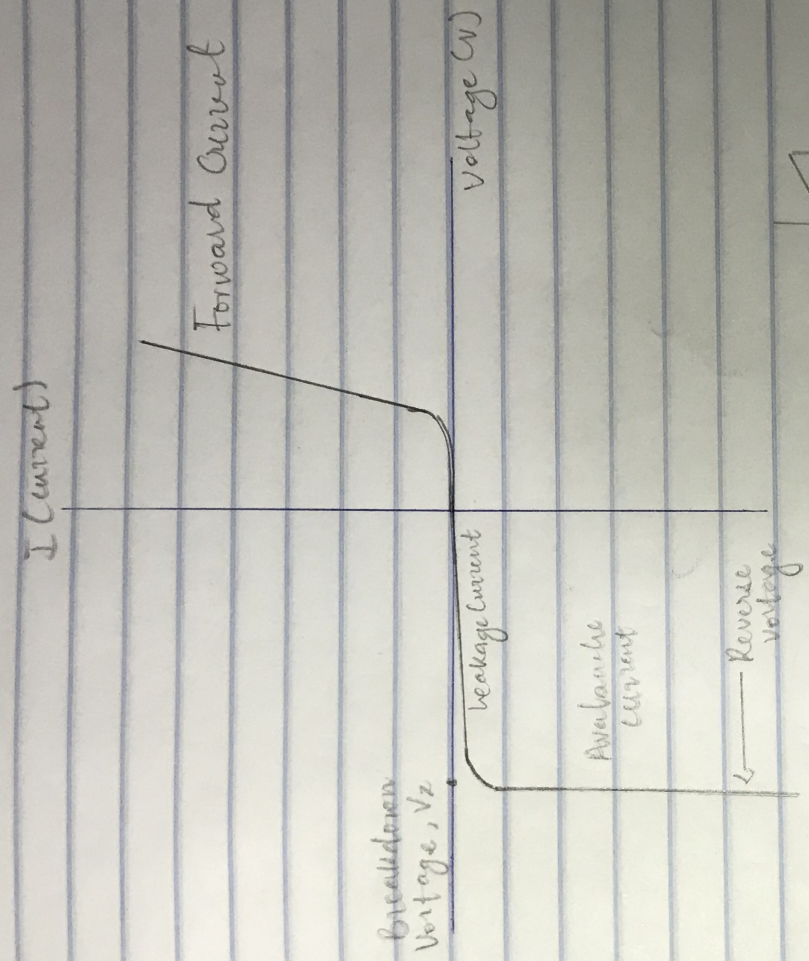i → Sketch the symbol and I-V characteristics curve



Symbol for zener diode

ii → Sketch and label the circuit diagram

