

ANALOGUE ELECTRONICS -
DIODES

① The Zener diode is used in its reverse bias or reverse breakdown mode i.e. the diode anode connects to the negative supply. The ability to control load can be used. Its great effect to regulate a voltage across the load. The source against supply. The fact that the voltage across the diode in the breakdown region is almost constant turns out to be an important application of the zener diode as a voltage regulator.

The function of a regulator is to provide a constant output voltage to a load connected in parallel with it in spite of the ripples in the supply voltage or the variation in the load current and the zener diode will continue to regulate the voltage until the diode current falls below the maximum I_{zmax} value in the reverse breakdown region.

② I-V characteristics curve for zener diode

V_s - DC source
 R_1 - Resistor
 I_L - Load current
 R_L - Load resistance
 V_s - Working source
 V_z - Stabilised output voltage
 I_z - Load current across zener diode

Maximum Power = $I_L R_L$
 $I_{zmax} = 500 \times 10^{-3} \text{ A}$
 $P_{Vmax} = V_s$
 Maximum - Max Power Voltage.
 $500 \times 10^{-3} = \frac{V}{V}$
 $V = \frac{5}{500 \times 10^{-3}} = 10 \text{ Volt}$

\rightarrow Min Resistance = $\frac{V_s - V_z}{I_z}$
 $V_s = 0.637 \times 20$
 $V_s = 0.637 \times 20 = 12.74 \text{ Vdc}$

Min Resistance = $\frac{12.74 - 10}{0.5} = \frac{2.74}{0.5} = 5.48 \Omega$

(ii) Load current
 $I_L = \frac{V_z}{R_L} = \frac{10}{500} = 0.02 \text{ A} = 20 \text{ mA}$

$I_z = I_s - I_L$
 $= 500 - 20$
 48 mA