
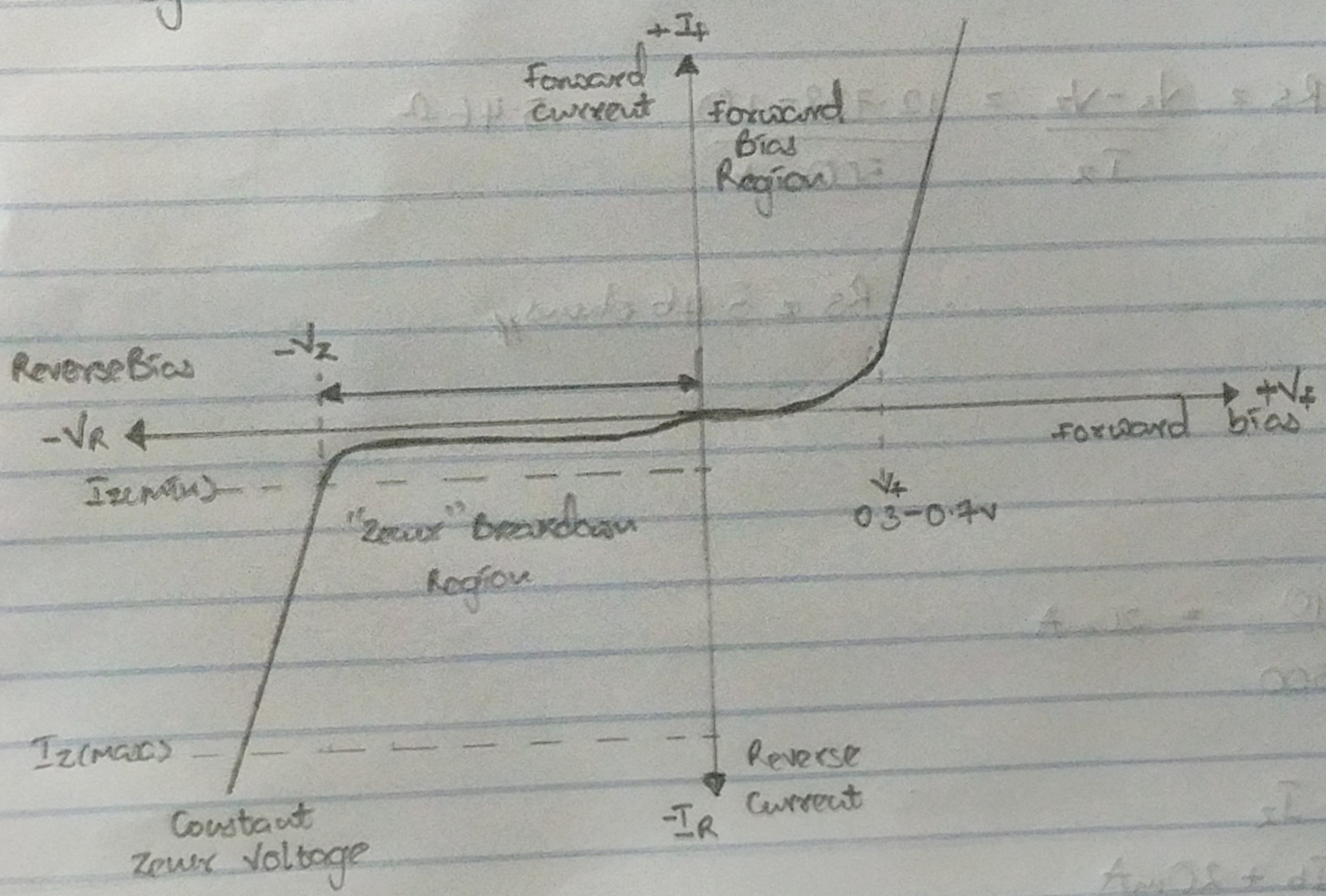



18/ENG06/057

Oliver Ashley I
Mechanical Engineering
ENG222

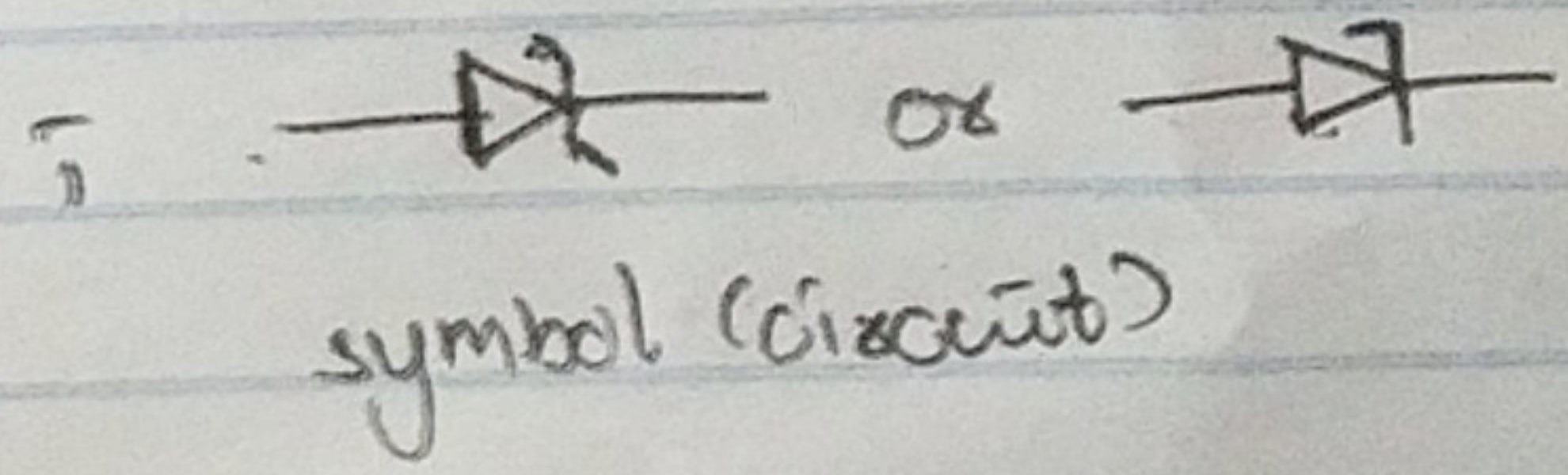1) A zener diode commonly called "Breakdown Diode" is described as a general purpose signal diode consisting of a silicon P-N junction. They have low pre-determined reverse breakdown voltage which also means it is mostly used in its reversed bias mode.



I-V characteristics

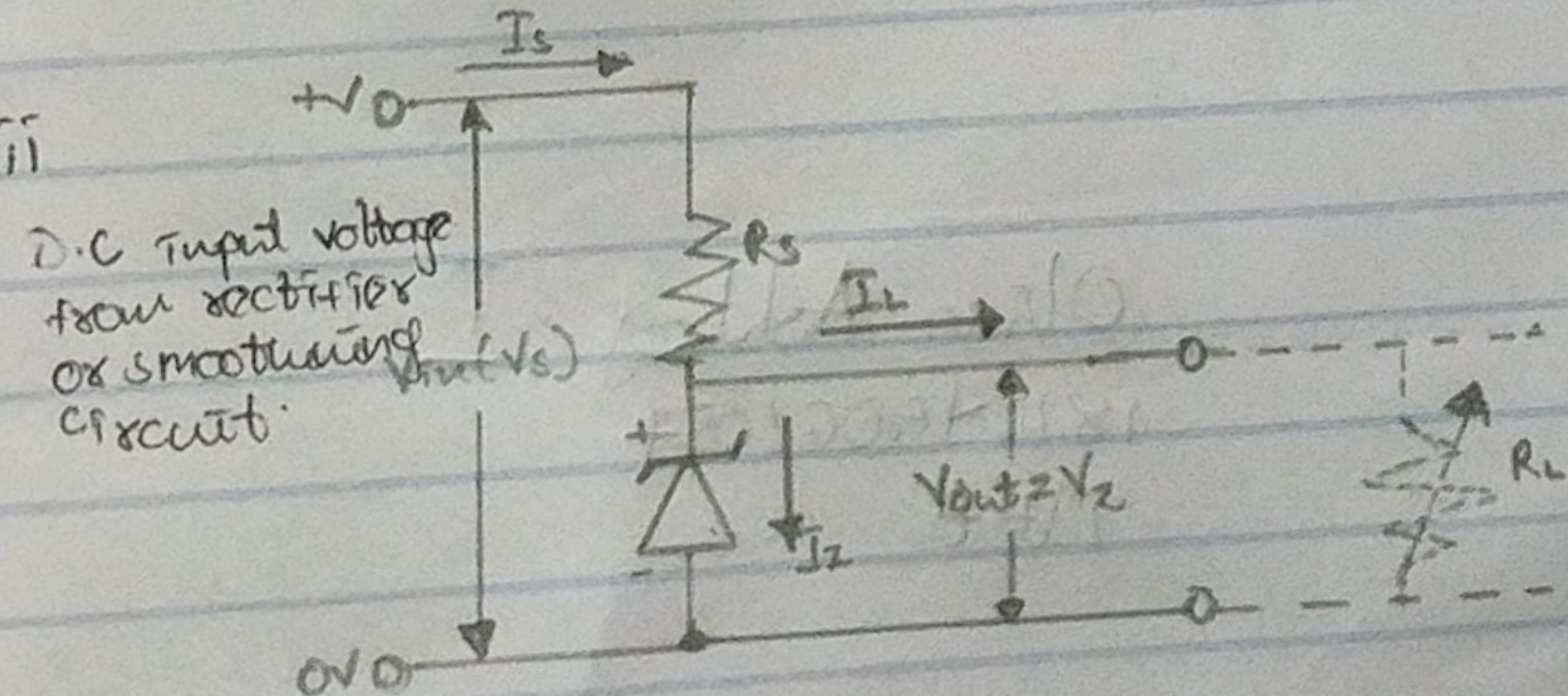

Circuit Diagram

2) minimum value current = 500mA power = 5W
 $V_z = 10V$, $V_{max} = 20V$
 max current = $\frac{\text{watts}}{\text{voltage}}$

$$500mA = \frac{5}{V}$$

$$\text{voltage} = \frac{5}{500 \times 10^{-3}} = 10V$$

$$V_{do} = \frac{2V_{max}}{\sqrt{\pi}} = \frac{2 \times 20}{\sqrt{\pi}} = 12.732V$$

using $R_s = \frac{V_s - V_z}{I_z} = \frac{12.732 - 10}{500mA} = 5.46\Omega$

$\therefore R_s = 5.46 \text{ ohms}$

ii $V = IR$

$$I = \frac{V}{R} = \frac{10}{500} = 20mA$$

$$I_a = I_b + I_z$$

$$500mA = I_b + 20mA$$

$$I_b = 500mA - 20mA$$

$$= 480mA$$

Olivia Ashley - I
 1818NEOG/057
 MEE