
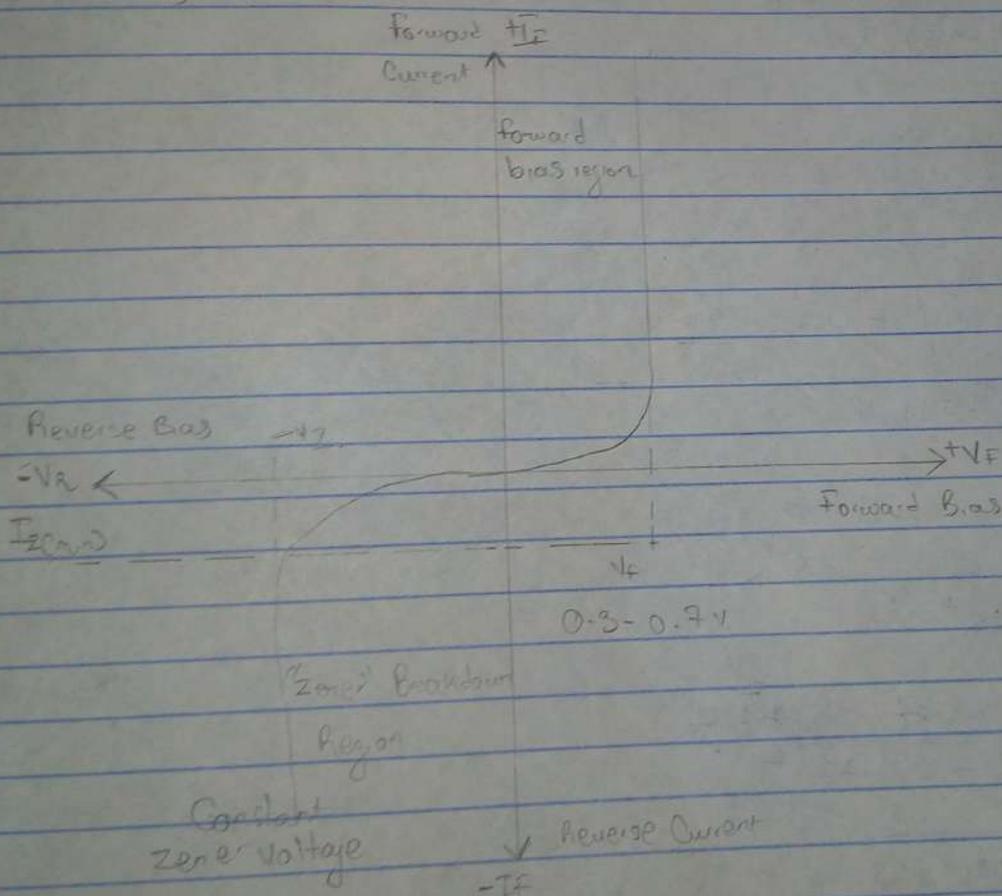


Name: Kalo Sango Nathan
matric No: 181EN02055


Computer Engineering.

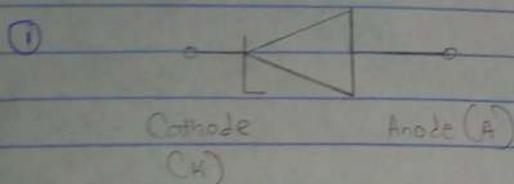1) The Zener diode is used in its "reverse bias" or reverse breakdown mode, i.e. the diode's anode connects to the negative supply. The Zener diode has a region in its reverse bias characteristics of almost a constant negative voltage regardless of the value of the current flowing through the diode and remains nearly constant even with large changes in current as long as the Zener diode current remains between the breakdown current $I_{Z(m)}$ and max current rating $I_Z(max)$



ZENER DIODE I-V CHARACTERISTICS

taken $t=2$, $P=20$, $K=-2$

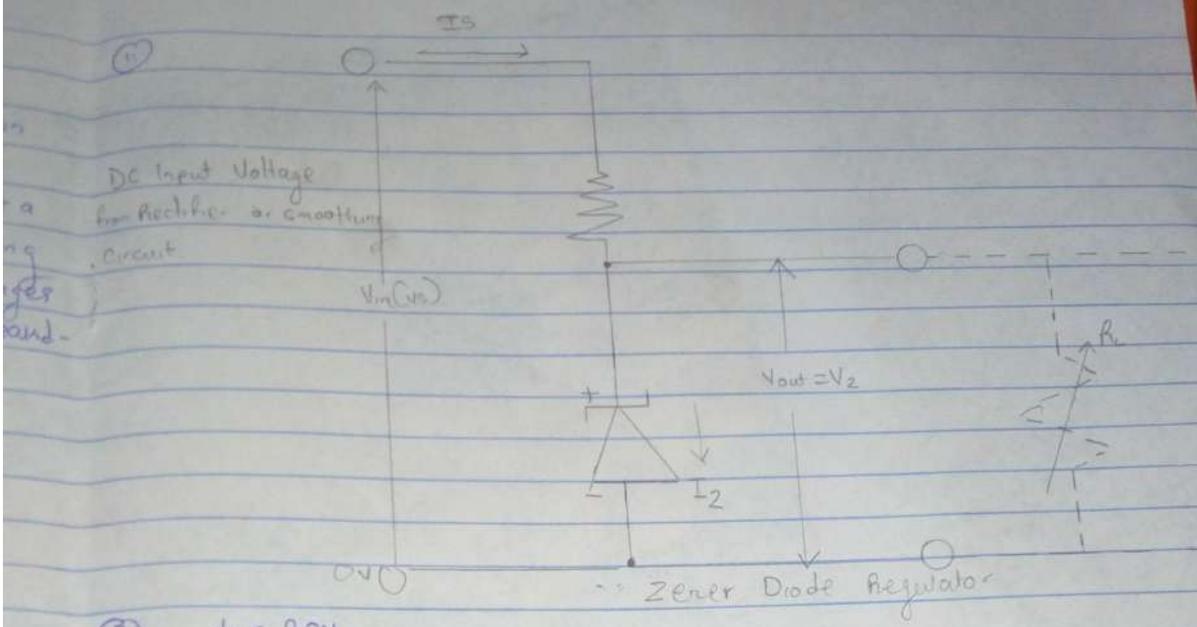

② $V_s = 20V$
 $V_z = ?$
 max current $I = 500mA = 1g$
 $P_z = 5W$

i) $I_{s_{max}} = \frac{P_z}{V_z} = \frac{5}{500 \times 10^{-3}} = 10V$

$\therefore V_z = 10V$
 $R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{500 \times 10^{-3}} = 20$

$R_s = 20\Omega$

ii) $I_z = I_s - I_L$
 $I_L = \frac{V_z}{R_L} = \frac{10}{500} = 0.02A$

$\therefore I_z = (500 - 20) mA = 480 mA$

$t = 2, P = 20, K = 2$