
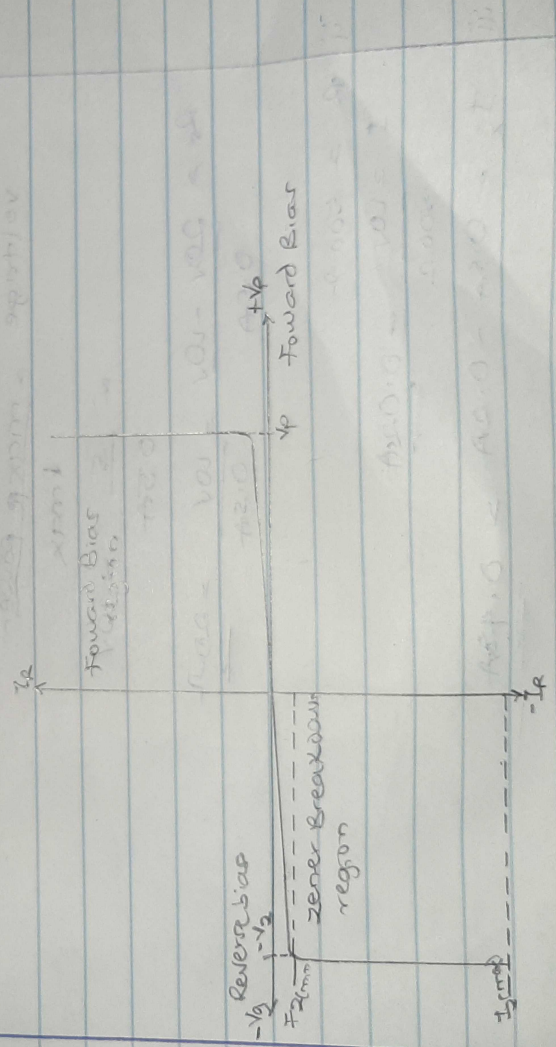


Name: Ketey Godwin Ketey-Olad
 Roll No: 18/ENIA06/035


1 Define a Zener diode regulator.
 2 A Zener diode is a general purpose diode, which behaves like a normal diode when forward biased, but when it is reverse biased above a certain voltage known as Zener breakdown voltage or Zener voltage the voltage remains constant for a wide range of current.

A Zener diode can be used as a regulator, and in this context it can be called a Zener diode regulator since it keeps the voltage constant for a range above the Zener breakdown voltage.

i) symbol for the Zener diode is

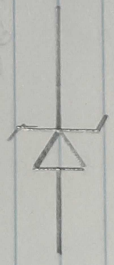

Zener diode I-V characteristic

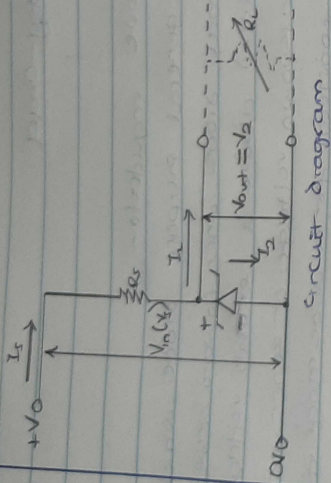

Number 2

Current = $500\text{mA} = 0.5\text{A}$

power (P) = 5watts

maximum current = max power = max voltage

$I_{\text{max}} = 0.5\text{A}$

Voltage = max power

I_{max}

$= \frac{5}{0.5\text{A}} = 10\text{V}$

$P_s = \frac{20\text{V} \cdot 10\text{V}}{0.5\text{A}} = \frac{10\text{V}}{0.5\text{A}} = 20\Omega$

i) $R = 500\Omega$

$I = \frac{10\text{V}}{500\Omega} = 0.02\text{A}$

ii) $I_x = 0.5\text{A} - 0.2\text{A} = 0.48\text{A}$