

NAME: SHUIAB, Khalifa Yaqub

MATRIC N^o: 18/ENG05/056


DEPARTMENT: Mechatronics Engineering

COURSE: ENG 222 (Electrical Engineering
II) Assignment 1

SHUAIB, Khalifa Yaqub
 18/ENG05/056
 Mechatronics Engineering
 ENG 222 Assignment

1.) A zener diode regulator is a type of voltage regulator. They are designed to have a specific reverse breakdown voltage called the Zener Voltage (V_Z). It works like a regular signal diode, although when it is in the reverse bias, it does not conduct electricity until the threshold value (V_Z) is exceeded.

(ii) Circuit Diagram:

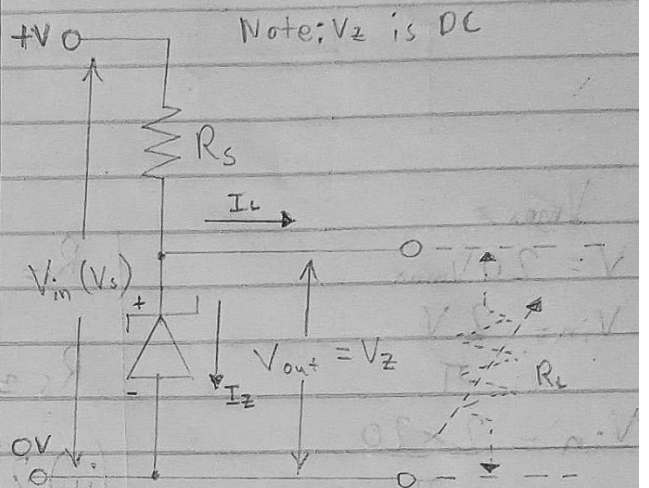

(i) Symbol: cathode (K) Anode (A)

R_L = Load Resistor

R_s = Series Resistor

V_{in} = Input Voltage


V_{out} = Output Voltage

I_L = Load Current


I_Z = Zener Current

V_Z = Zener Voltage

I-V Characteristic Curve:

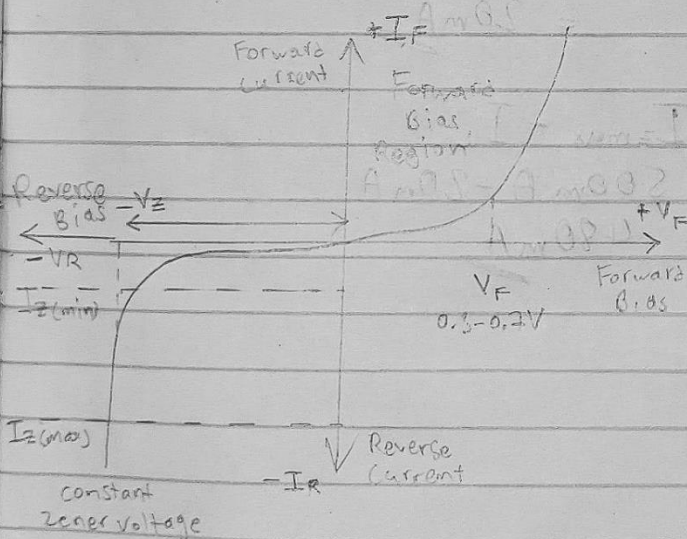

2.) Circuit diagram:

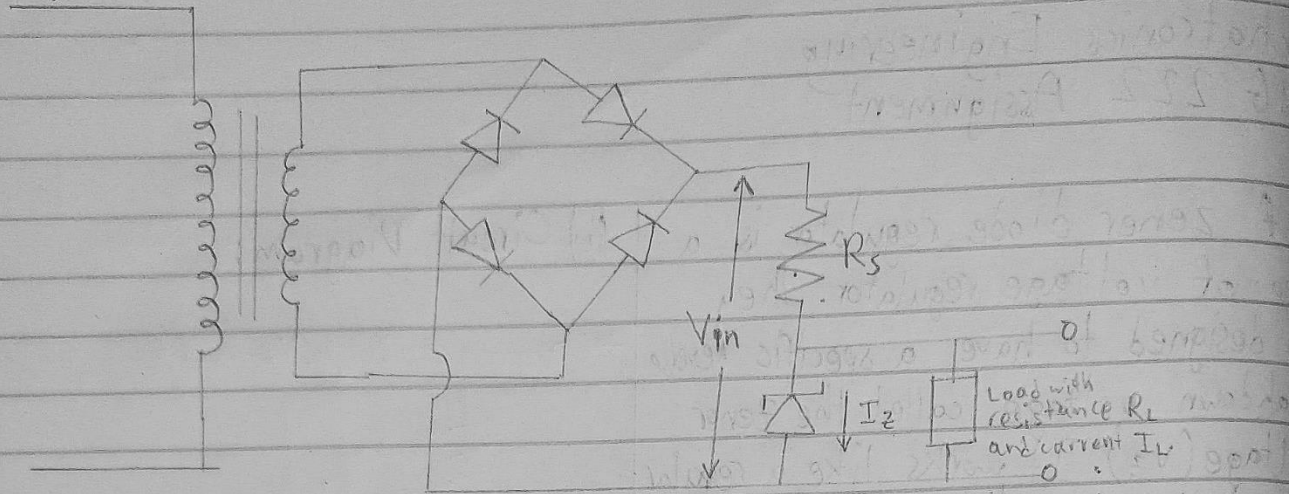

$$V = 20 \sqrt{V_{max}}$$

$$V_{in} = \frac{2V}{\pi}$$

$$V_{in} = \frac{2 \times 20}{\pi} \approx 12.732V$$

$$I_{zmax} = 500mA = 0.5A$$

$$P_z = 5W$$

$$R_s = ?$$

$$I_{zmin} = ? , I_L = ?$$

$$(i) P_z = I_{zmax} \times V_z$$

$$V_z = \frac{P_z}{I_{zmax}}$$

$$= \frac{5}{0.5}$$

$$V_z = 10V$$

$$R_s = \frac{V_{in} - V_z}{I_{zmax}}$$

$$R_s = \frac{12.732 - 10}{0.5}$$

$$R_s \approx 5.464 \Omega$$

(ii) Zener current at full load of $500 \Omega = I_{zmin}$

$$I_L = \frac{V_z}{R_L} = \frac{10}{500}$$

$$= 0.02A$$

$$= 20mA$$

$$I_{zmin} = I_{zmax} - I_L$$

$$= 500mA - 20mA$$

$$= 480mA$$