

Image

Task

Systems Ltd

John-Ogbe Jonathan

19/EM904/062



Elect/Elect

EM9 222


b) The Zener diode is like a general-purpose signal diode consisting of a silicon PN junction. When biased in the forward direction it behaves just like a normal signal diode passing the rated current, but ^{as} soon as a reverse voltage is applied across the zener diode exceeds the rated voltage of the device, the diode's breakdown voltage is reached at which point a process called Avalanche Breakdown occurs in the semiconductor depletion layer and a current starts to flow through the diode to limit this increase in voltage.

Zener Diode I-V Characteristic

Symbol:

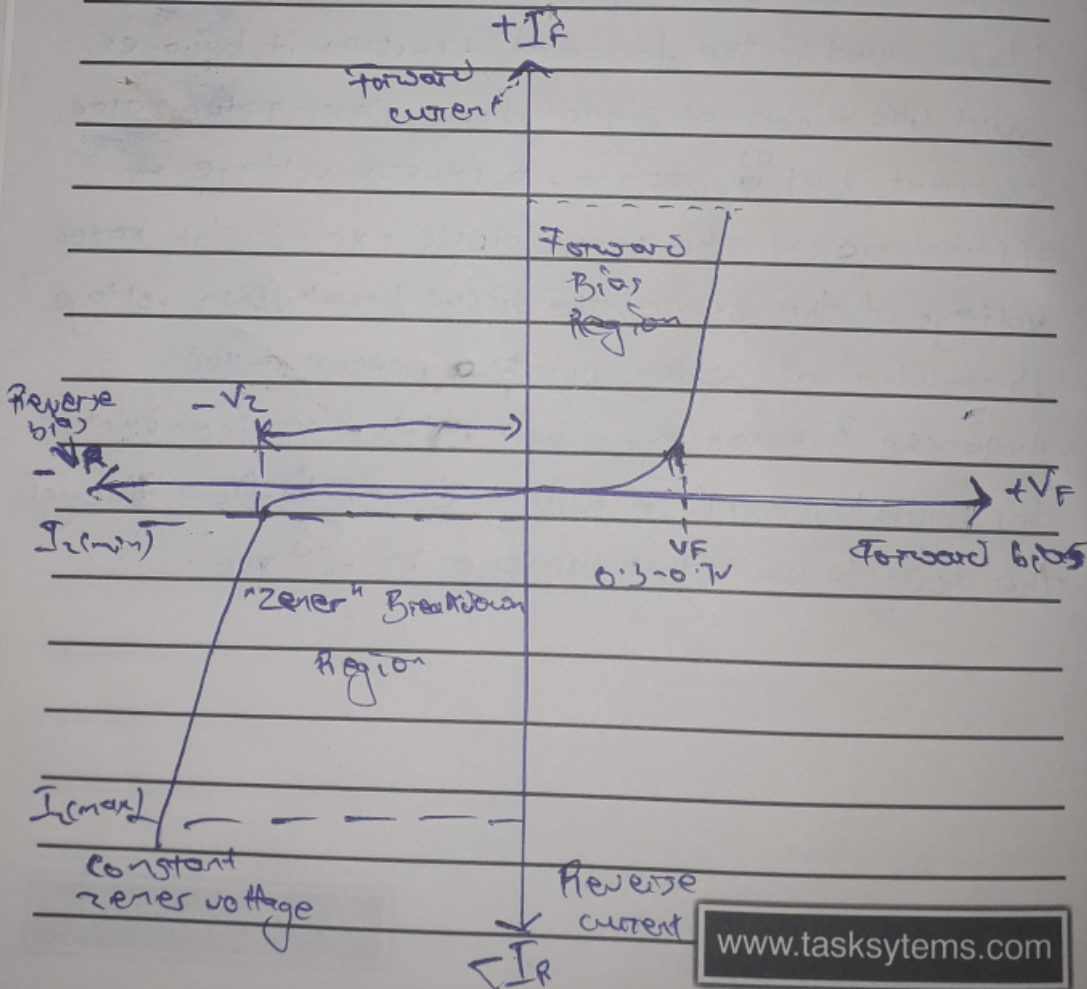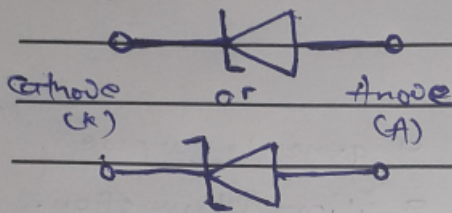

ii) Zener Diode Regulator

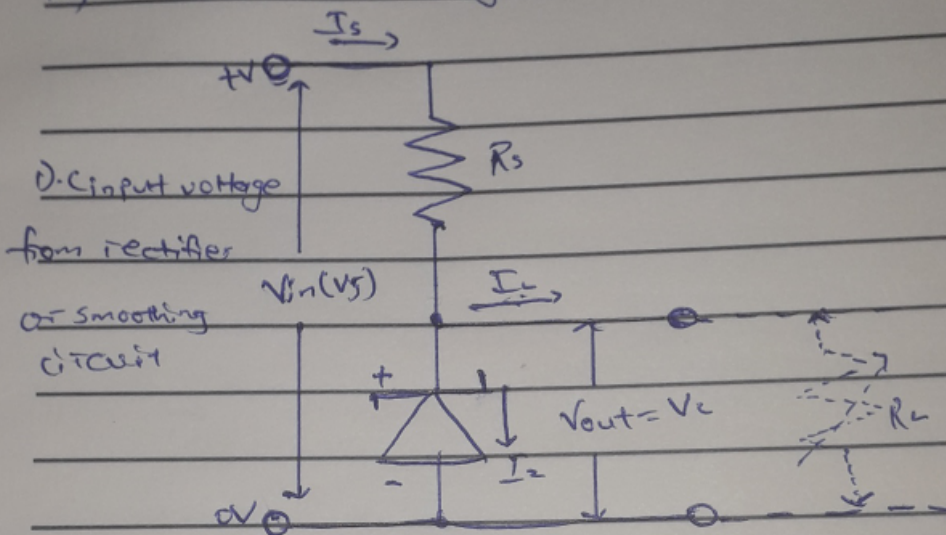

2.)

$$i) V_z = \frac{P_{max}}{I} = \frac{5}{500mA} = 10V$$

$$\therefore \text{Minimum value, } R_s = \frac{V_s - V_z}{I_c} = \frac{20 - 10}{500mA}$$

$$R_s = 20\Omega$$

ii) Current across full load.

$$I_c = \frac{V_z}{R_L} = \frac{10}{500\Omega} = 0.02A$$

