

ISOHABIBI DATONYE


18/Eng06/029

Mechanical Engineering

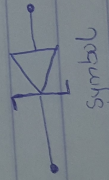
Question 1

A zener diode behaves just like a normal general purpose diode when forward biased but unlike a conventional diode that blocks flow of current in the reverse biased direction, when the reverse voltage reaches a predetermined value, it conducts current.


As a regulator, it can be used to produce a stabilized voltage output with low ripple under varying load current conditions by passing small current through the diode from a voltage source. It basically stabilizes the ripples on the DC output voltage.



Symbol

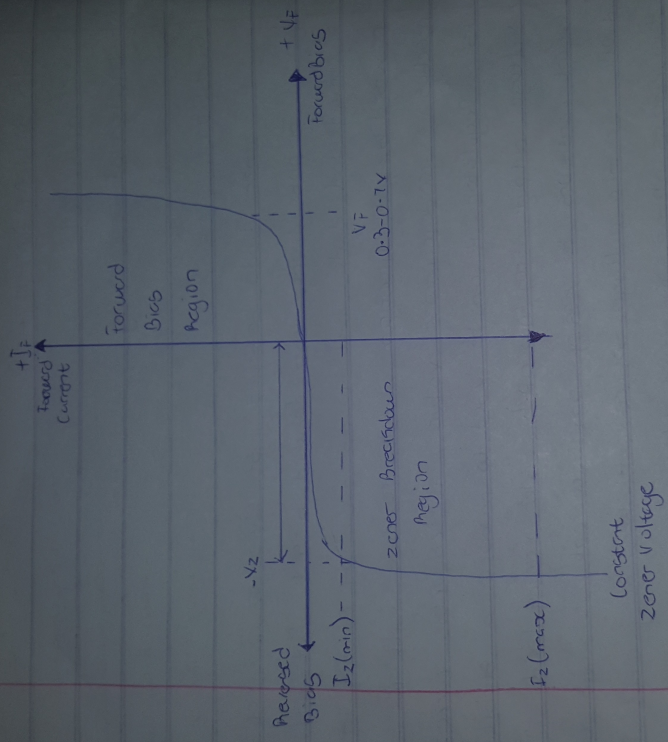

I-V Characteristics

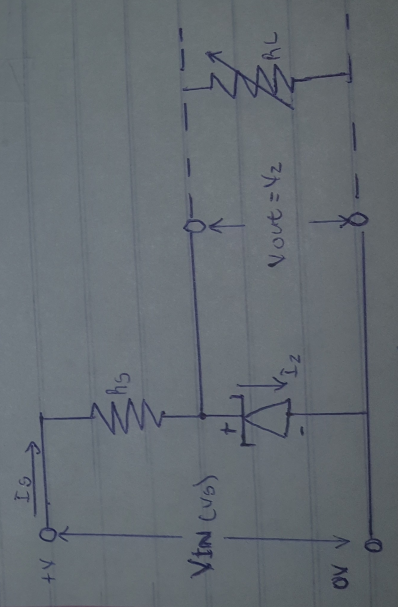

DIAGRAM

Question 2

$$P = IV$$

$$\therefore V = \frac{P}{I_2}$$

$$V_2 = \frac{5 \text{ watts}}{500 \text{ mA}} = 10 \text{ V}$$

Minimum value

$$= \frac{V_1 - V_2}{I_2} = \frac{20 - 10}{500 \text{ mA}}$$

$$R_S = 20 \Omega$$

$$\text{if } I_L = \frac{V_2}{R_L} = \frac{10}{500 \Omega} = 0.02 \text{ A}$$

$$I_L = 0.02 \text{ A}$$