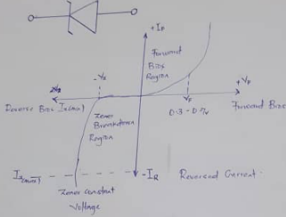
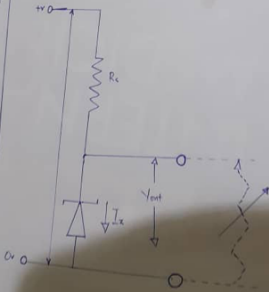


A Zener diode is a diode similar to the standard PN junction diode but they are specially designed to have a low and specified Breakdown voltage.



1-4 Characteristic Curve.



Labels

- V_0 - Source
- R_z - Series Resistor
- V_z - Zener Voltage
- I_z - Zener Current
- I_L - Load Current
- R_L - Load Resistor
- V_L - Load Voltage

Max Power = $I_z \times V_z$
 $I_z = 50 \text{ mA} = 0.05 \text{ A}$
 $V_z = 5 \text{ V}$

Maximum Power = Max Power = $\frac{V_z^2}{R_z}$
 $V_z = 5 \text{ V}$

Minimum Resistance = $\frac{V_z - V_L}{I_z}$
 $V_z = 5 \text{ V}$
 $V_L = 0.5 \text{ V}$
 $I_z = 0.05 \text{ A}$
 $= 10 \text{ } \Omega$

Minimum Resistance = $\frac{12.74 - 10}{0.5}$
 $= 5.48 \text{ } \Omega$

Load Current $I_L = \frac{V_z}{R_L}$

$= \frac{5 \text{ V}}{10 \text{ } \Omega} = 0.5 \text{ A}$