

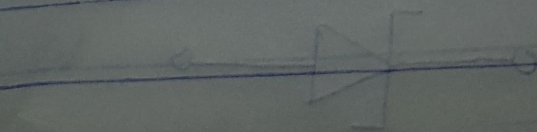



NWUDU OKECHUKWY JEREMIAH
18/ENG041055
ELECTRICAL/ELECTRONICS ENGINEERING


- 1 Zener diode is a type of diode that allows current to flow in the conventional manner from its anode to its cathode i.e. when the anode is positive with respect to the cathode. When the voltage across the terminals is reversed and the potential reaches the Zener voltage (or "knee"), the junction will break down and current will flow in the reverse direction a desired characteristic. However, the Zener Diode or "Breakdown Diode" as they are sometimes called are basically the same as the standard PN junction diode but are specially designed to have a low predetermined reverse breakdown voltage that takes advantage of this high reverse voltage

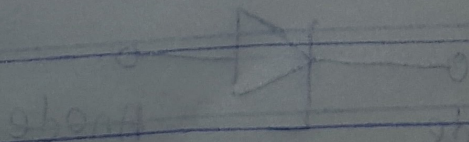

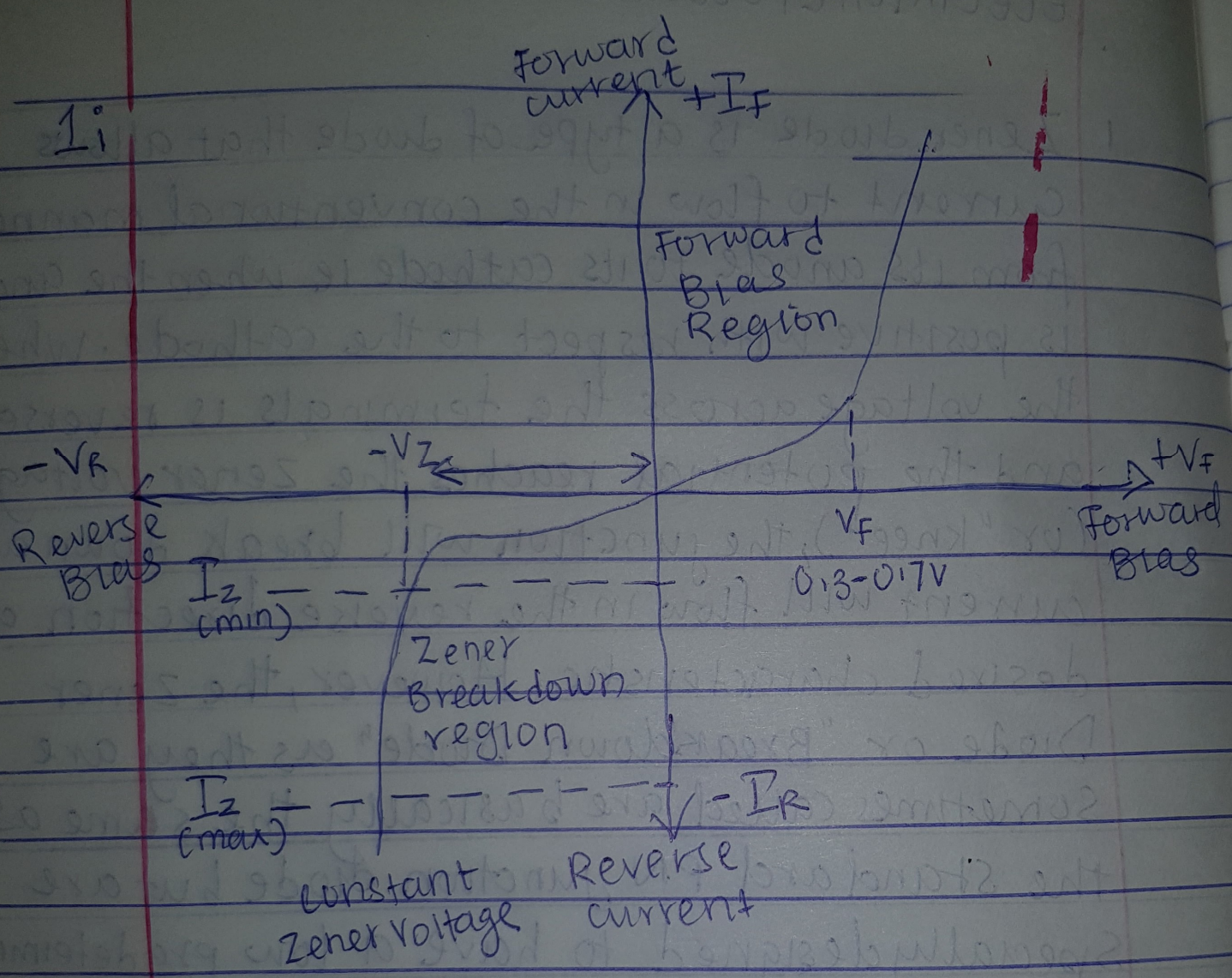

symbol

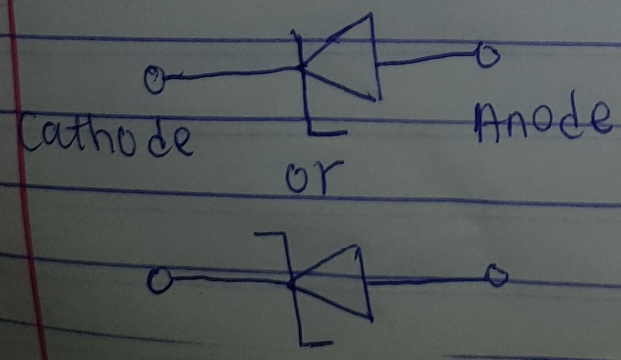

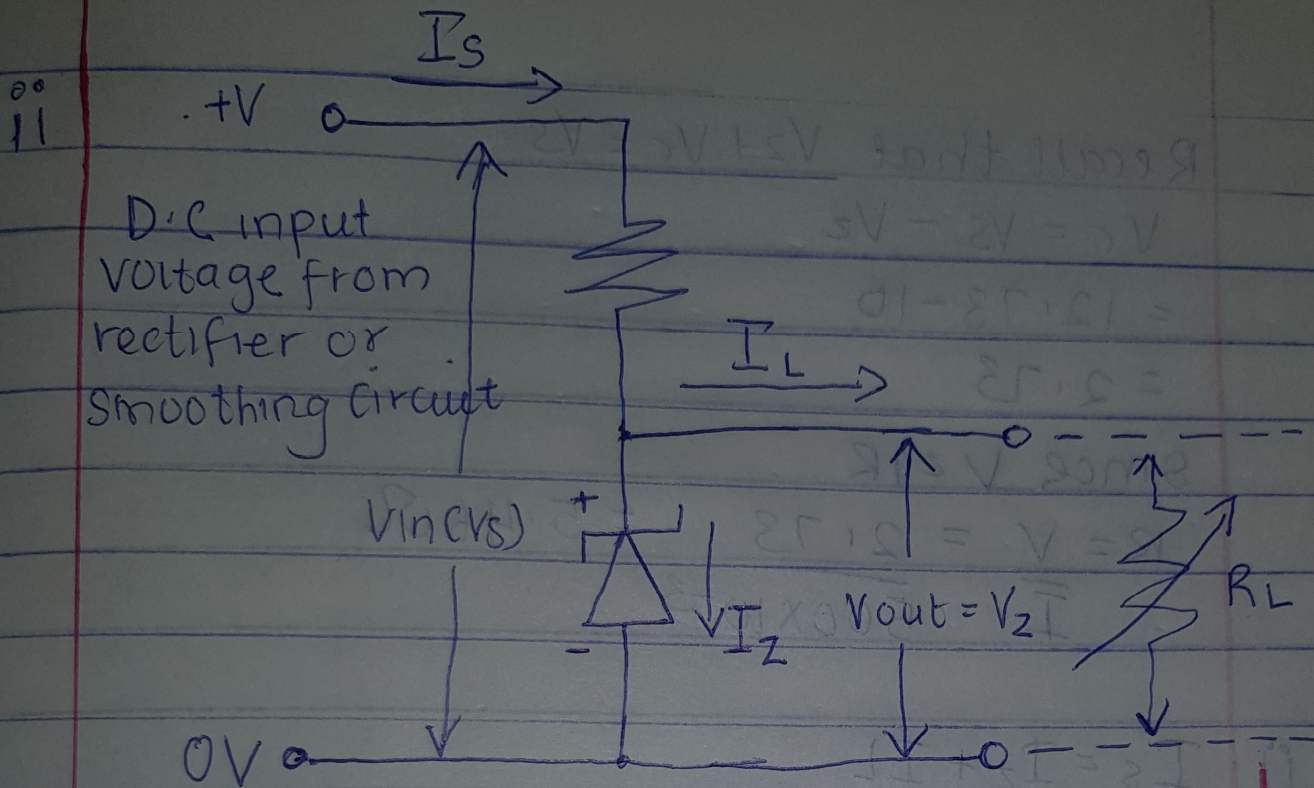

2 i) $P_z = 5W$

$I_z = 500mA$

$20V_{max}$

To convert V_{max} to V_{DC}

$$V_s = V_{DC} = \frac{2V_{max}}{\pi}$$

$$V_s = \frac{2 \times 20}{\pi} = 12.73V_{DC}$$

Recall that $P = IV$

$$V_z = \frac{P_z}{I_z} = \frac{5}{500 \times 10^{-3}} = 10V$$

Recall that $V_z + V_r = V_s$

$$V_r = V_s - V_z$$

$$= 12.73 - 10$$

$$= 2.73$$

Since $V = IR$

$$R = \frac{V}{I} = \frac{2.73}{500 \times 10^{-3}} = 5.46 \Omega$$

$$\bar{I} = 500 \times 10^{-3}$$

ii $I_s = I_z + I_L$

$$I_z = I_s - I_L$$

$$I_L = \frac{V_z}{R} = \frac{10V}{500\Omega} = 0.02A = 20mA$$

$$I_z = 500mA - 20mA$$

$$= 480mA = 0.48A$$