

ASALEM ALABO JOSHUA  
18/ENG06/007  
MECHANICAL ENGINEERING  
ENG 222



### Assignment



- 1) Describe a Zener diode regulator and
- a) sketch the symbol and I-V characteristic curve
- b) sketch and label the circuit diagram

### Answer

A zener diode is a special type of rectifying diode that can handle breakdown due to reverse breakdown voltage without failing completely. It allows current to flow in either a forward or reverse direction. A semiconductor diode will suffer from premature breakdown or damage if the reverse voltage applied across becomes too high. But zener diodes are designed to have a low and specified Reverse Breakdown Voltage which takes advantage of any reverse voltage applied to it.

Zener diode as a voltage regulator consists of a current limiting resistor  $R_s$ , connected to in series with the input voltage  $V_s$  with the zener diode  $R_z$  in this reversed biased condition. The  $S$  connected in parallel with the load  $R_L$  in this reversed biased condition. The stabilized output voltage is always selected to be the same as the breakdown voltage  $V_z$  of the diode. The function of the regulator is to provide a constant output voltage to a load connected in parallel with it. Despite of the ripples in the supply voltage or the variation in the load current  $I_L$ , the Zener diode will continue to regulate the voltage until the diode current  $I_z$  falls below the minimum value in the reverse breakdown region.

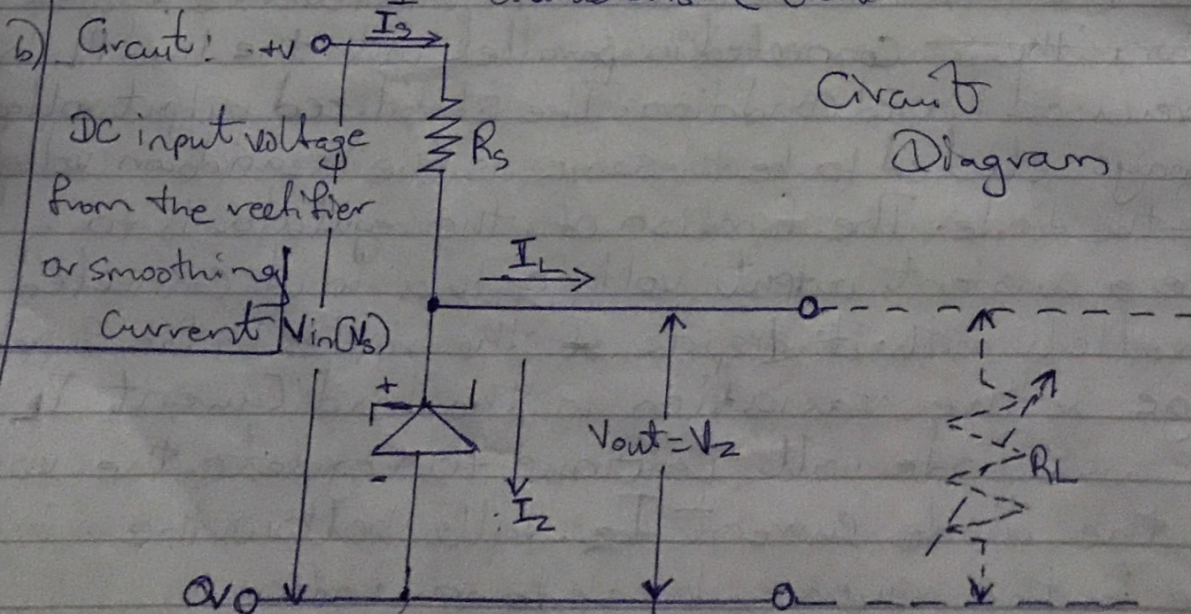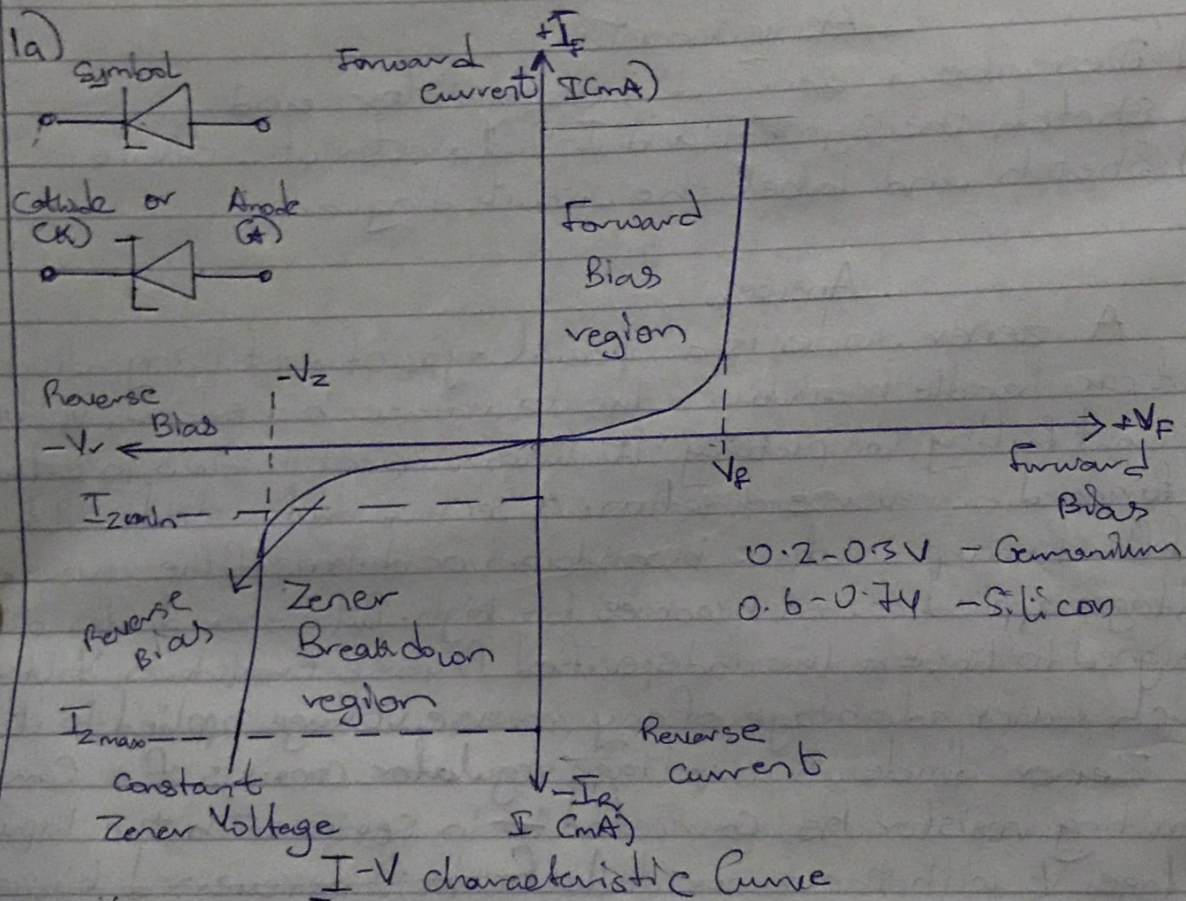Then to summarise a little, a Zener diode is always operated in its reverse biased condition. As such a simple voltage regulator circuit can be designed using a Zener diode to maintain a constant DC output voltage across the load in spite of variations in the input voltage or changes in the load current.



2)

$$P = 5W$$

$$I_A = 500mA = 500 \times 10^{-3}$$

$$= 0.5A$$

$$V_{max} = 20V_{max}$$

$$V_{dc} = \frac{2 \times V_{max}}{\pi} = \frac{2 \times 20}{\pi}$$

$$= \frac{40}{3.142}$$

$$= 12.73V_{dc}$$

i) The minimum value of the series resistor of the zener diode;  $R_s = \frac{V_s - V_z}{I_z}$ ,  $V_z = ??$

$$P = IV$$

$$P_z = I_z V_z$$

$$V_z = \frac{P_z}{I_z} = \left( \frac{5}{0.5} \right) V$$

$$= 10V$$

$$R_s = \frac{12.73 - 10}{0.5}$$

$$= \frac{2.73}{0.5}$$

$$\therefore = 5.46 \Omega$$

ii) The current across the diode at full load of  $500 \Omega$

$$I_L = \frac{V_z}{R_L}$$

$$= \frac{10}{500}$$

$$= 0.02A$$

$$\therefore I_L = 20mA$$

$$V_z = 10V$$

$$R_L = 500 \Omega$$