


Ogundare Emmanuel Jesuferanmi
1016N61061055

Mechanical Engineering.


i) Describe zener diode regulator

This consists of a current limiting resistor R_s connected in series with the input voltage V_s with the zener diode R_z in the reverse biased condition. The established output voltage is always selected to be ^{the} ~~rather~~ same as the breakdown voltage V_z of the diode. The function of a regulator is to provide a constant output voltage to a load connected in parallel with it in spite of the ripples in the supply voltage or ~~the~~ variation in the load current in parallel with it or ~~the~~ variation in the load current and the zener diode will continue to regulate the voltage until the diodes current falls below the minimum $I_{z(min)}$ value in the reverse breakdown region. There're two types of regulator such as line regulation and load regulation.

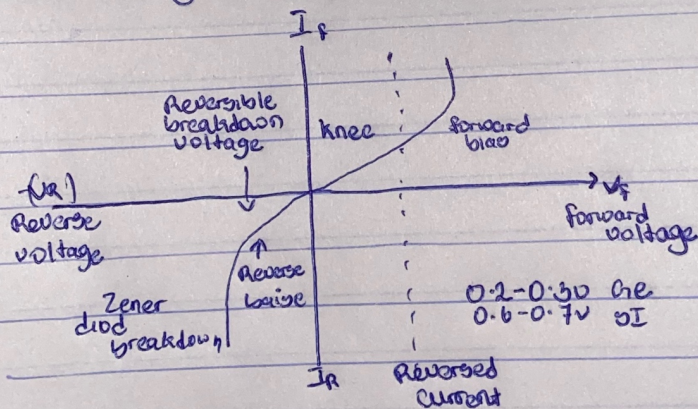ii) Sketch the symbol and I-V characteristic curve



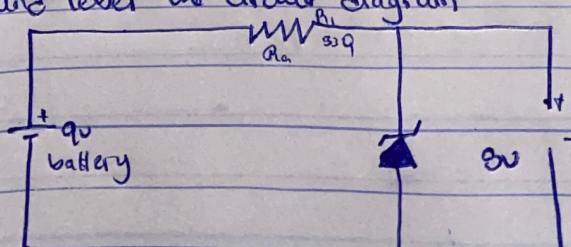iii) sketch and label the circuit diagram



$$2 \quad P_z = 5W$$

$$I_z = 500mA$$

$$20V \text{ max}$$

To convert V_{max} to V_{DC}

$$V_{DC} = \frac{2V_{\text{max}}}{\pi}$$

$$V_0 = \frac{2 \times 20}{\pi} = 12.73 \text{ VDC}$$

Recall that $P = IV$

$$\therefore V_z = \frac{P_z}{I_z} = \frac{5}{500 \times 10^{-3}}$$

$$V_z = 10V$$

Recall that $V_z + V_R = V_0$

$$V_R = V_0 - V_z$$

$$= 12.73 - 10$$

$$= 2.73V$$

$$\therefore V = IR$$

$$R = \frac{V}{I} = \frac{2.73}{500 \times 10^{-3}}$$

$$= 5.46$$

Since V_z connected in series and same current flows

$$I_0 = I_z + I_L$$

$$I_z = I_0 - I_L$$

$$I_L = \frac{V_z}{R}$$

$$= \frac{10}{500} = 0.02A = 20mA$$

$$I_z = 500mA = 20mA$$

$$= 480mA \quad \underline{\underline{0.48A}}$$