
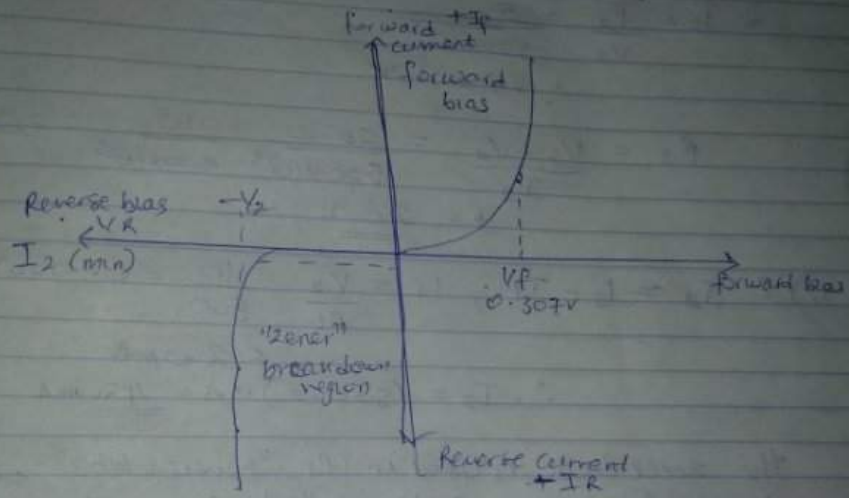


OKUMWENSE OSAYAMEN ENNA
181616041068


Elect/Elect Engineering

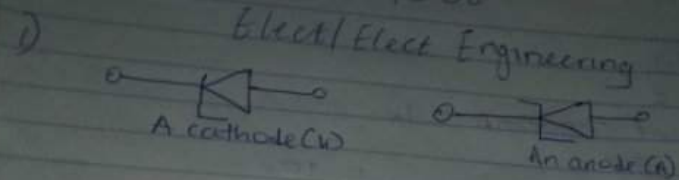

THE ZENER DIODE IV CHARACTERISTICS CURVE

ii) DC input voltage from rectifier or smoothing circuit $V_{in}(V_s)$

THE ZENER DIODE REGULATOR

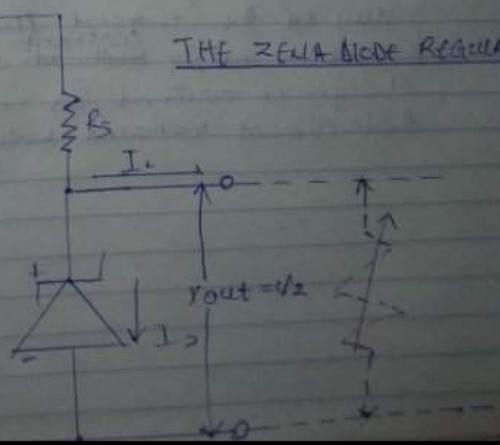

$$2) i) V_1 = 20V$$

$$V_2 = 2$$

$$\text{max current} = 500\text{mA} = I_s$$

$$P_2 = 5W$$

$$i = I_s = \frac{P_2}{V_2} = \frac{5}{500 \times 10^{-3}} = 10V$$

$$\therefore V_2 = 10V$$

$$R_s = \frac{V_s - V_2}{I_2} = \frac{20 - 10}{500 \times 10^{-3}} = \frac{10}{500 \times 10^{-3}} = 20$$

$$R = \underline{20\Omega}$$

$$ii) I_2 = I_s - I_L; I_L = \frac{V_2}{R_L} = \frac{10}{500} = 0.02A$$

$$= 20\text{mA}$$

$$\therefore I_2 = (500 - 20)\text{mA} = \underline{480\text{mA}}$$

The zener diode is used in its "reverse bias" or reverse breakdown mode, i.e. the diode anode is connected to the negative supply. The zener diode has a region in its reverse bias characteristics of almost a constant ~~to~~ negative voltage regardless of the value of the current flowing through the diode. It remains nearly ~~at the~~ ^{constant} even with large changes in current as long as the zener diode current remains between the breakdown