


Arogunmati Oluwadamilola Alexander 18/eng05/011 Mechatronics Engineering

Arogunmati Oluwadamilola Alexander
18/ENG05/011
Mechatronics Engineering


ENG 222 Assignment

① **Zener diode Regulator**


This is a voltage regulator circuit designed using a zener diode to maintain a constant DC output voltage across a load even if the input voltage is changing. When a zener diode is forward biased, it acts like a normal general purpose diode by passing the rated current. However, unlike a normal signal diode which blocks and current when reverse biased, the zener diode begins to conduct in the reverse direction. This happens when the voltage applied across the zener diode exceeds the rated voltage of the device and an Avalanche Breakdown occurs in the depletion layer and current starts to flow through the diode to limit this increase in voltage.

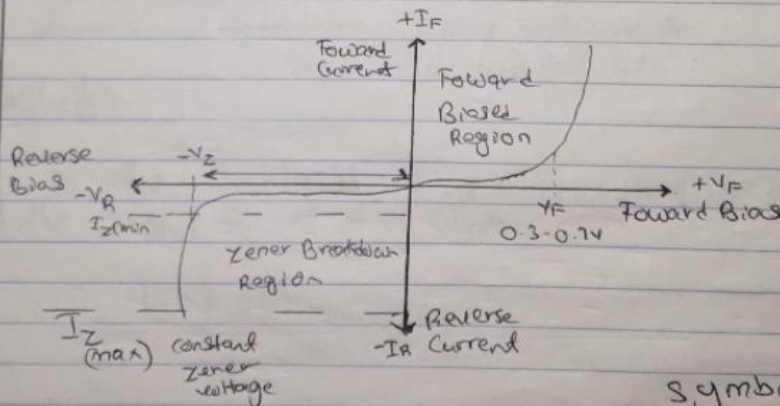

Symbol

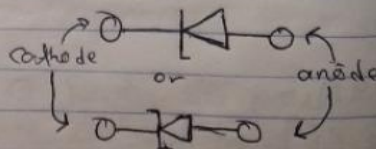

g=00

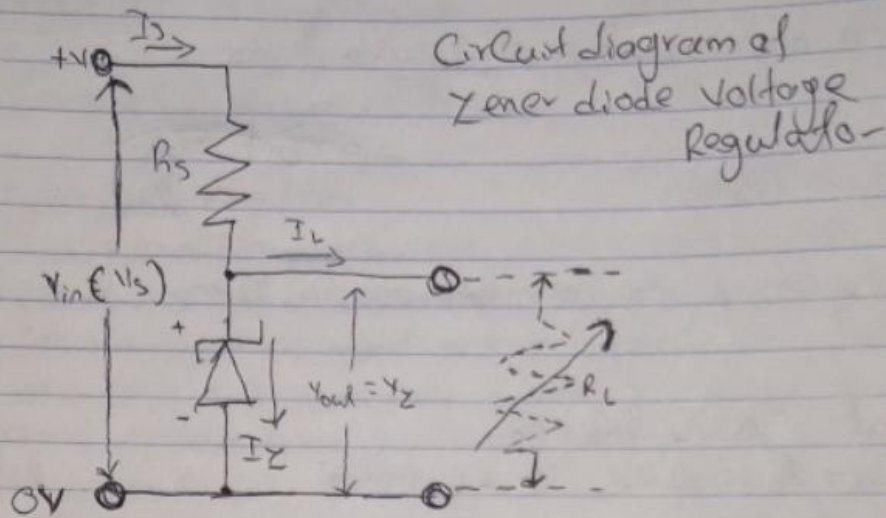

(2) $P = 5W, 30$
 $I_Z = 500mA \Rightarrow 0.5A$
 $V_s \Rightarrow 20V_{max}$

(i) $V_Z = ?$
 $P = I_Z V_Z$
 $\frac{5}{0.5} = V_Z$
 $V_Z = 10 \text{ Volts}$
 $V_s = 20V_{max}$
 $V_{dc} = \frac{2V_{max}}{\pi} \Rightarrow \frac{2 \times 20}{\pi} = 12.73V \text{ (input voltage)}$
 $R_s = \frac{V_s - V_Z}{I_Z} \Rightarrow \frac{12.73 - 10}{0.5} = 5.46 \Omega$

$\therefore 5.46 \Omega$ is the minimum value of the series resistor to the Zener diode

(11) I_2 at $500\ \Omega$ full load

Current across the $500\ \Omega$ resistor

$V \Rightarrow IR$

$$I_L = \frac{V_L}{R_L} \Rightarrow \frac{12.73}{500} \Rightarrow 0.025\text{A}$$

but at full load

$$I_2 + I_L = 0.5\text{A}$$

~~$$I_2 + 500 = 0.5$$~~

$$I_2 + 0.025 = 0.5$$

$$I_2 = 0.5 - 0.025$$

$$\Rightarrow 0.475\text{A} \Rightarrow 475\text{mA}$$