
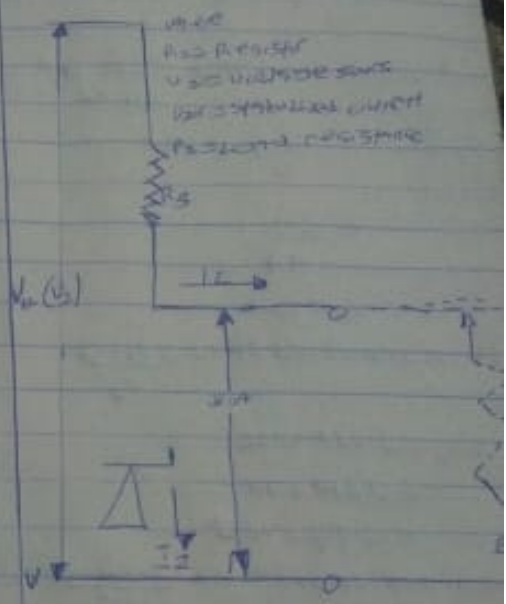
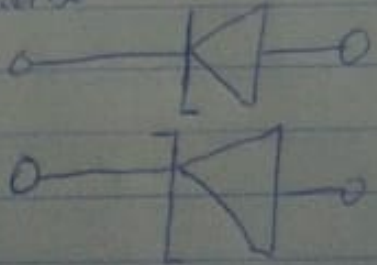


Handed assignments for week 10
 18/11/2023
 mechanical engineering
 basic sketch
 Eng 202

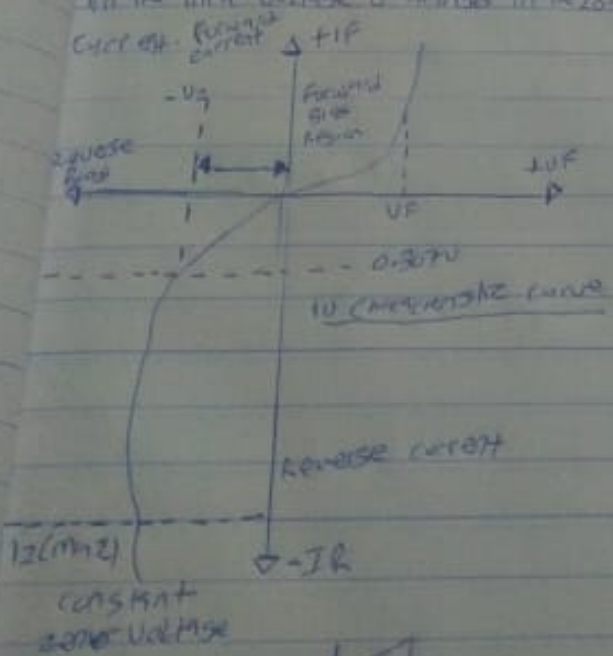(1) describe a zero-volt regulator, and
 sketch the symbol and I-V characteristic
 (2) sketch and label the circuit diagram

A zero-volt regulator is a device which in its
 reverse biased condition as such a zero-volt
 regulator circuit can be designed using a
 zero-volt diode to maintain a constant reverse current
 voltage across the load resistor & maintain
 the output voltage of constant in the load



100 mA current across the
 diode

② The minimum value of the source
resistor is the source value.

$$S_{12} = \text{max. Cur} = 50$$

$$I_2 = 50 \text{ mA} = 0.05 \text{ A}$$

$$V_2 = 20 \text{ V max}$$

③ The minimum current is max. Power
Voltage

$$= \frac{S_{12}}{V} = 0.5 \text{ A}$$

$$V = \frac{S_{12}}{0.5 \text{ A}}$$

$$= 0.5 \text{ A}$$

$$\therefore V_2 = 10 \text{ V}$$

The minimum resistance = $\frac{V_2 - V_1}{I_2}$

$$V_{DC} = 0.637 \text{ V max}$$

$$= 0.637 \times 20$$

$$= 12.74 \text{ V max}$$

$$\text{minimum resistance} = \frac{12.74 - 10}{0.5}$$

$$= 5.48 \text{ } \Omega$$

④ The current across the load at all

load of $900 \text{ } \Omega$

$$\text{Load current } I_L = \frac{V_2 - V_1}{R_L} = \frac{10}{900}$$

$$= 0.02 \text{ A or } 20 \text{ mA}$$

$$I_2 = 15 - 10$$

$$= 500 - 20$$

$$= 480 \text{ mA}$$