

18/ENG051010



Agencia Aceleradora de Partículas
Mechatronics


EN6222

Assignment

1) Zener Diode as voltage regulator. They are widely used as shunt voltage regulators to regulate voltage across small loads. Zener diodes have a sharp reverse breakdown voltage and breakdown voltage will be constant for a wide range of currents. Thus we will connect the zener diode parallel to the load such that the applied voltage will reverse bias it. Thus if the reverse bias voltage across the zener diode exceeds the knee voltage, the voltage across the load will be constant.

Symbol

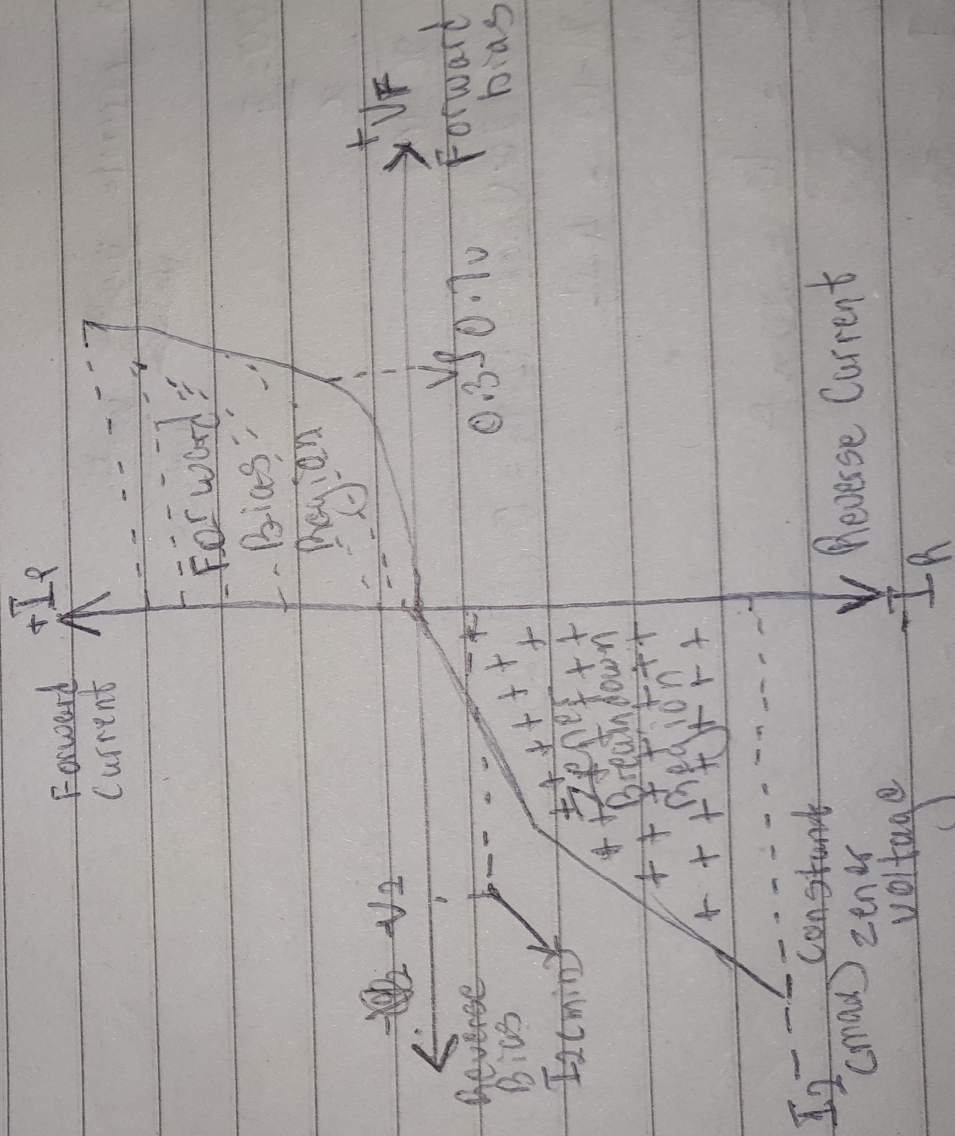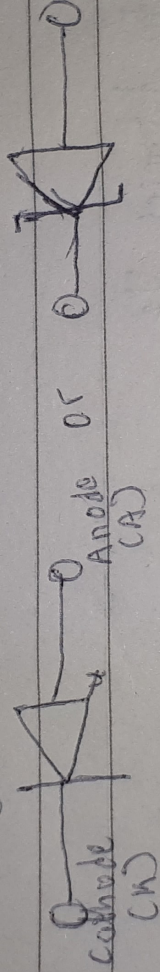

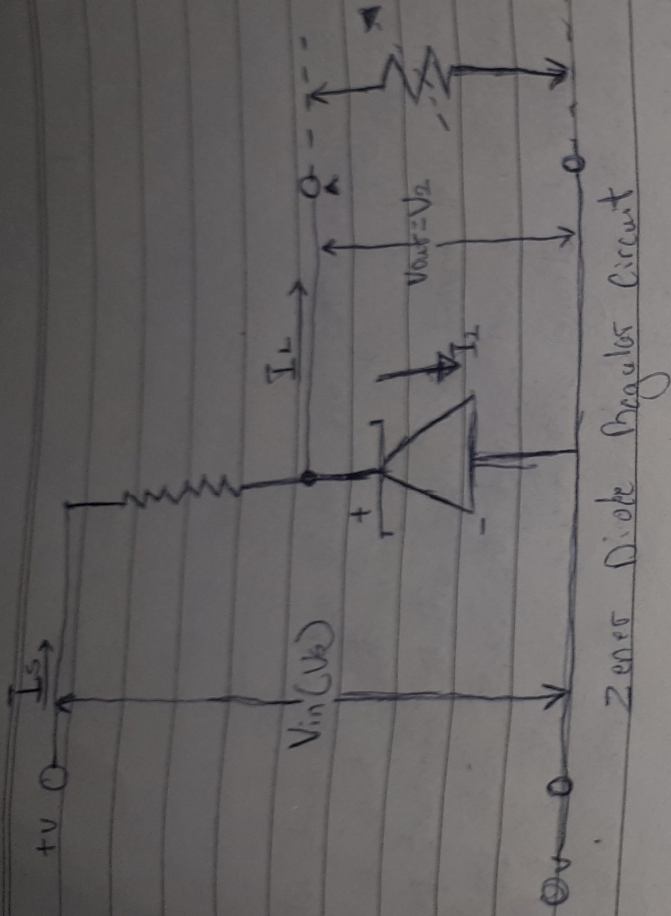

2 To determine the minimum value of the series resistor to the zener diode.

$$R_s = \frac{V_s - V_z}{I_z}$$

I_z

We need to determine V_z

Max current $\frac{\text{watts}}{\text{voltage}}$

$$500 = \frac{\quad}{x}$$

$$x = 10V$$

$$V_s = 20V_{\text{max}} = 12.74 = 0.657 + 20$$

$$R_s = \frac{12.74 - 10}{500} = 4 \Omega$$

$$I_1 = \frac{V_z}{R_L} = \frac{10}{500} = 20 \text{ mA}$$

$$I_2 = I_s - I_1 = 500 \text{ mA} - 20 \text{ mA} = 480 \text{ mA}$$