
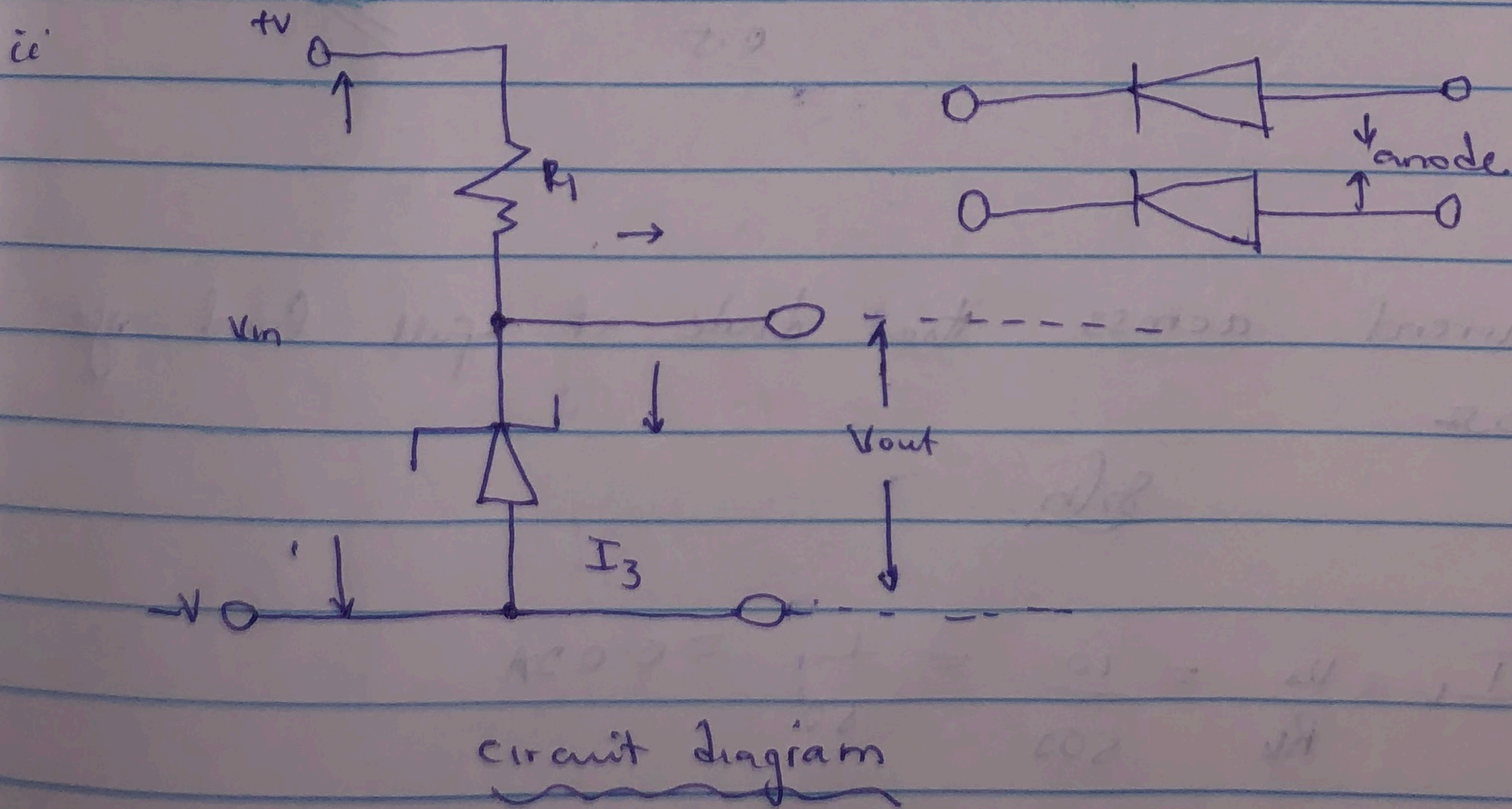


USMAN HARIBA LAMU  
 18/ENG08/025  
 BIOMEDICAL ENGINEERING  
 ENG222

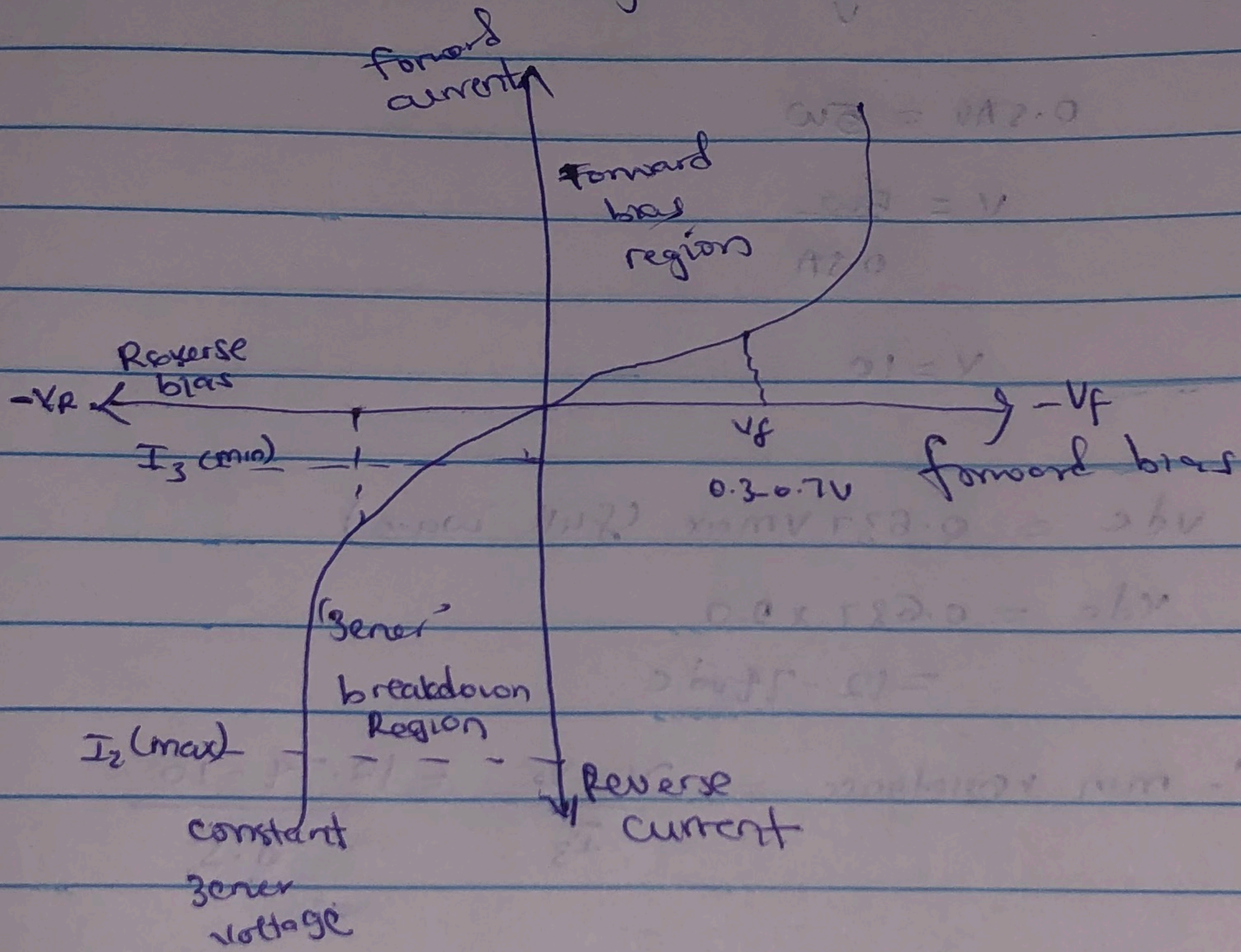i. A zener diode is always operated in its reverse biased condition. As such a simple voltage regulator circuit can be designed using a zener diode to maintain a constant DC output voltage across the load in spite of variations in the input voltage or changes in the load current



2. (i)  $P_z = 5W$

$I_z = 500mA = 0.5A$

Max Current =  $\frac{I_{max} \text{ Power}}{V}$

$0.5A = \frac{5W}{V}$

$0.5AV = 5W$

$V = \frac{5W}{0.5A}$

$V = 10$

But  $v_{dc} = 0.637 V_{max}$  (full wave)

$v_{dc} = 0.637 \times 20$   
 $= 12.74 v_{dc}$

$\therefore \text{min resistance} = \frac{V_2 - V_1}{I_z} = \frac{12.74 - 10}{0.5}$

$= \frac{2.74}{0.5} = 5.48 \Omega$

(ii) The current across the diode at full load of  $500\Omega$

soln

$I_L = \frac{V_2}{R_L} = \frac{10}{500} = \frac{1}{50} = 0.02A$

Current across the diode at  $500\Omega$

full load = 0.02A or 20mA

$$I_3 = I_s - I_n$$

$$= 500 - 20 = 480\text{mA} \text{ or } 0.48\text{A}$$