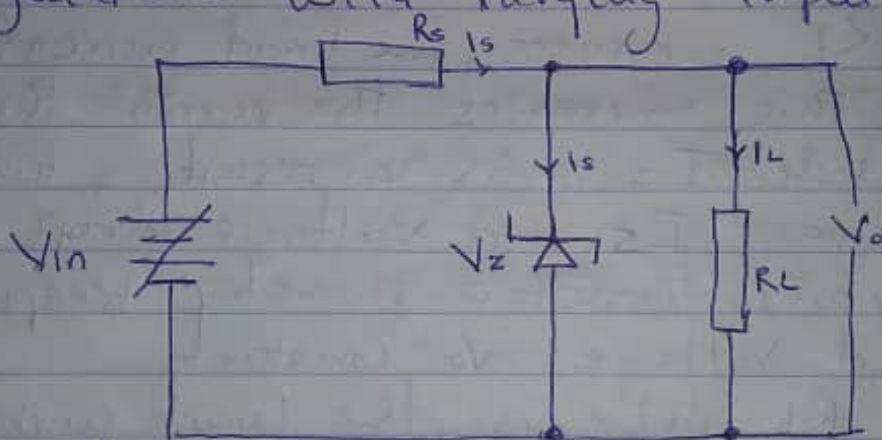


JOHN EDWIN AKPAN.  
18/EM9061033  
MECHANICAL ENA.  
ENA 22.

## Zener Diode Regulator.

This can be described under the following


- (1) Regulation with varying input voltage  $V_{in}$
- (2) Regulation with varying load Resistance  $R_L$
- (3) Regulation with varying input Voltage  $V_{in}$



When  $V_{in}$  increases, input current  $I_s$  also increases. This increases the current through Zener diode  $I_z$  without affecting the load current  $I_L$ . With the increase in input current the voltage drop across resistor  $R_s$  will also increase, thereby keeping the load voltage  $V_o$  constant.

When  $V_{in}$  decreases, the input current also decreases. This decreases the current through Zener diode  $I_z$  without affecting the load current  $I_L$ . With the decrease in input current the voltage drop across resistor  $R_s$  will also decrease thereby keeping the load  $V_o$  constant.

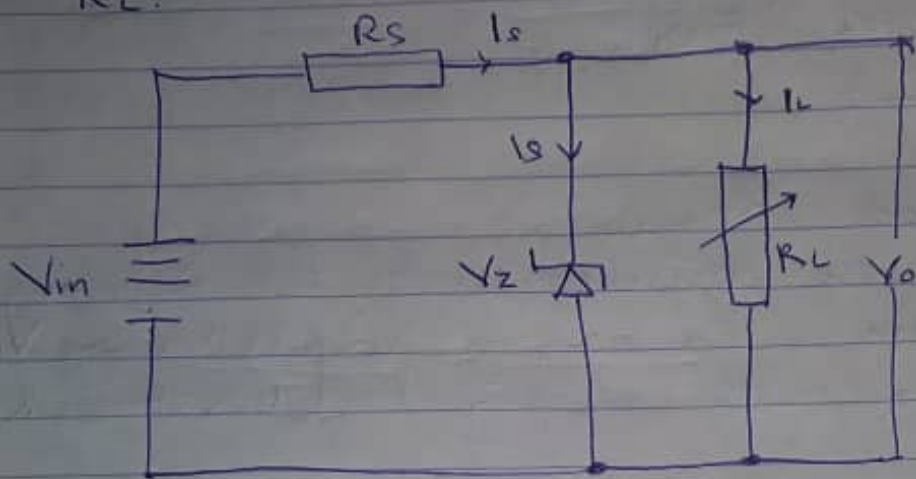
## k) Regulation with varying load resistance $R_L$ .



When  $R_L$  increases, the load current  $I_L$  decreases. This increases the current through Zener diode  $I_z$ . As a result of this the input current  $I_s$  and voltage drop across  $R_s$  remains constant, thereby keeping the load voltage  $V_o$  constant.

When  $R_L$  decreases, the load current  $I_L$  increases. This decreases the current through Zener diode  $I_z$ . As a result of this the input  $I_s$  and voltage drop across  $R_s$  remains constant, thereby keeping the load voltage  $V_o$  constant.


### 1(i) Symbols.

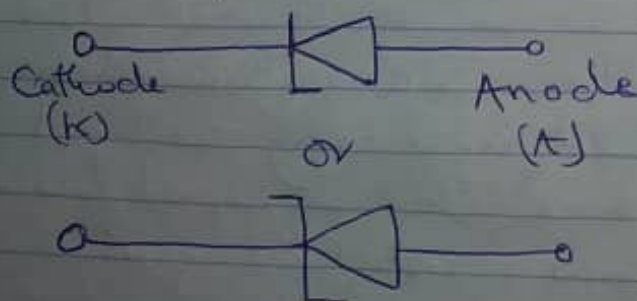




stage

# I-V Characteristic Curve

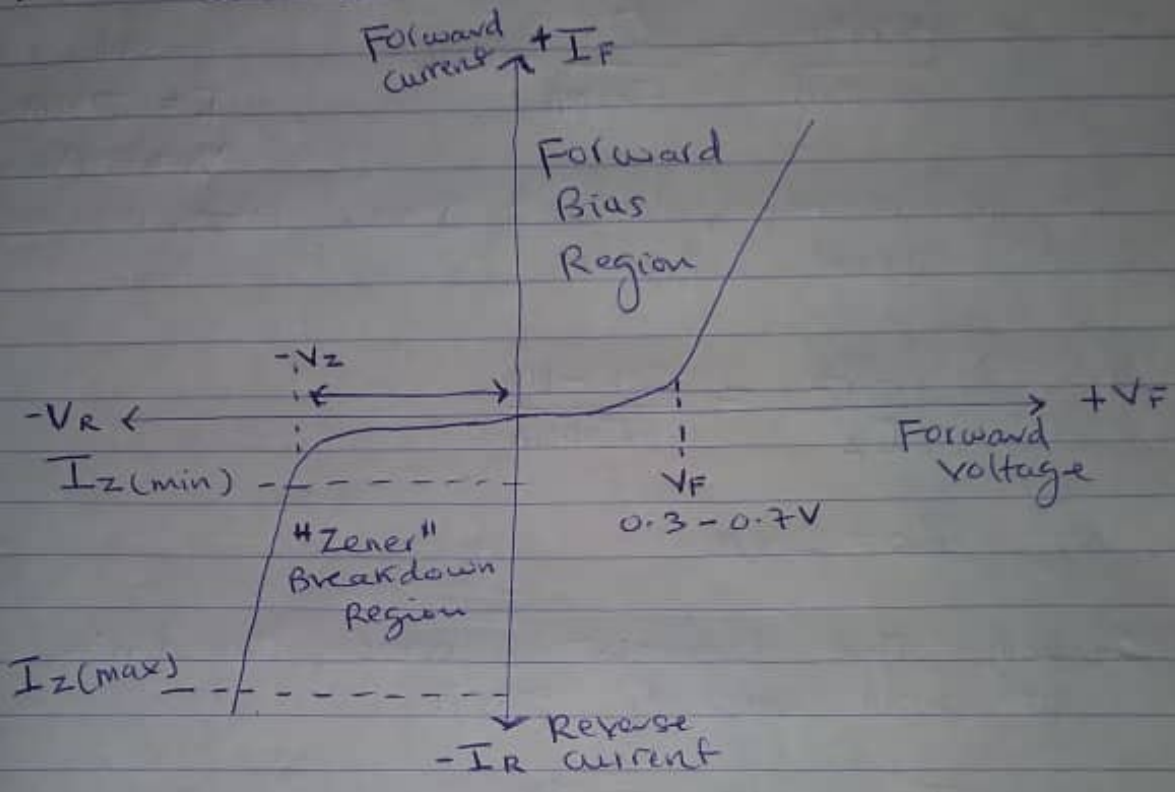

## Circuit Diagram.

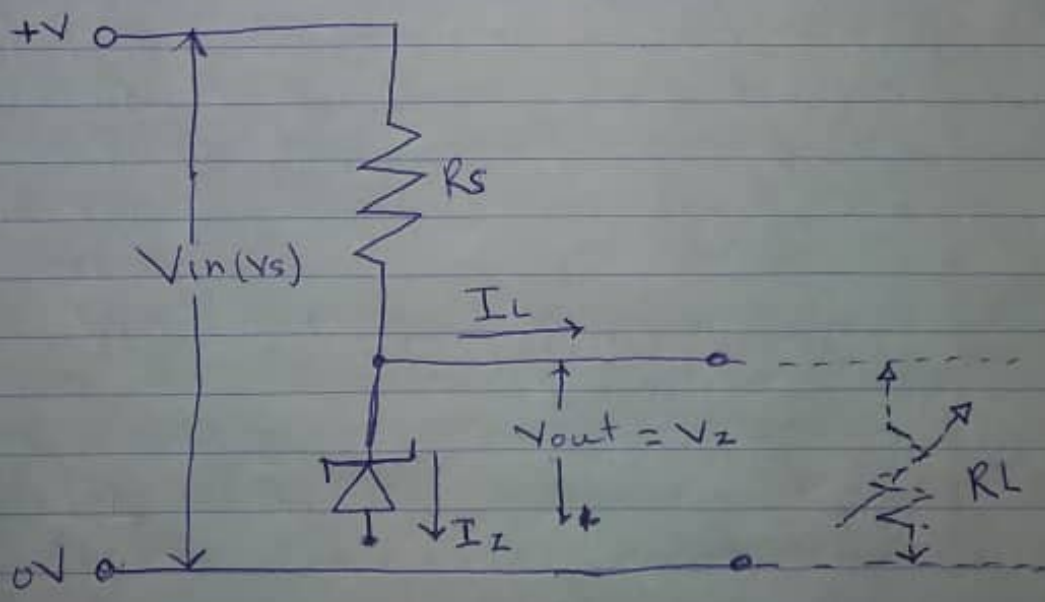

(2) Voltage of the Zener diode.

$$V_z = \frac{\text{Power}}{\text{Current}} = \frac{5}{500\text{mA}} = 10\text{V}$$

$$P = 5\text{W}$$

$$I = 500\text{mA}$$

$$V_s = 20\text{V}_{\text{max}}$$

The minimum value of series resistor of the Zener diode.

$$R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{500\text{mA}}$$

$$R_s = 20\Omega$$

(2)(ii) The current across the diode at full load of  $500\Omega$

$$I_L = \frac{V_z}{R_L} = \frac{10}{500\Omega}$$

$$I_L = 0.02\text{A}$$