
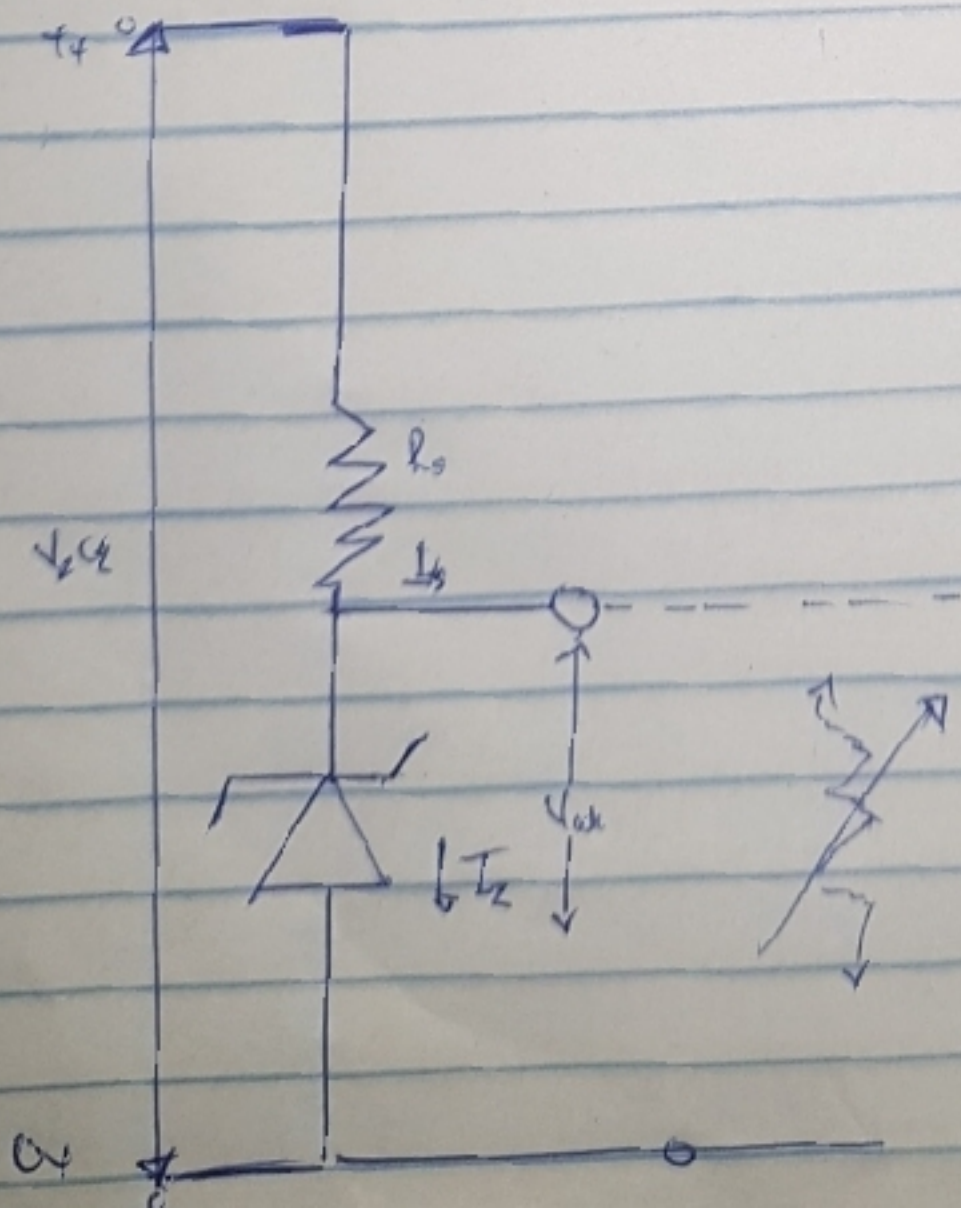
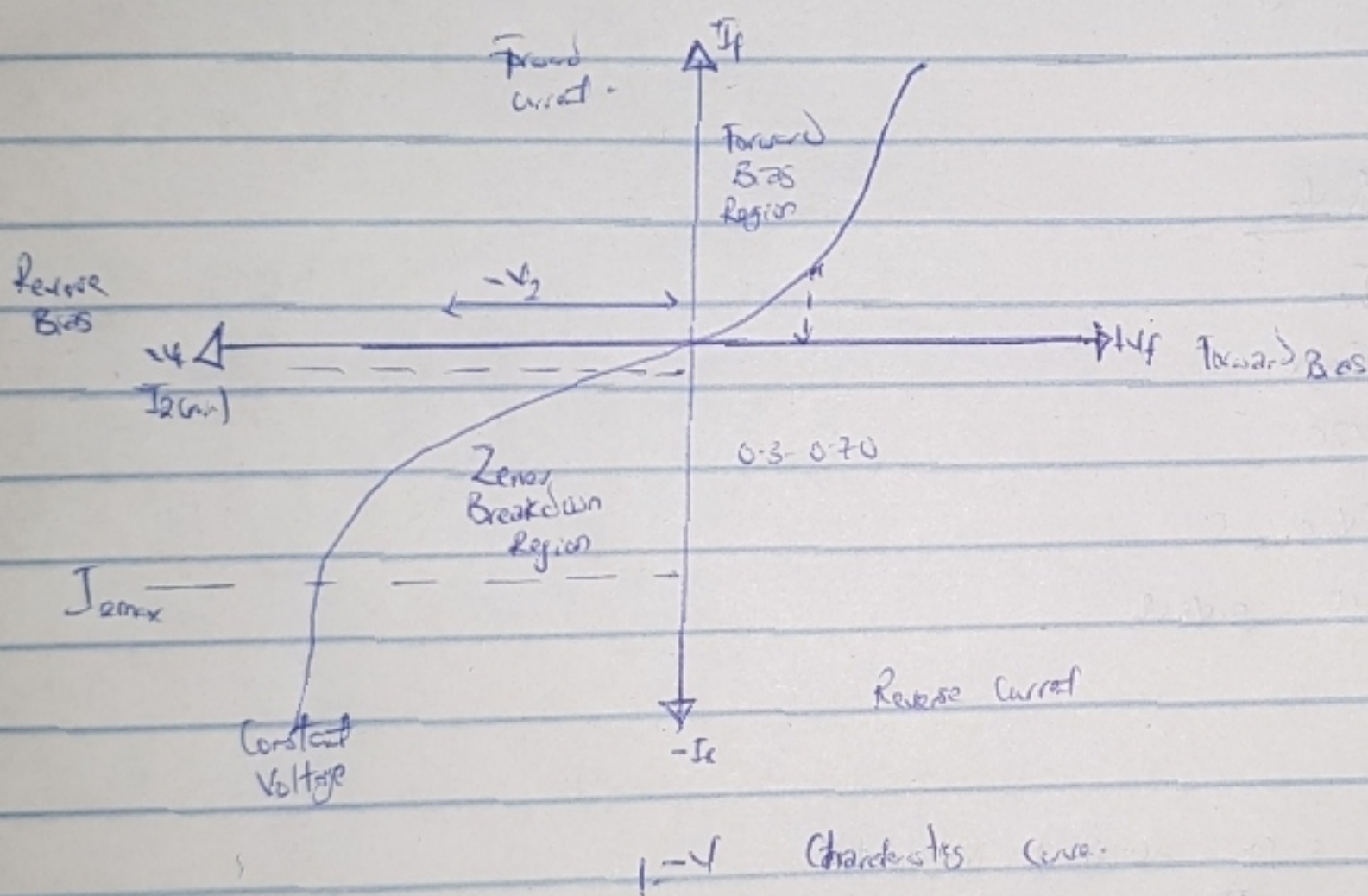


Design of Zener Diode Wisdom

18/MHSA/322

ELECTRICAL ENGINEERING

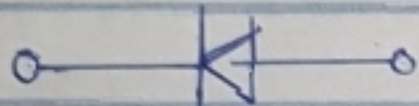1. A Zener diode is a diode similar to the standard P-N Junction diode but they are specially designed to have a low and specified reverse breakdown voltage.



R_s - Resistor

V_s = Voltage source

V_{out} - stabilized output voltage

R_L - Load resistance

I_L - Load current across Load device

2. Max Power = W $I_L = 500mA = 0.5A$, and V_s

$$\text{Maximum Current} = \frac{\text{Maximum Power}}{\text{Voltage}} = \frac{5W}{10V} = 0.5A$$

$$V_2 = 10 \text{ volts}$$

$$\text{Minimum resistance} = \frac{V_s - V_2}{I_L}$$

$$\begin{aligned} b_{dc} &= 0.637 \times \text{max} \\ &= 0.637 \times 20 \\ &= 12.74 \text{ Vdc} \end{aligned}$$

i Minimum resistance = $\frac{12.74 - 10}{0.5} = 5.48 \Omega$

i Load current $I_L = \frac{V_2}{R_L} = \frac{10}{500} = 0.02A$ or $20mA$

$$\begin{aligned} I_2 &= I_s - I_L \\ &= 500 - 20 \\ &= 480 \text{ mA} \end{aligned}$$