
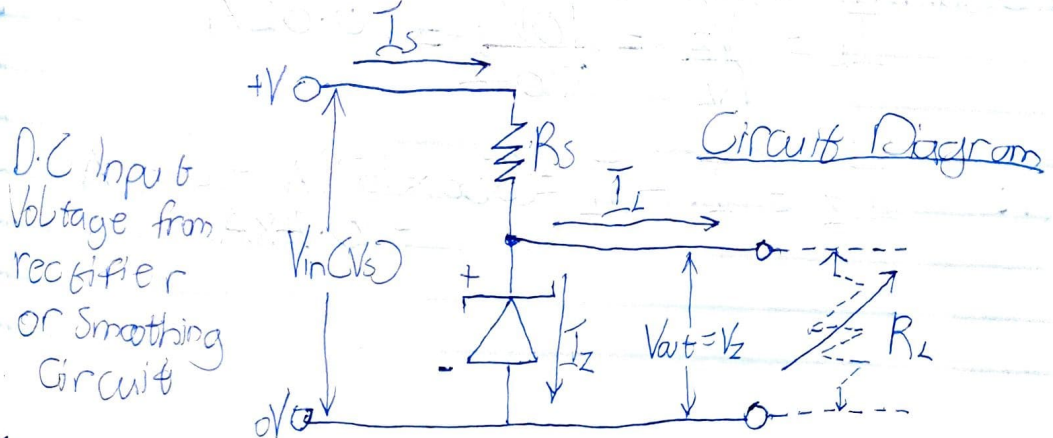
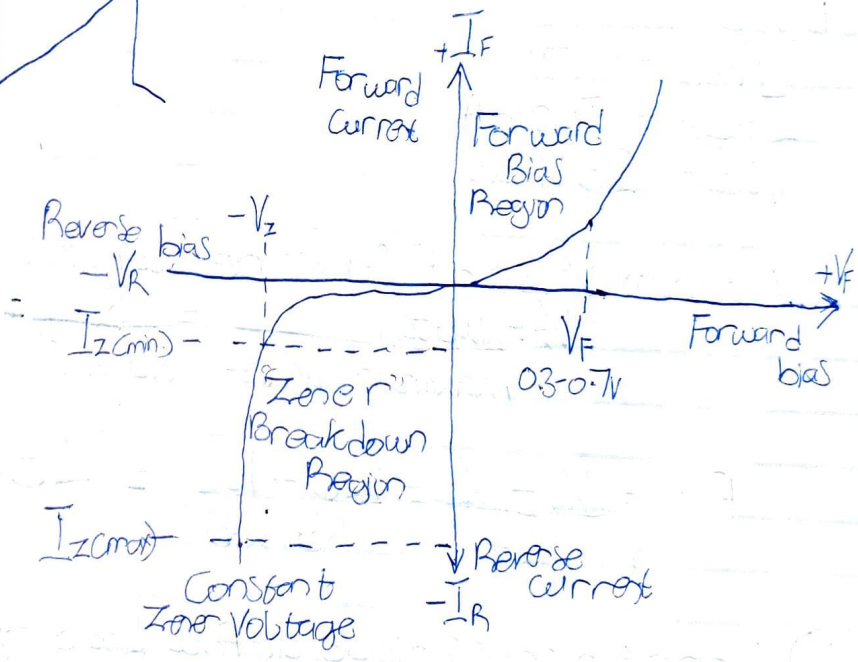


Nwachini Emmanuel Chukwuraemeka
18/ENG 04/054

Electrical/Electronics

1.) Zener diode Regulator;
A Zener diode is always operated in its reverse biased condition. As such a simple voltage regulator circuit can be designed using a Zener diode to maintain a constant DC output voltage across the load in spite of variations in the input voltage or changes in the load current.

It merely entails connecting the Zener diode between the unregulated source of voltage and ground.

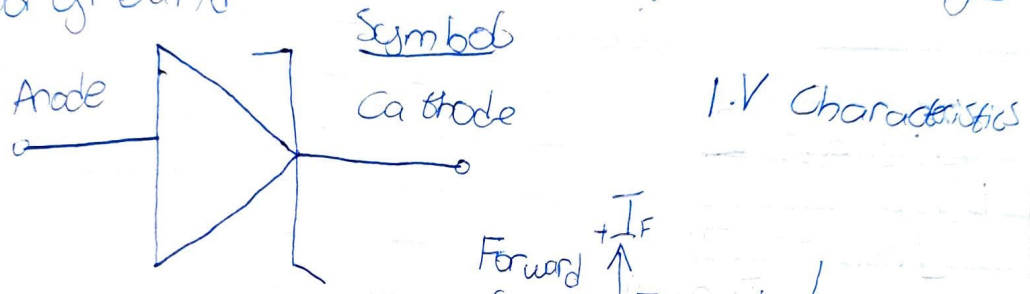

Number 2

Data

$$\text{Power} = 5W$$

$$I_{\text{max}} = 500mA$$

$$V_s = 20V_{\text{max}}$$

i) Minimum value of Series resistor, R_s

$$V_z = \frac{\text{Watts}}{\text{maximum current}} = \frac{5}{500 \times 10^{-3}} = 10V$$

$$R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{500 \times 10^{-3}} = 20\Omega$$

ii) Current across diode at full Load of 500Ω

$$I_L = \frac{V_z}{R_L} = \frac{10V}{500\Omega} = 0.02A$$

$$\therefore I_z = I_s - I_L = (500 \times 10^{-3})A - 0.02A \\ = 0.48A$$