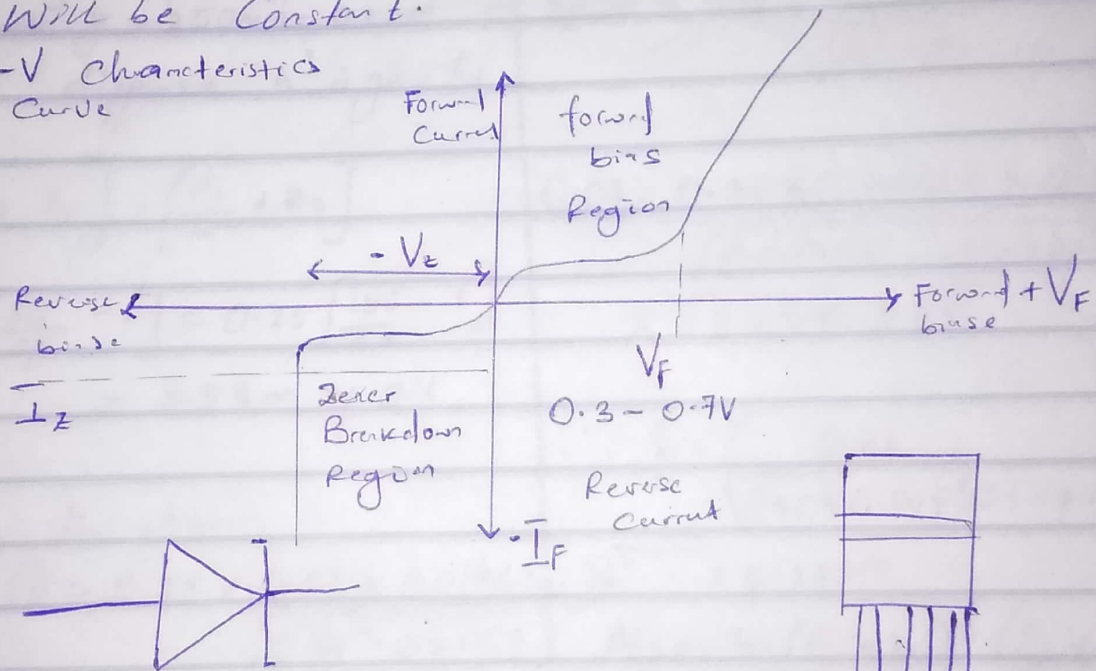



Name: OKPO, Asugbo Eyo  
 Dept: Mechanical Engineering  
 MATRIC NO: 18/ENG06/056

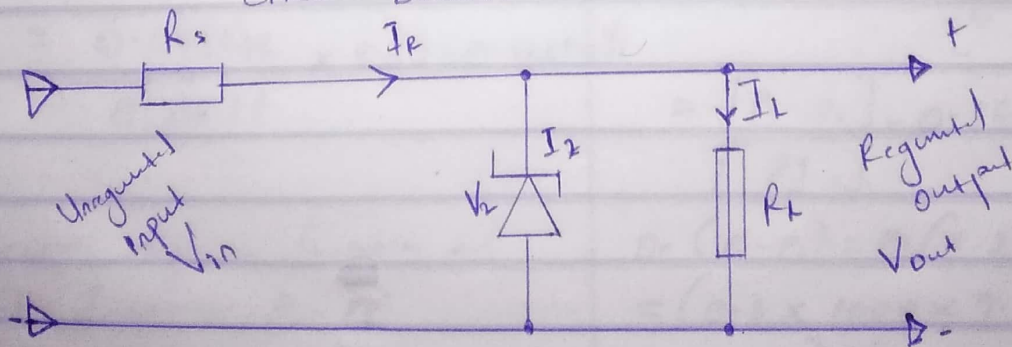(1.) The Zener diodes are used as Shunt Voltage Regulators to regulate voltage across small loads. Zener diodes have a sharp reverse breakdown voltage and breakdown voltage will be constant for a wide range of currents. Hence the Zener diodes will be connected parallel to the load such that the applied voltage will be reverse biased. If the reverse bias voltage across the Zener diode surpasses the knee voltage, the voltage across the load will be constant.

I-V Characteristics Curve



ZENER DIODE VOLTAGE REGULATOR Voltage Regulator  
Circuit Diagram



$$2(i) \text{ Maximum Current} = \frac{\text{Watts}}{\text{Output Voltage}}$$

$$\text{Watts} = 5W$$

$$\text{Max Current} = 500\text{MA}$$

$$\text{Output Voltage} = ?$$

$$V_s = 20V_{\text{max}}$$

$$500\text{MA} = \frac{5}{V}$$

$$500V = 5$$

$$\text{Output Voltage} = \frac{5}{500\text{MA}} = \frac{5}{0.5A} = 10V_2 \text{ (Output Voltage)}$$

Minimum Value of the series resistor

$$R_s = \frac{V_s - V_2}{I_2}$$

$$\text{recall } V_s = \frac{20V_{\text{max}}}{\pi}$$

$$V_s = 0.318 \times 20$$

$$V_s = 6.36V_{\text{dc}}$$

$$R_s = \frac{V_s - V_2}{I_2}$$

$$= \frac{6.36 - 10}{500\text{MA}} = -\frac{3.64}{0.5A} = -7.28\Omega$$

(II) Load Resistor Current across the diode at  $500\Omega$

$$I_L = \frac{V_2}{R_L} = \frac{10}{100} = 20\text{MA} \text{ (0.02A)}$$

$$\therefore \text{Zener Current } I_z = I_s - I_L$$

$$= 500\text{mA} - 20\text{MA} = 480\text{MA} \text{ (0.48A)}$$