
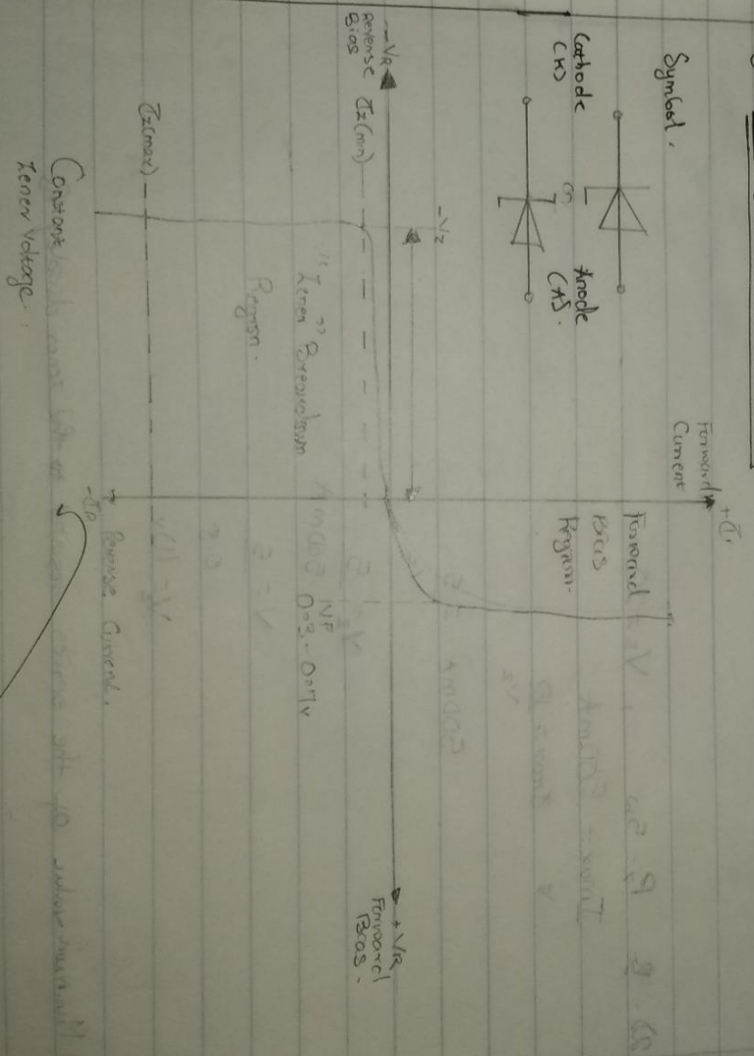


NAME: TUNDE - ADERUWA SORISOLUN
 MATRIC NUMBER: 181ENGG081022
 DEPARTMENT: ELECTRICAL ENGINEERING
 COURSE: BASIC ELECTRICAL ENGINEERING (ENG 212)
 DATE: MAY, 201 2020.

1). Zener Diode Regulator


Zener diodes can be used to produce a stabilised voltage output with low ripple under a varying load current conditions. By passing a small current through the diode from a voltage source via a suitable current limiting resistor (R_s), the zener diode will conduct sufficient current to maintain a voltage drop of V_{z0} .

① I-V Characteristics Curve

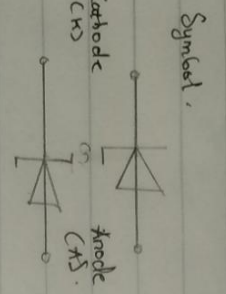

From the I-V characteristics curve above, we can see that the zener diode has a region in its reverse bias characteristics of almost a constant negative voltage regardless of the value of the current flowing through the diode.

11) Circuit Diagram.

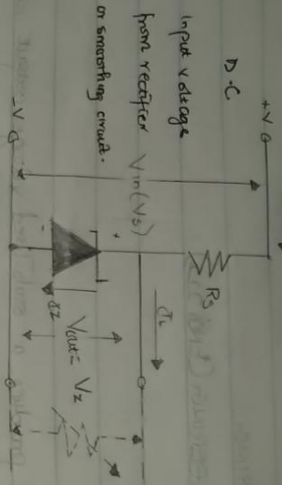

The resistor R_s is connected in series with the Zener diode. Limit the current flow through the diode with the voltage source, V_s being connected across the combination. The stabilised output voltage V_o is taken from across the Zener diode.

20. $R_s = 5 \Omega$, $V_s = 20 \text{ V}$

$I_{max} = 50 \text{ mA}$

$I_{max} = \frac{V}{V_z}$

$50 \text{ mA} \geq \frac{V}{V_z}$

$V_z \geq \frac{V}{50 \text{ mA}}$

$V \geq \frac{V}{0.5}$

$V_z \geq 10 \text{ V}$

1) Minimum value of the series resistor to the Zener diode, R_s

$R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{50 \text{ mA}}$

$= \frac{10}{0.5} = 20 \Omega$

10) Current across the diode at full load of 500Ω , I_L

$$I_L = \frac{V_Z}{R_L} \quad E = 20$$

$$I_L = \frac{10}{500} = 2\text{mA}$$

connected to
across the

shadows
0.2

loadings