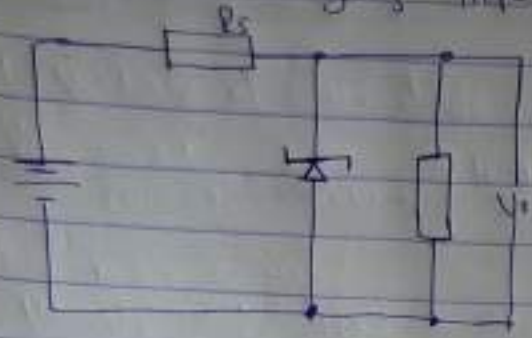


Zener Diode Regulator

This can be described under the following


- 1. Regulation with varying input voltage V_{in}
- 2. Regulation with varying load resistance R_L



When V_{in} increases, input current I_s also increases. This increases the current through zener diode I_z without affecting the load current I_L . With the increase in input current the voltage drop across resistor R_s will also increase thereby keeping the load voltage V_o constant.

When V_{in} decreases, the input current also decreases. This decreases the current through zener diode I_z without affecting the load current I_L . With the decrease in input current the voltage drop across resistor R_s will also decrease thereby keeping the load V_o constant.

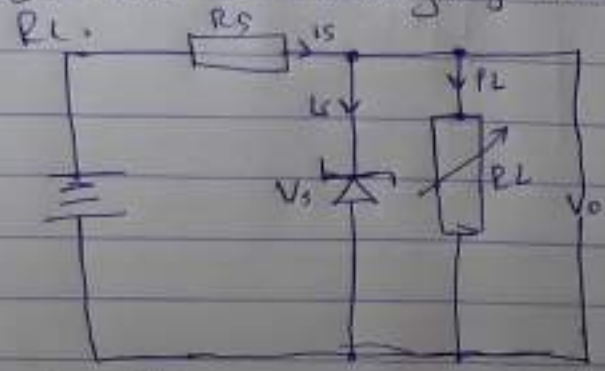2. Regulation with varying load resistance




When R_L increases, the load current I_L decreases. This increases the current through zener diode I_z . As a result of this

the Input Current I_s and voltage drop across R_s remains constant thereby keeping the load voltage V_o constant. when R_L decreases, the load current I_L increases. This increases the Load Current through zener diode I_z and voltage drop across R_s remains constant thereby keeping the load voltage V_o constant.


1 (i) Symbols



I-V Characteristic Curves

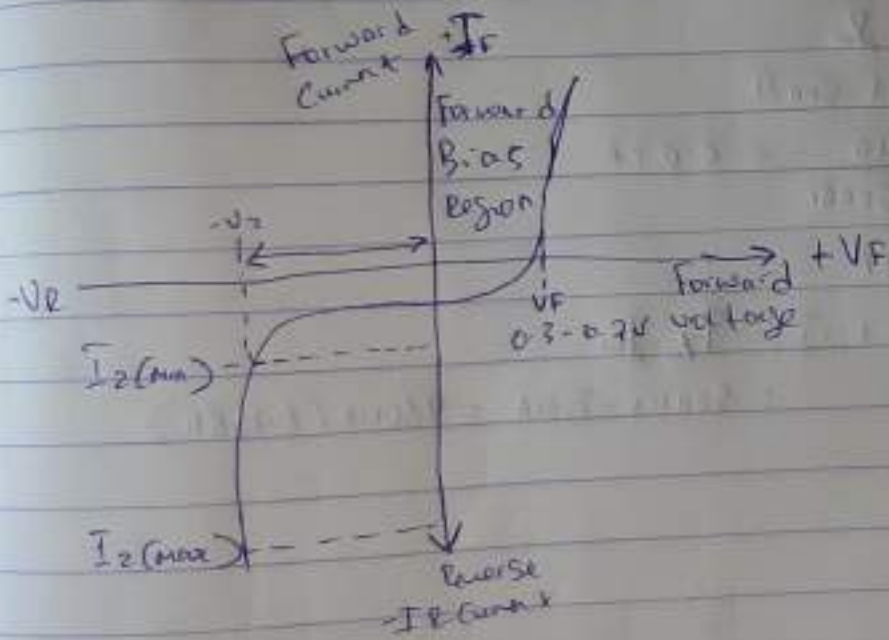

Circuit Diagram

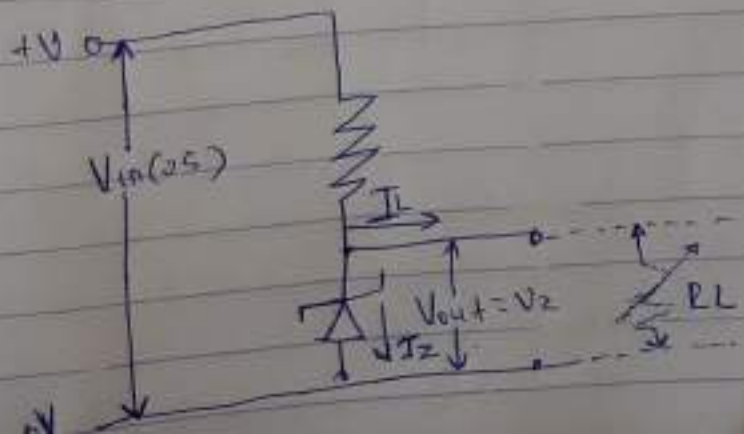

2a) First voltage of zener diode

$$V_z = \frac{\text{Watt}}{\text{Current}} = \frac{5}{500\text{mA}} = 10\text{V}$$

This minimum value

$$R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{500\text{mA}}$$

$$R_s = 20\Omega$$

2b) Current at 500Ω

$$I_L = \frac{V_z}{R_L} = \frac{10}{5000\Omega} = 0.02\text{A}$$

$$I_L = 0.02\text{A}$$

$$\therefore \text{Zener Current: } I_z = I_z - I_L$$

$$= 500\text{mA} - 20\text{mA} = 480\text{mA} (0.48\text{A})$$