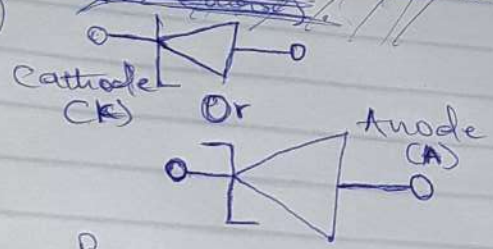



Name: Adewunmi Tolulope Gboyege  
 matric: 181616021008  
 Dept: Computer Engineering  
 Course: Basic Electrical Engineering


Assignment (ENG 222)  
 ① A Zener diode is a diode that behaves like a normal diode but also functions in its

breakdown region to regulate voltage, when voltage is reversed in the Zener diode. It allows the flow of current in that direction and it takes in more current at the same voltage. When the voltage is reversed, this the reverse bias voltage exceeds the Zener voltage, the voltage across it will be constant.



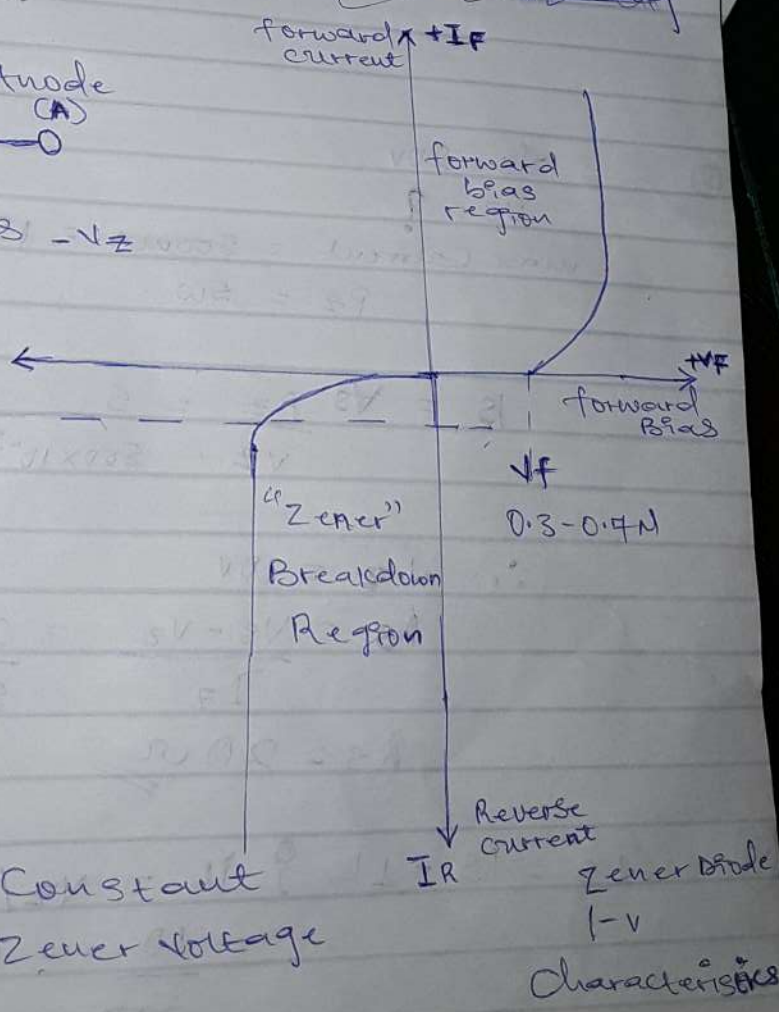Reverse Bias  $-V_Z$   
 $V_R$   
 $I_{Z(max)}$



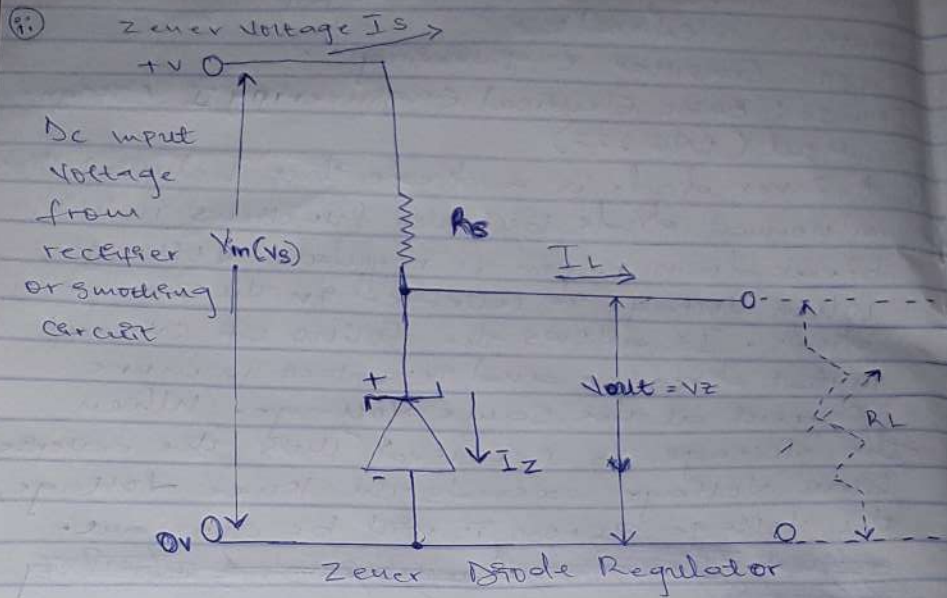

②

$$V_S = 20V$$

$$V_Z = ?$$

$$\text{max Current} = 500\text{mA} = 1S$$

$$P_Z = 5W$$

$$1S = \frac{V_S P_Z}{V_Z} = \frac{5}{500 \times 10^{-3}} = 10V$$

$$\therefore V_Z = 10V$$

$$R_S = \frac{V_S - V_Z}{I_Z} = \frac{20 - 10}{500 \times 10^{-3}} = \frac{10}{500 \times 10^{-3}} = 20\Omega$$

$$R_S = 20\Omega$$

③

$$I_Z = 1S - I_L \quad \& \quad I_L = \frac{V_Z}{R_L}$$

$$= \frac{10}{500} = 0.02\Omega$$

$$= 20\text{mA}$$

$$\therefore I_Z = (500 - 20)\text{mA} = 480\text{mA}$$