

Ajani Abdulsalam Ajibola

181ENG03/010


Civil Engineering

ENG 222


1 Describe a Zener diode regulator

Zener diodes are widely used as shunt voltage regulators to regulate voltage across small loads. Zener diodes have a sharp reverse breakdown voltage and breakdown will be constant for a wide range of currents. Thus we will connect the Zener diode parallel to the load such that the applied voltage will reverse bias it. Thus if the reverse bias voltage across the Zener diode exceeds the knee voltage, the voltage across the load will be constant.

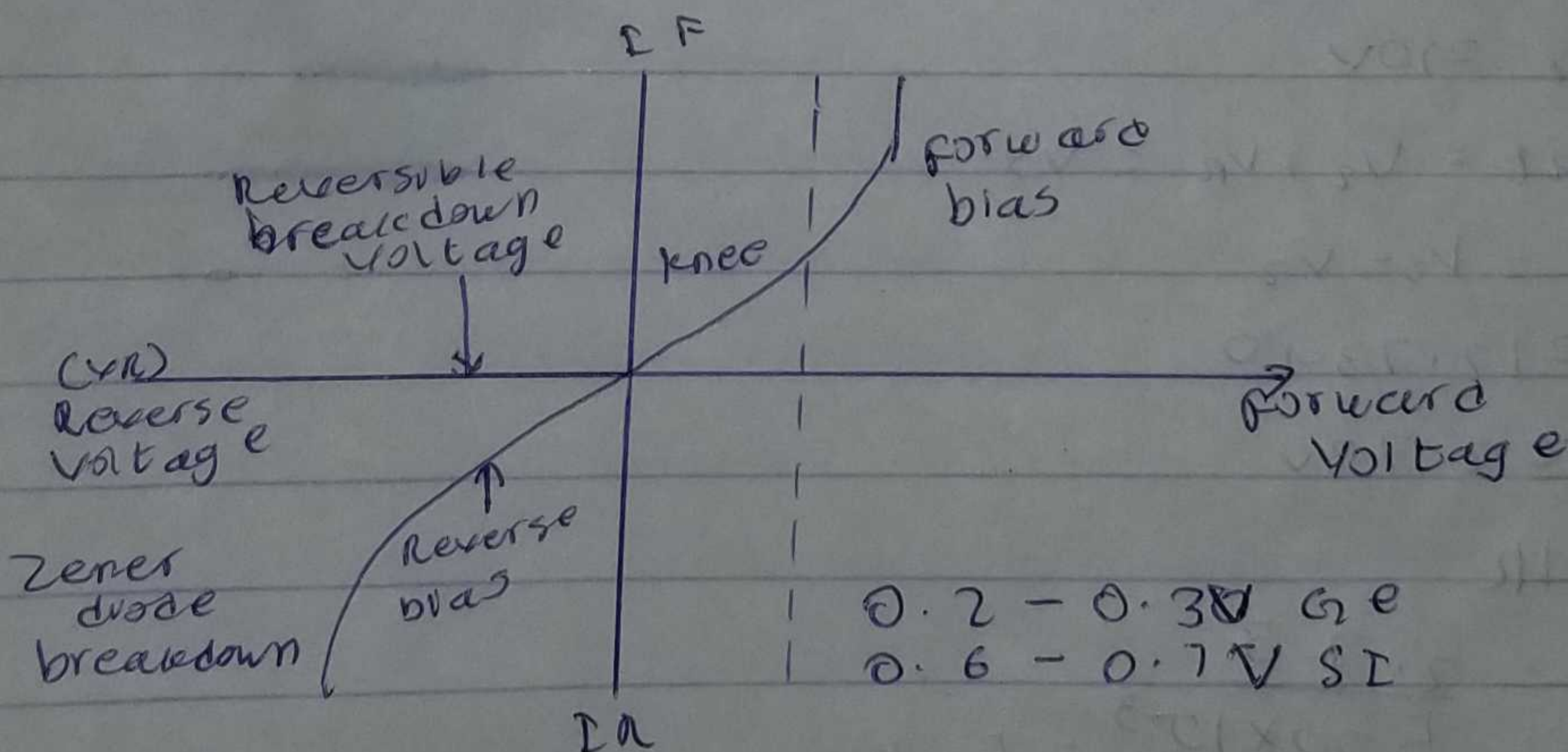1) sketch the symbol and $I-V$ characteristic curve



ii) Sketch and label the circuit diagram

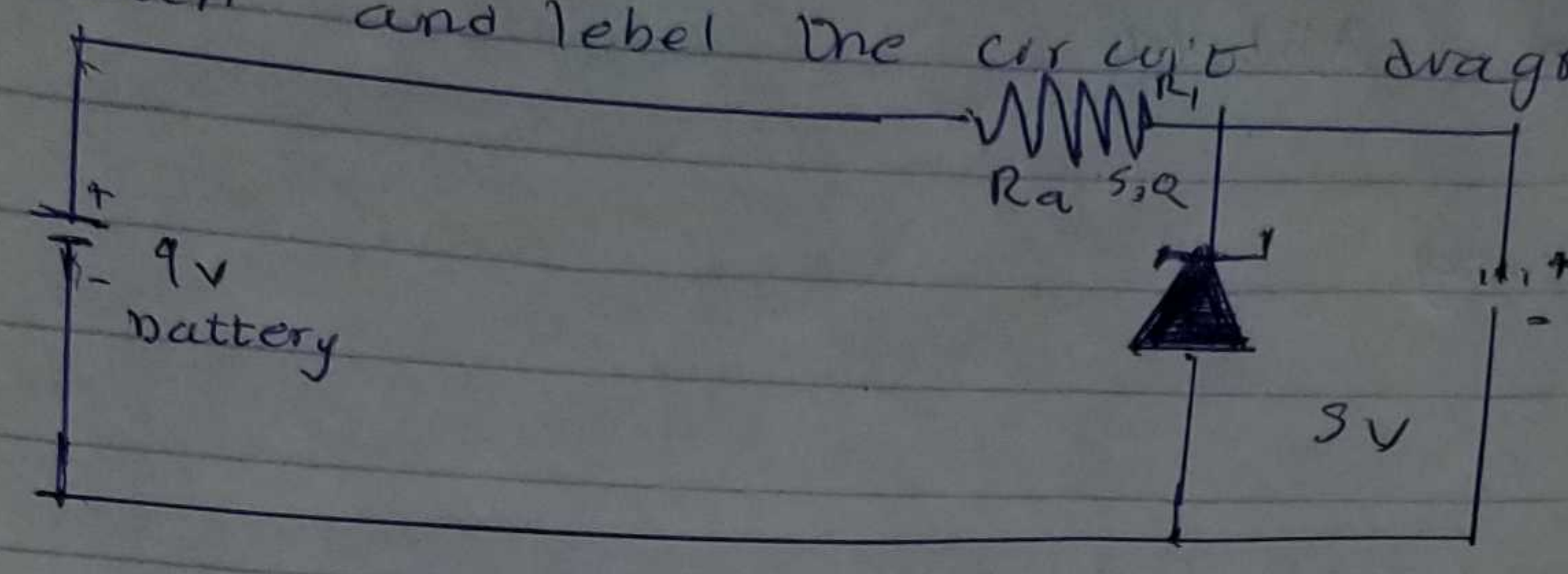

2) $P_z = 5 \text{ W}$
 $I = 500 \text{ mA}$
 200 V max

To convert V_{max} to V_{OC}

$$V_{\text{DC}} = \frac{2 \times V_{\text{max}}}{\pi}$$

$$V_s = \frac{2 \times 20}{\pi} = 12.73 \text{ V OC}$$

Recall that $P = IV$

$$\therefore V_z = \frac{P_z}{I_z} = \frac{5}{500 \times 10^{-3}}$$

$$V_z = 10 \text{ V}$$

Recall that $V_s = V_z + V_R = V_s$

$$V_R = V_s - V_z$$

$$= 12.73 - 10$$

$$= 2.73 \text{ V}$$

$$\therefore V = IR$$

$$R = \frac{V}{I} = \frac{2.73}{500 \times 10^{-3}} = 5.46$$

Since r_z is connected in series and same current flows

$$I_s = I_z + I_c$$

$$I_z = I_s - I_c$$

$$I_z = \frac{V_z}{r_z}$$

$$= \frac{10}{500} = 0.02 \text{ A} = 20 \text{ mA}$$

$$I_z = 500 \text{ mA}$$

$$= 20 \text{ mA}$$

$$= 480 \text{ mA} \setminus 0.48 \text{ A}$$