
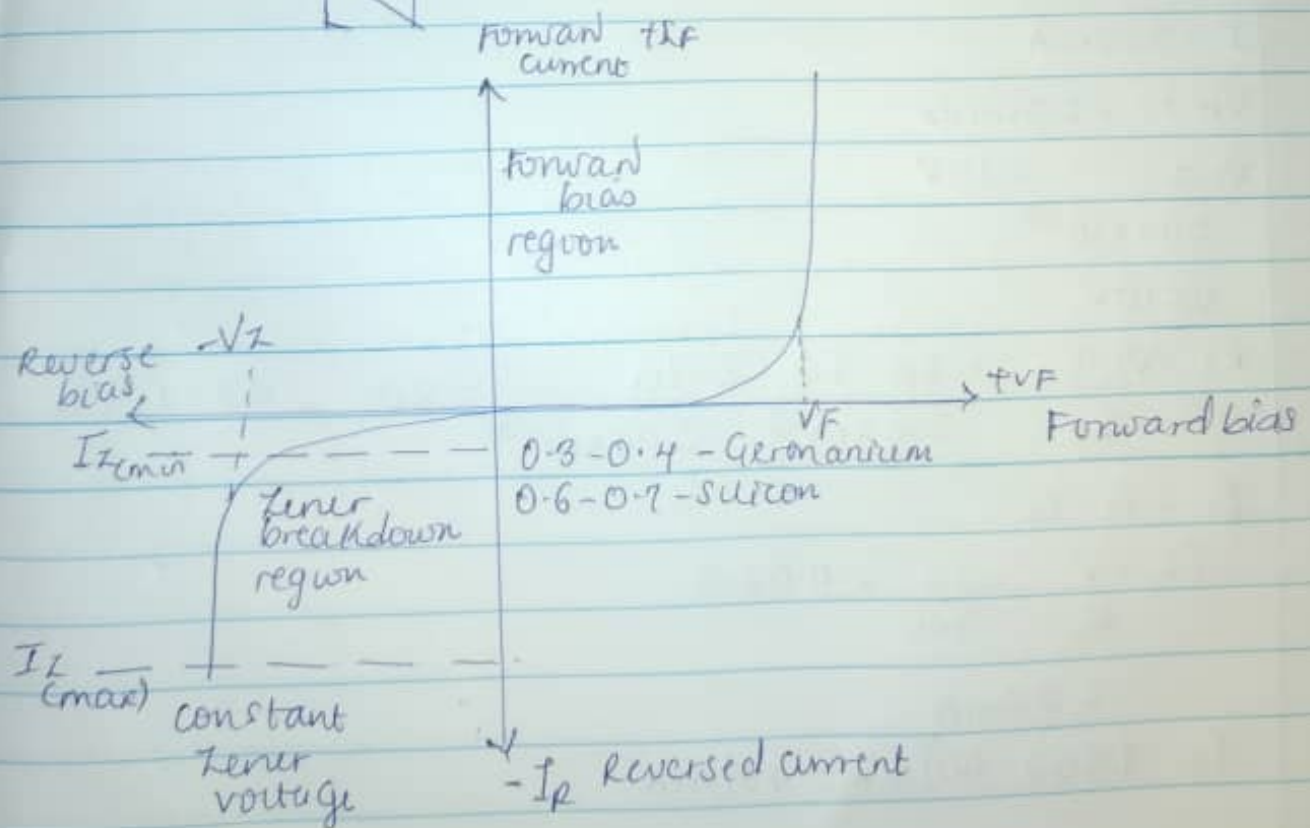


030, Oluwadara Toluwani


Basic Electrical Engineering II

18/ENG02/072

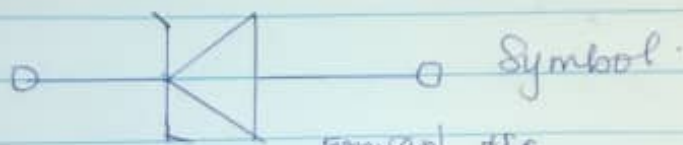1. A Zener diode is always operated in its reversed biased condition. The constant reverse voltage  $V_Z$  of the Zener diode makes it a valuable component for the regulation of the output voltage against both variations on the input voltage from an unregulated power supply in the load resistance. A Zener diode regulator is a shunt regulator used to regulate voltage across small loads. It steps down the input voltage and limits the current into the diode.



IV- characteristics curve.

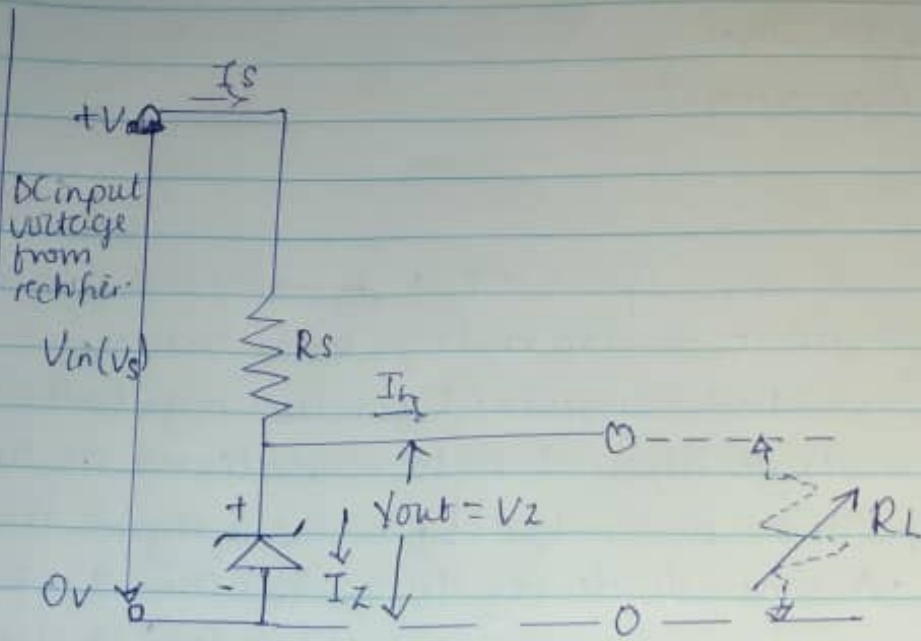

Zener diode regulator

2  $P = 5W$

$I = 500mA$

$V_{max} = 20V_{max}$

$V_s = \frac{P}{I} = \frac{5}{500 \times 10^{-3}} = 10V$

$V_z = 10V$

$R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{500 \times 10^{-3}} = \frac{10}{500 \times 10^{-3}} = 20$ ,  $R_s = 20 \Omega$

$I_z = I_s - I_L$

$I_L = \frac{V}{R_L} = \frac{10}{500} = 0.02 \Omega$

$= 20mA$

$I_z = (500 - 20) mA = 480mA$