

1.

NAME: SUNDNY WINNER CATHCOURM


COURSE:

MATRIC: 18/ENG05/057


DEPT: MECHATRONIC ENGINEERING

BASIC ELECTRICAL ENGINEERING ASSIGNMENT SOLUTION

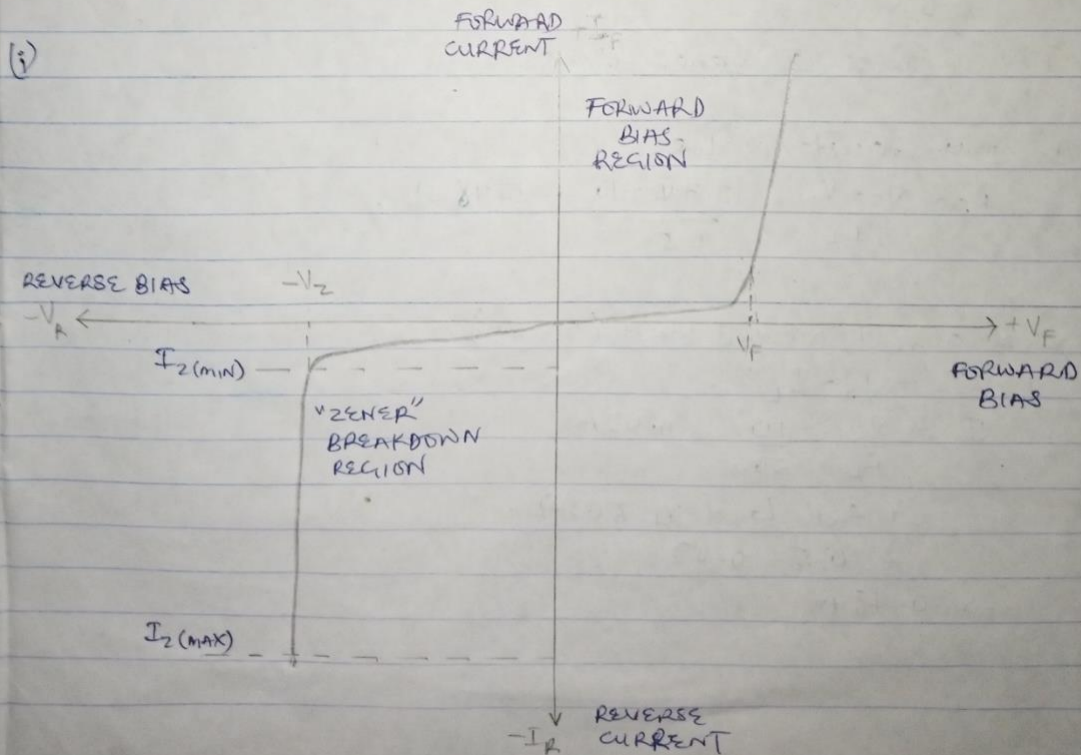(i) The zener diode is like a general purpose signal diode. When biased in the forward direction, it behaves just like a normal signal diode, but when a reverse voltage is applied to it, the voltage remains constant for a whole wide range of currents. The reverse voltage can increase until the diode breakdown voltage is achieved. This point is called the "avalanche ~~region~~ breakdown region". At this point maximum current will flow through the zener diode. This point of breakdown is called the "zener voltage". At its reverse bias, the diode has a constant negative voltage regardless of the current flowing through the diode and remains ~~constant~~ nearly constant even with large changes in current as long as zener diode current remains nearly constant between the breakdown current and the maximum current.




(ii)

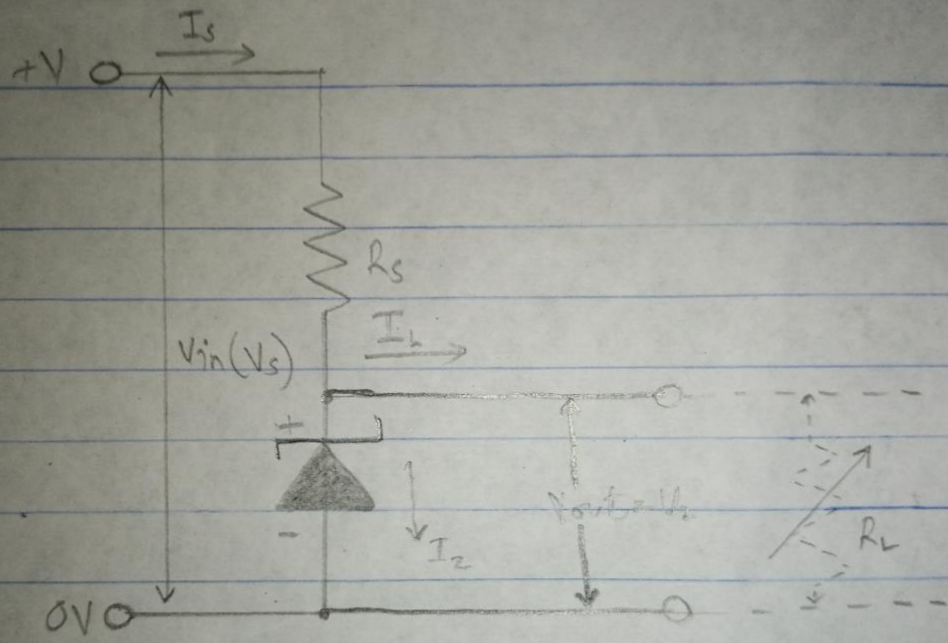

2.

(2) Power = $SW = P_r$

$I_s = 500 \text{ mA} = 0.5 \text{ A}$

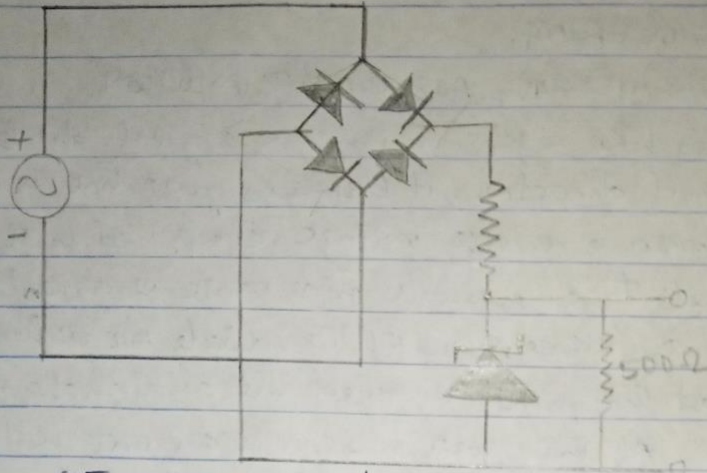

Since $V_{\text{max}} = 20 \text{ V}$

$V_{\text{DC}} = 0.637 \times V_{\text{max}} = 0.637 \times 20 = 12.74 \text{ V} = V_s$

$\therefore 12.74 \text{ V}$ produced from A-C source.

(a) Power = current \times voltage

$SW = 0.5 \text{ A} \times V_2$

$V_2 = \frac{5}{0.5} = 10 \text{ V}$

$\therefore 10 \text{ V}$ is across the zener diode

Minimum resistor value:

$R_s = \frac{V_s - V_2}{I_2} = \frac{12.74 - 10}{0.5} = 5.48 \Omega //$

(b) zener current at full load (500Ω)

$I_2 = I_s - I_L$

$I_L = \frac{V_2}{R_L} = \frac{10}{500} = 0.02 \text{ A}$

I_2 at full load of 500Ω ;
 $= 0.5 - 0.02$

$\Rightarrow 0.48 \text{ A} //$