
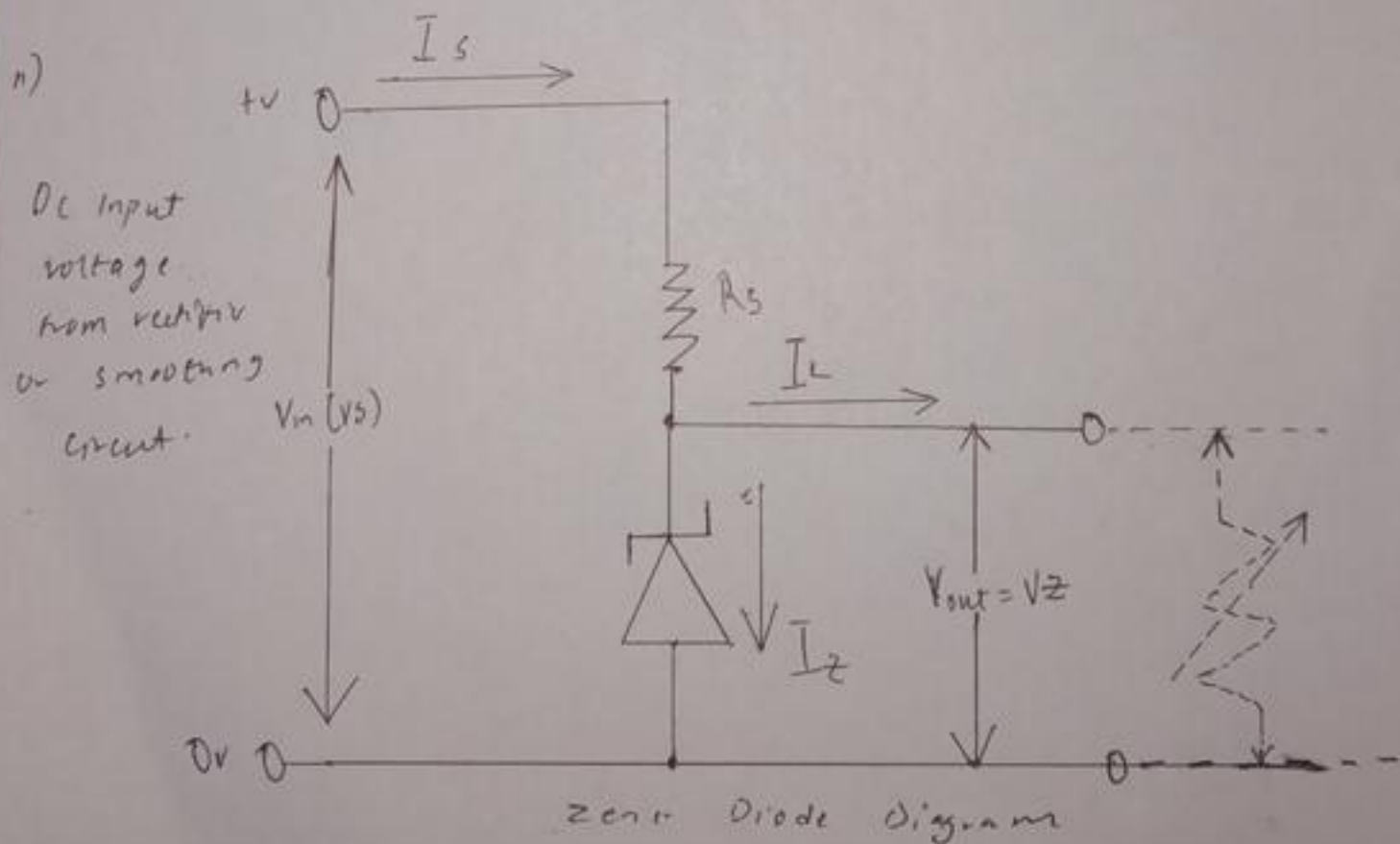
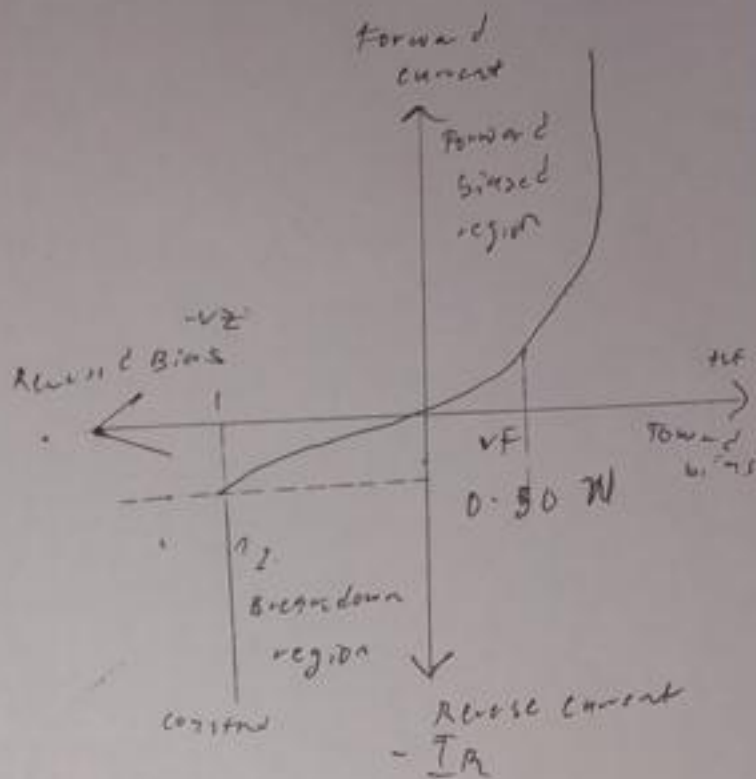


Name: Egbuho Oghenechuko Jeffrey

Department: Computer Engineering

mat no: 18/Engo2/035

Course: Basic Elect

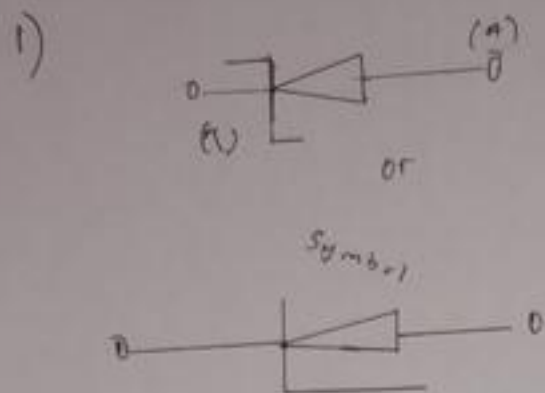

Q 2.

$$V_3 = 20V$$

$$V_2 =$$

$$\text{max current} = 500 \text{ mA} = 0.5$$

$$P_3 = \frac{5W}{V} = 0.5A$$

$$V_2 = 10 \text{ volts}$$

$$\text{minimum resistance} = \frac{V_3 - V_2}{I_2}$$

$$V_{dc} = 0.637 V_m$$

$$= 0.637 \times 20$$

$$= 12.74 \text{ dc}$$

$$\text{minimum resistance} = \frac{12.74 - 10}{0.5} = 5.48 \Omega$$

$$\therefore \text{load current } I_L = \frac{V_2}{R_L} = \frac{10}{500} = 0.02A \text{ or } 20mA$$

$$I_2 = I_3 - I_L$$

$$= 500 - 20$$

$$= 480 \text{ mA}$$