

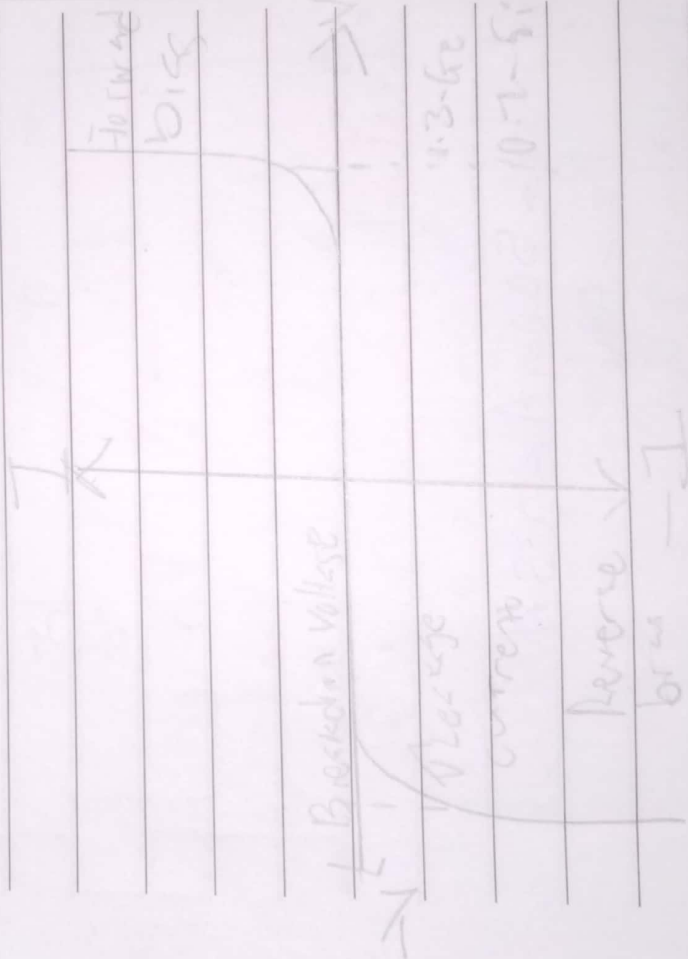


Nixon Victory
18/ENG04/0523
Elect - Elect
ENG 222

D

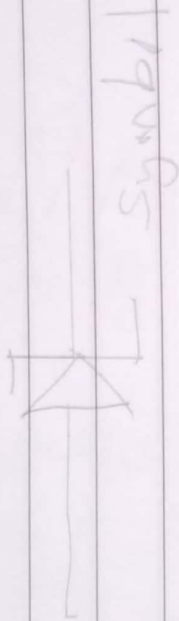

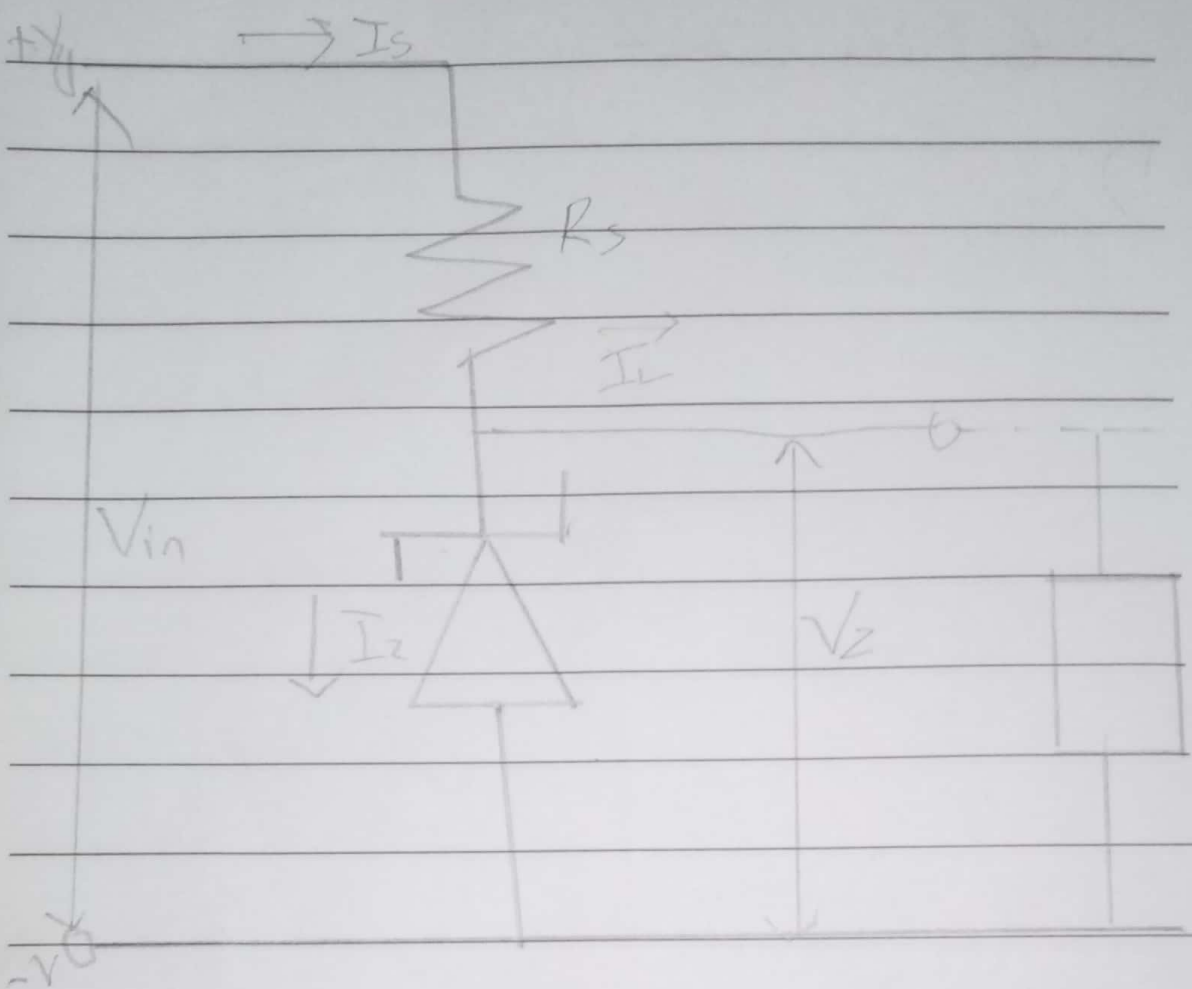

2) $I_z = 500 \text{ mA} = 0.5 \text{ A}$
 $P_z = 5 \text{ W}$
 $V_{in} = 20 \text{ V}$
 $V_z = ?$
 $R_s = ?$
 $I_z (\text{Full load}) = ?$



$$V_2 = 0.638 V_{in} = 0.638 \times 20 = 12.72V$$

$$P_2 = \frac{1}{2} V_2$$

$$V_2 = \frac{P_2}{I_2} = \frac{5}{0.5} = 10V$$

$$1) R_s = \frac{V_s - V_2}{I_L} = \frac{12.72 - 10}{0.5} = 5.44\Omega$$

5.1 I_2 at full load

I_L = load current = ?

5.1 full load $V_2 = V_L$

At load of 500Ω $I_s = I_L + I_2$

$$I_s = 500\mu A$$

$$I_L = \frac{V_2}{R_L} = \frac{10}{500\Omega} = 20\mu A$$

$$I_2 = I_s - I_L = 500 - 20 = 480\mu A$$