



OKEKE CHIDERA SAMUELLA

18/ENG08/014


Biomedical engineering.

1) A zener diode as a voltage regulator is a silicon semiconductor with a p-n junction that is specifically designed to work in the reverse biased condition. It consists of a current limiting resistor R_s connected in series with the input voltage V_s with the zener diode connected in parallel with the load R_L in this reverse biased condition.

i) symbol.

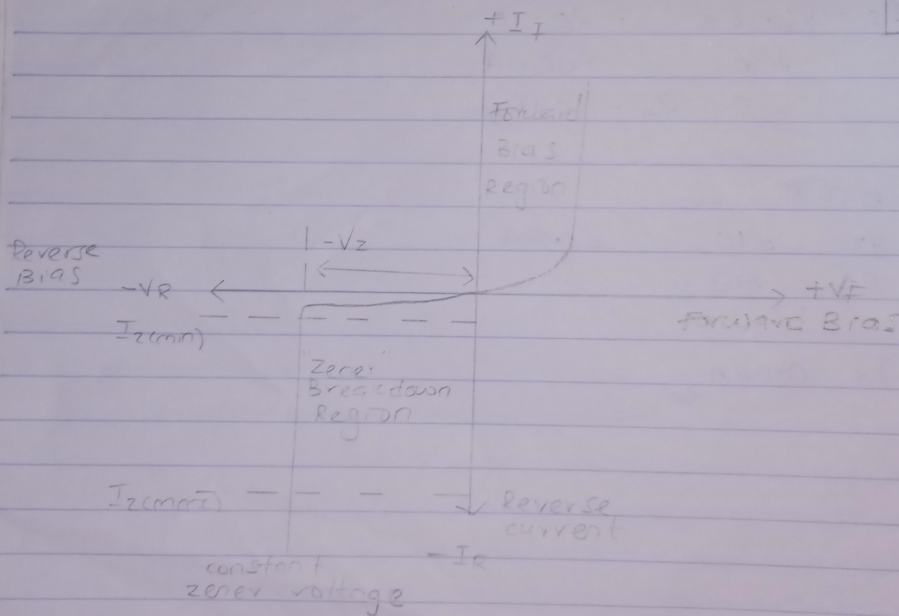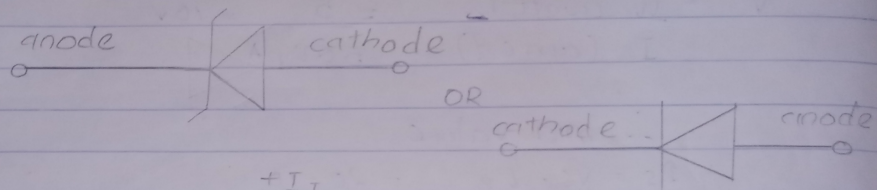

I-V characteristic curve

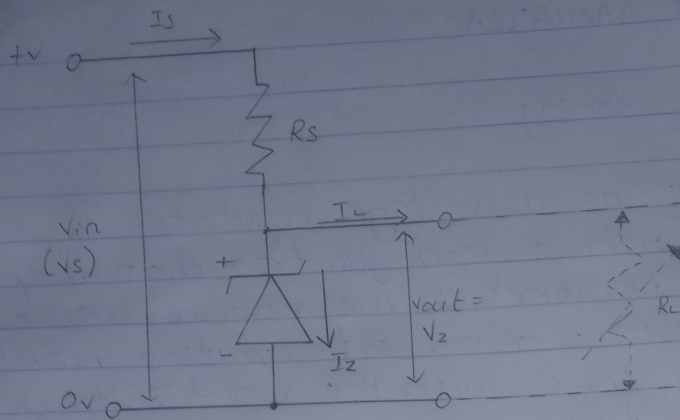

circuit diagram of a zener diode regulator.

2a) First v_z of the zener diode

$$V = \frac{W \text{ (watt)}}{I \text{ (current)}} = \frac{5}{500 \text{ mA}} = 10 \text{ V}$$

\therefore min value

$$R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{500 \text{ mA}}$$

$$R_s = 20 \Omega //$$

b) I at 500Ω

$$I_z = \frac{V_z}{R_L} = \frac{10}{500 \Omega} = 0.02 \text{ A}$$

$$\therefore I_z = 0.02 \text{ A} //$$

$$R_2 = (500 - 20) = 480 \Omega //$$